

ELECTRONIC TELEPHONE



นาย เกษม	วศิธรวิสุทธิ	เลขประจำตัว	31-3003
นาย สานิต	แซ่เอี่ยม	เลขประจำตัว	31-3027



ปริญญาบัตรเป็นส่วนของการศึกษาตามหลักสูตรปริญญาอุตสาหกรรมศาสตรบัณฑิต
 ภาควิชาเทคนิคอุตสาหกรรม
 คณะวิศวกรรมศาสตร์
 สถาบันเทคโนโลยีพระจอมเกล้า เจ้าคุณทหาร ลาดกระบัง

027954

ปริญญาโทศึกษาศาสตร์ 2533

เรื่อง Electronic Telephone

ผู้จัดทำ

1. นาย เกษม วศิษฐวิสาhti 31-3003

2. นาย สานิต แซ่เอี้ยบ 31-3027

..... อาจารย์ที่ปรึกษา
(..... นพ. พงษ์พร...

..... อาจารย์ที่ปรึกษา
(..... นพ. นพ. ...)

..... อาจารย์ที่ปรึกษา
(.....)

เลขหมึ T. 33181 ก 5
เลขทะเบียน 027954
วัน, เดือน, ปี 180.0.44

สารบัญ

หน้า

กิจกรรมประกาศ	1
บทนำ	2
TONE DIALING (DTMF) AND PULSE DIALERS	13
PULSE DIALER	14
THE ELECTRONICS RINGER	22
TELEPHONE SET VOICE CIRCUITRY	31
THE CENTRAL OFFICE	45
SUBSCRIBER'S LINE INTERFACE CIRCUITRY	46
PULSE CODE MODULATION AND CODEC	56
DELTA MODULATION	66
LINE CODING OF DIGITAL TRANSMISSION AND TSAC	75

กิติกรรมประกาศ

ขอขอบพระคุณอย่างสูงต่อ ดร. กนก เจนจิระมงคลเวช ในฐานะอาจารย์ที่ปรึกษาในการให้คำปรึกษาและ แนะนำเรื่องการทำปริญญาโท

นาย เกษม วศิธรวิสุทธิ

นาย สานิต แซ่เอี่ยม

ภาควิชา เทคโนโลยีสารสนเทศ

สถาบันเทคโนโลยี พระจอมเกล้าเจ้าคุณทหารลาดกระบัง



เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า
ไม่ว่ากรณีใดๆทั้งสิ้น อีกทั้งห้ามมิให้ตัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

เครื่องโทรศัพท์

การตอบสนองความต้องการในทางการค้าและอุตสาหกรรม, ซึ่งเหมือนกับความต้องการในเรื่อง เครื่องคอมพิวเตอร์, เคเบิลทีวีโอเกมส์, และโทรภาพที่เพิ่มมากขึ้น ระบบโทรศัพท์ที่ทำงานด้วยระบบอะนาลอก ก็จะถูกเปลี่ยนมาเป็นระบบดิจิตอล การเปลี่ยนรูปแบบจากอะนาลอกมาเป็นดิจิตอล เริ่มต้นในปี ค.ศ 1950 เมื่อ PULSE-CODE MODULATION (PCM) ถูกนำมาใช้ในสำนักงานส่วนกลาง ตั้งแต่นั้นเป็นต้นมา เครื่องมือที่ทำงานด้วยระบบดิจิตอลก็ได้เข้ามาแทนที่อุปกรณ์กึ่งอิเล็กทรอนิกส์ เป็นความตั้งใจอันยิ่งใหญ่ที่จะขยายขีดความสามารถของสำนักงานส่วนกลาง ให้มีประสิทธิภาพมากยิ่งขึ้นกว่าเดิม ในการที่จะรับมือกับการใช้โทรศัพท์จำนวนมาก ๆ และการใช้ดิจิตอลคอมพิวเตอร์ที่เพิ่มมากขึ้น ผลของการเปลี่ยนแปลงที่สำนักงานส่วนกลางระหว่างประเทศเป็นสิ่งที่เห็นได้อย่างง่ายดาย หลังจากที่พนักงานโทรศัพท์ทำการนัดหยุดงาน ในปี ค.ศ 1983 บริษัทโทรศัพท์ประกาศว่า ระบบโทรศัพท์ระหว่างประเทศยังคงทำงานด้วยประสิทธิภาพ 95 เปอร์เซ็นต์ ด้วยการนำเอาระบบคอมพิวเตอร์มาเสริมกับการที่ผู้ใช้บริการหมุนโทรศัพท์ได้โดยตรง ระบบก็เกือบจะกลายเป็นอัตโนมัติ เต็มที่ความสนใจอยู่ที่การเปลี่ยนเครื่องโทรศัพท์ของผู้ใช้บริการจากแบบ อะนาลอกมาเป็นแบบดิจิตอล และการเปลี่ยนสายเคเบิลทองแดงมาเป็นสายเคเบิลที่ใหม่กว่า และมีประสิทธิภาพมากกว่า การเปลี่ยนระบบโทรศัพท์จากอะนาลอกมาเป็นระบบดิจิตอล จะเป็นการเพิ่มความสามารถให้กับผู้ผลิตชิ้นส่วนที่จำเป็นได้อย่างไม่ยากนัก และต้นทุนลดลงด้วยการลดขนาดและน้ำหนักของอุปกรณ์ที่จำเป็น และลดการใช้วัสดุที่มีราคาแพงในการผลิตในขณะเดียวกัน การเพิ่มการให้บริการก็จะเกิดขึ้น การพัฒนาทั้งหมดจะขึ้นกับระบบโทรศัพท์เหมือนกับที่เกิดขึ้นกับสิ่งอื่น ๆ ซึ่งเป็นวิถีทางของวิวัฒนาการ ไม่มีการเปลี่ยนแปลงอย่างฉับพลันและไม่ยอมให้มีแนวความคิดที่มีผลกระทบอย่างกว้างขวาง สายโทรศัพท์มีอยู่ทั่วไปในอเมริกา และจะถูกใช้ต่อไปอีกหลาย ๆ ปี อย่างไรก็ตามโทรศัพท์กำลังมีการเปลี่ยนแปลงอย่างรวดเร็ว และ IC HIGH-DENSITY กำลังเข้ามาแทนที่ RINGER, CARBON MICROPHONE และ TRANSFORMERS

โทรศัพท์ที่ไม่ค่อยคล่องตัวก็กำลังกลายมาเป็นโทรศัพท์ที่มีความคล่องตัว อุปกรณ์พิเศษที่ทำให้มีความคล่องตัวที่สัมพันธ์กับเทคโนโลยีทางด้านคอมพิวเตอร์ กำลังได้รับการออกแบบ ท้ายที่สุดการออกแบบโทรศัพท์แบบดิจิตอลที่รวมเอา IC ใหม่ ๆ เข้าไว้ด้วยกันก็จะกลายเป็นเรื่องจริง

องค์ประกอบของเครื่องโทรศัพท์

1. HOOK SWITH
2. RINGER
3. LINE-BALANCING และ SIDETONE COMPONENT
4. อุปกรณ์ป้องกัน FLASH-VOLTAGE
5. SWITH และหน้าปัทม์
6. TRANSDUCERS
7. โครงสร้างที่จะระบุองค์ประกอบด้านบน

การออกแบบโทรศัพท์แบบดิจิตอลซึ่งขึ้นอยู่กับความคล่องตัวของอุปกรณ์ต่าง ๆ นั้น ต้องการ
ใช้ IC มาแทน RINGER, วงจร UTILIZED VOICE, BALANCE และ SIDETONE ELECTRONICS
แอมป์รีไฟเออร์สำหรับ LINE-LOSS COMPENSATION, ไมโครโฟนแบบ SOLID-STATE ที่มีคุณสมบัติที่
ดีกว่า หน้าปัทม์แบบเดิมก็ถูกแทนที่ด้วยแบบกดปุ่ม ด้วยการลดขนาดขององค์ประกอบที่ใช้ก็เลยทำ
ให้โทรศัพท์มีน้ำหนักเบา และมีที่ว่างพอที่จะใช้ไปในการปรับปรุงทำอย่างอื่น สิ่งใหม่ ๆ ที่เพิ่มให้กับ
โทรศัพท์ ก็คือการใช้ UNIVERSAL DATA LINK TRANSCEIVERS (UDLT). IC ชนิดนี้มีอยู่ใน
เครื่องโทรศัพท์ ทำให้เกิดการผสมกันของเสียงแบบ DIGITIZE กับข้อมูลของคอมพิวเตอร์และภาพ
ของวิดีโอหรือแฟลชไมล์ ความสำคัญอีกอย่างที่ไม่ยิ่งหย่อนไปกว่ากันก็คือ LOOP ของผู้ใช้บริการสาย
สองเส้นยังคงใช้ได้อยู่ด้วยการติดตั้ง อุปกรณ์ UDLT CODEC กับ VOICE FILTER และ COMPANDER/
EXPANDER สามารถที่จะถ่ายทอดจากศูนย์ไปยังเครื่องโทรศัพท์ได้ เมื่อ INPUT/OUTPUT ของโทร-
ศัพท์ถูก DIGITIZE จนเต็ม เครื่องโทรศัพท์ก็ยังสามารถติดต่อกันได้ ความสามารถชนิดจะมีความ
สำคัญที่สุดต่อการติดตั้งระบบ VOCAL PRIVATE-BRANCH EXCHANGE (PBX) ในส่วนนี้จะได้ทำการ
ศึกษาอุปกรณ์ IC ใหม่ ๆ ที่ถูกออกแบบให้มาใช้ในเครื่องโทรศัพท์ อุปกรณ์ที่ก้าวหน้ามาก ๆ ซึ่งรวม
เอาวงจรหลาย ๆ วงจรไว้ใน IC ตัวเดียว จะไม่ใช้มาเป็นตัวอย่าง แต่โดยทั่วไปจะใช้อุปกรณ์ที่ทำ
ให้ผู้ทำการศึกษานำเข้าใจถึงแนวความคิดอย่างถ่องแท้ ทั้งนี้จะไปเกี่ยวข้องกับการผลิต LARGE-SCALE
IC ที่จะใช้กับระบบโทรศัพท์และการสื่อสารแบบดิจิตอลด้วย

การทดลองที่ 7

SUBSCRIBER'S LOOP และการส่งสัญญาณ

ขอบเขตที่จะศึกษา

1. LOOP ของสายเคเบิลที่เชื่อมต่อระหว่างผู้ใช้บริการกับศูนย์
2. การส่งสัญญาณที่เหมือนกับการส่งตามสายที่ยาวกว่านี้ ซึ่งเป็นการให้คำแนะนำทั้งกับผู้ใช้และผู้ปฏิบัติงานเกี่ยวกับสถานะภาพของสาย

วัตถุประสงค์

เมื่อทำการศึกษานี้จบจะสามารถ

1. อธิบายถึง คุณสมบัติโดยทั่วไปของ SUBSCRIBER'S LOOP
2. อธิบายถึงการใช้ DC LOOP เพื่อ MODULATION VOICE และการค้นหา ON OFF HOOK
3. อธิบายถึง ชนิดของสัญญาณที่ส่ง ไปยังผู้ใช้ เพื่อบอกสถานะภาพของสาย สัญญาณนี้ยังถูกส่ง ไปยัง ศูนย์ด้วย


ผู้ใช้โทรศัพท์ทุก ๆ คนจะเชื่อมต่อเข้ากับศูนย์ด้วยคู่สายซึ่งใช้อ้างถึง เหมือนกับเป็น SUBSCRIBER'S LOOP และเป็นที่รู้จักว่าเป็น LINE-SIDE INTERFACE SUBSCRIBER'S LOOP จะ อยู่ใน LEAD-COVERCABLE สาย TRUNK CABLE ระหว่างศูนย์ถือว่าเป็น TRUNK-SIDE INTERFACE INTERFACE อยู่ในรูปของ MATCHING DEVICE ซึ่งเหมือนกับ TRANSDUCER เพื่อให้ได้การทำงานที่มีประสิทธิภาพจาก INTERFACE ดังเช่น SUBSCRIBER'S LOOP จึงมีความจำเป็นเมื่อทำการ MATCH LOOP โทรศัพท์ของผู้ใช้บริการกับศูนย์ จึงจำเป็นที่จะต้องรู้ความต้องการที่มีลักษณะของ LOOP ใดๆก็ตาม ในปัจจุบันจำนวนคู่สาย INTERFACE ที่ใช้กันอยู่อาจจะเป็นสิ่งที่มีความสำคัญน้อยที่สุด ที่ บริษัทโทรศัพท์จะทำการเปลี่ยนแปลง ศูนย์จะให้ความสามารถในการทำงานกับ LINE-SIDE INTERFACE ด้วย BORSOHT : BATTERY POWER (-48V), OVER-VOLTAGE และการทดสอบ เต็มวันได้นำเอา FUNCTION หลายอย่างมาใช้ โดยใช้ร่วมกับส่วนที่มีความสัมพันธ์กัน ภายใน IC ที่ติดตั้งอยู่ที่ศูนย์เพื่อที่จะทำให้เกิด BORSOHT FUNCTION เรียกว่า SLIC (SUBSCRIBER'S LOOP INTERFACE CIRCUIT) การทำงานของ SLIC จะอธิบายอยู่ในการทดลองอื่นต่างหาก ในส่วนนี้ลักษณะเฉพาะที่มีความสำคัญที่สุดบางอย่างของ TWISTED-WIRE LOOP จะถูกนำมาใช้ จะทำการศึกษาย่างคร่าว ๆ เกี่ยวกับ CABLE LOSS INDUCTANCE และ CAPACITY, BAND WIDTH, COMMON MODE หรือ LOGITUDINAL SIGNALS, ECHOS ON LINE และขนาดของสาย และการซ่อมบำรุง สายหนึ่งของ SUBSCRIBER'S LOOP จะเรียกว่า TIP หรือ L2, และอีกเส้นหนึ่งจะเรียกว่า RWE หรือ L1

ไม่ว่ากรณีใดๆทั้งสิ้น อีกทั้งห้ามมิให้ตัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

ซึ่งนี้ได้มาจาก การใช้งานด้วยมือของพนักงาน SWITCHBOARD คู่สาย L1 และ L2 เป็น METALLIC CONDUCTORS ปลั๊กและสายซึ่งนำมาใช้งานและ BALANCE ด้วย EARTH & ROUND RING จะต่อเข้ากับ -48V SUPPLY ซึ่งเทียบกับกราวด์สัญญาณของผู้ใช้ทั้งหมด และสถานะภาพของสายจะประมาณได้จากค่ากระแสที่ไหลผ่านวงจรถัด รูปที่ 7.1 แสดงให้เห็นวงจรแบบง่ายของ INTERFACE ของโทรศัพท์ระหว่างผู้ใช้ 2 คน ศูนย์จะให้ TALKING BATTERY (-48V) ซึ่งจ่ายกระแสเพื่อให้ CARBON BUTTON MICROPHONE ทำการ MODULATE หรือ เพื่อให้พลังงาน ELECTRONIC กับโทรศัพท์ที่ทันสมัยมากขึ้น ไมโครโฟนที่อยู่ในโทรศัพท์มาตรฐาน MODEL 500 ซึ่งเป็นโทรศัพท์แบบที่ใช้กันอยู่มาก DRAIN โดยเฉลี่ย -20 -30 mA ที่ศูนย์จะตรวจสอบ LINE CURRENT โดยใช้ LOOP RELAY ซึ่งสามารถตรวจวัดได้เมื่อโทรศัพท์ถูกยกขึ้นจาก HOOK SWITH RELAY ถูกกำหนดให้ทำงานที่ 20 mA อย่างไรก็ดี กระแสอาจจะมากกว่า 100 mA ขึ้นอยู่กับความ LOOP RESISTANCE รูปที่ 7.2 แสดงให้เห็นถึงองค์ประกอบหลักซึ่งทำให้เกิด LOOP RESISTANCE


LOOP RESISTANCE

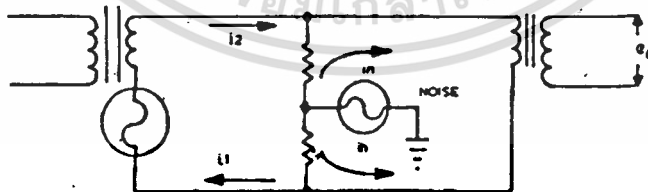ในศูนย์บางแห่งความต้านทานรวม (R_T) ของ RESISTOR R1 และ R2 เท่ากับ 400-800 ที่ 400 LOOP CURRENT ในระบบมาตรฐานจะอยู่ในช่วง 20-126 mA ด้วย SUPPLY - 48V เมื่อเทียบกับกราวด์บางประเทศในยุโรปใช้ช่วงความต้านทาน 380-780 เป็นค่ามาตรฐาน เครื่องโทรศัพท์ของผู้ให้บริการประกอบไปด้วย CARBON MICROPHONE, HYBRID TRANSFORMER และจะมีค่า EQUIVALENT RESISTANCE 400




Differential and Common-Mode Signals on Lines

FIGURE 7-3

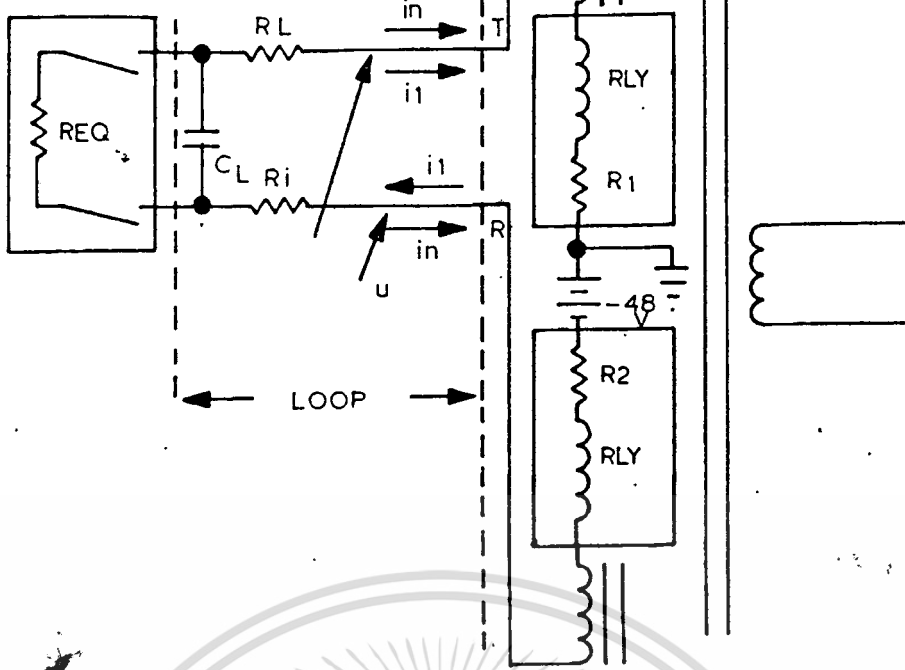

Loop Resistance and Current

FIGURE 7-2

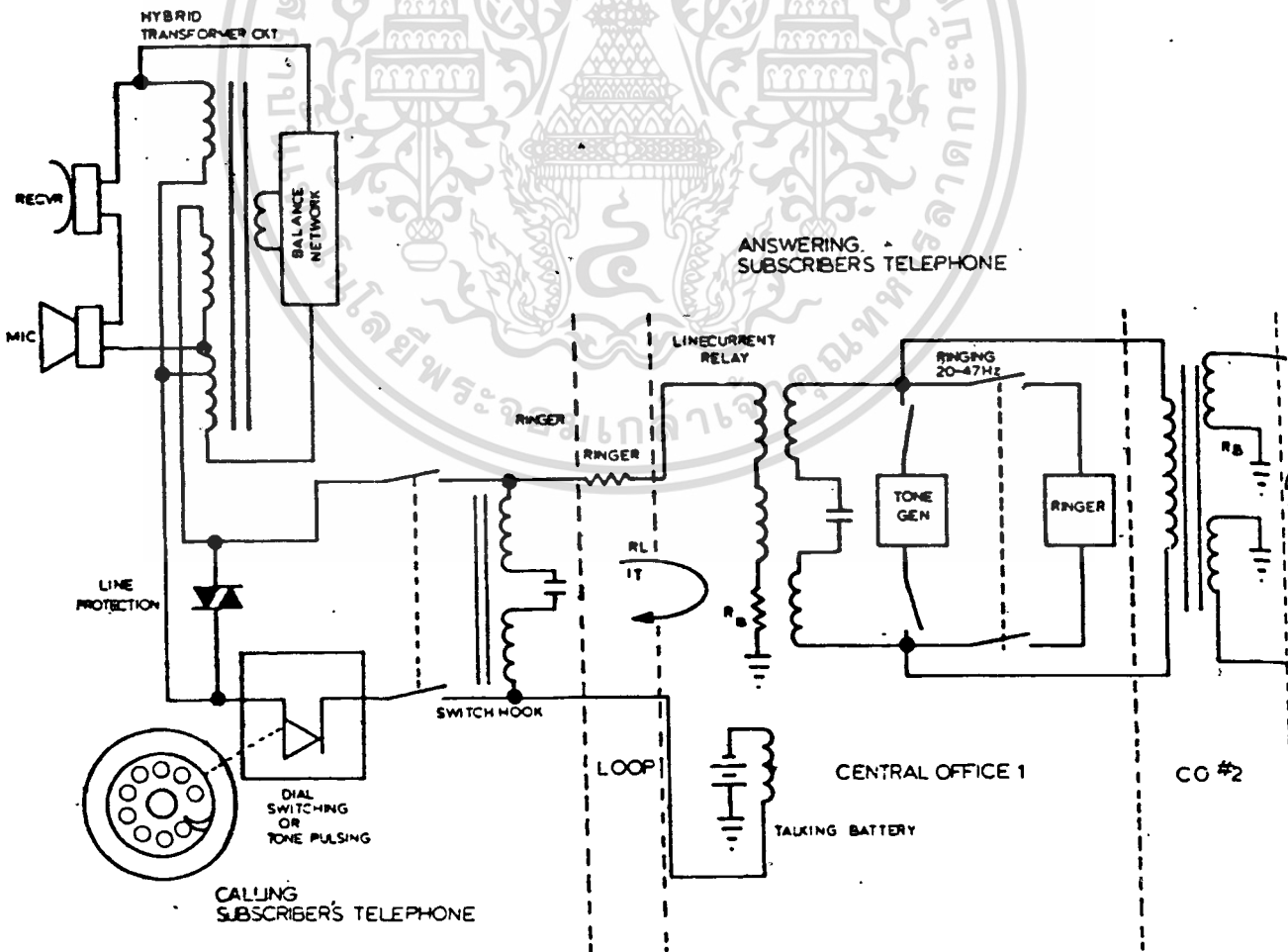

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

Simplified Interface Between Two Subscribers

ไม่ว่ากรณีใดๆ ทั้งสิ้น อีกทั้งหาว่าเป็นเหตุบังเอิญไปขอหา และต้องวางเรื่องถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

ค่าความต้านทานที่ศูนย์ก็ถือว่ามิต่างกับ 400 ค่าความต้านทานนี้จะรวมเข้ากับ 400 ของเครื่องโทรศัพท์ของผู้ให้บริการ แล้วผลลัพธ์ที่ได้จากการเอาไปลบออกจาก ค่า LOOP RESISTANCE รวมจะได้ค่า ความต้านทานของ WIRE LOOP สำหรับ CARBON MICROPHONE ต้องการกระแสที่น้อยที่สุดคือ 23 MA ค่า WIRE LOOP RESISTANCE จะคำนวณได้จาก $RL = 48/0.023 = 2087 - 800$ หรือประมาณ 1300 ohm ในโทรศัพท์อิเล็กทรอนิกส์ ซึ่งค่ากระแสที่ต้องการจะถือว่ามิต่างน้อยมาก DPOF RELAY ที่จะทำให้ LOOP CURRENT มีค่าที่อาจจะมิต่างถึง 10 AM ในบางศูนย์อาจให้ค่า MINIMUM LOOP CURRENT 5 - 25 mA ในการทำงานที่ระดับต่ำอาจใช้ OPTOCOUPERS ในการควบคุมอุปกรณ์กำเนิดสัญญาณ และ SOLID - STATE SWITCHING กระแสที่ต่ำกว่าจะมีความสำคัญเป็นพิเศษ ใน RURAL AREA ซึ่งสายมักจะยาวกว่า 10 - 15 ไมล์ ระดับเสียงต่ำจะทำให้ VOLTAGE DROP ในสายเมื่อรวมกับ ELECTRICAL DISTURBANCE จะทำให้ การติดต่อสื่อสารทำได้ยากมาก ตัวอย่างเช่น โทรศัพท์อิเล็กทรอนิกส์ที่มี LINE - LOSS COMPENSATION - SIGNAL VOLTAGE ที่ขยาย SIGNAL VOLTAGE ออโตเมติก สามารถพิสูจน์ ได้ว่ามีส่วนช่วยได้มาก.

IC VOICE CIRCUIT ถูกนำมาใช้ในโทรศัพท์อิเล็กทรอนิกส์ เพื่อช่วยในการ COMPENSATE แบบนี้

ในกรณีที่สายสั้นก็อาจจะมิต่างอย่างอื่นเกิดขึ้น สมมุติว่า RL มีค่าเท่ากับ 100 LINE CURRENT ก็จะมีเพิ่มขึ้นเป็น $I = 48/900 = 53 \text{ mA}$

การลดค่าความต้านทานของอุปกรณ์ลงอาจทำให้ LOOP CURRENT เพิ่มขึ้นเป็น 100 หรือ 100mA เพื่อที่จะควบคุมค่าตามต้านทานของ SUBSCRIBER LOOP ความยาวของ LOOP ถูก จำกัดอยู่ที่ 3 - 12000 ฟุต อย่างไรก็ตามเนื่องจากโทรศัพท์อิเล็กทรอนิกส์ ต้องการปริมาณ กระแส น้อย ๆ LOOP LENGTH สามารถที่จะยึดออกไปได้ความดังของเสียงโทรศัพท์โดยปกติจะได้เป็นหัว อ่างอิง ระดับสัญญาณหรือ ระดับพลังงานของเครื่อง พลังงานที่มากที่สุดถูกถ่ายทอดไปเมื่อ LOOP RESISTANCE หรือ IMPIDANCE เข้ากันได้พอดีกับ SOURCE ค่าของสายขนาด 22 - GAUGED TWISTED ในสาย เคเบิลที่เป็น TRANSMISSION LINE มีค่า IMPEDANCE (Z) 600 SOURCE และ 600 LOAD จะ MATCH กันอย่างเหมาะสมในการถ่ายทอดพลังงานอย่างมีประสิทธิภาพ ที่ SOURCE, BALANCE CABLE จะกลายเป็น LOAD และพลังงานที่ได้รับจะหาได้จากสมการ $PL = e^2/Z$ เมื่อ PL คือพลังงานระดับสัญญาณที่เกิดขึ้นอย่างฉับพลัน es ถูกระบุเป็น VOLT และ Z เป็นค่า IMPEDANCE ในหน่วย ohm ระดับสัญญาณอาจอยู่ในรูปของค่าเฉลี่ยของ PEAK ระดับพลังงานของสัญญาณมักจะเทียบกับ ระดับพลังงานอ้างอิงบางตัวในโทรศัพท์ ก็เหมือนกับใน AUDIO TRANSMISSION LINE ตัวอย่างนี้จะประกอบไปด้วย พลังงาน 1mw คร่อมบน 600 LOAD จากสมการพลังงาน

$$0.001W = ES^2/600 \text{ เมื่อ } ES = 0.775 \text{ W}$$

027954

เอกสารนี้เป็นเอกสารที่ได้อีกอย่างหนึ่งว่า โดยประมาณ 3/4 ของ VOLT ที่คร่อมบน 600 LOAD

ไม่ว่ากรณีใดก็ตาม สิ่งทั้งห้ามิให้ตัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

จะก่อให้เกิดพลังงาน 1 mw เพราะว่าระดับของสัญญาณมักจะวัดที่ความถี่ของ SINGLE WAVE
พลังงานที่ต่ำกว่าจะอธิบายในรูปของ DECIBEL พลังงานเนื่องจาก LOAD คือ

$$dB = 10 \log_{10} (P1/P2)$$

เมื่อ 1mw ใช้เป็นตัวพลังงานอ้างอิง (P2) สัดส่วน DECIBEL (dB) แบบพิเศษรู้จัก
ว่าคือ 0dbm สามารถที่จะทำให้เกิดขึ้นได้เมื่อ P1 เท่ากับ 1mw ด้วย 0 dbm จะใช้แทน
DECIBELS ที่สูงหรือต่ำกว่า 1mw ที่ใช้อ้างอิง โดยความหมายของสัญลักษณ์นี้ ระดับพลังงานใด ๆ
ไม่ว่าจะมากเท่าหรือน้อยกว่า 0dbm อาจจะมาเปรียบเทียบกับ ระดับพลังงานเมื่อเริ่มต้นได้
ตัวอย่างเช่น เมื่อให้พลังงานเข้าไปในทิศทางใด ๆ ในสายที่ ZERO TRANSMISSION LEVEL,
พลังงานที่จุดนี้จะเรียกว่า OTLP และสัญลักษณ์ก็จะเปลี่ยนไปเป็น dbm0 พลังงานที่ลดลงไป -20
dbm0 หมายความว่า ระดับพลังงานที่จุดนี้ลดลงไป 10 mw เมื่อเทียบกับ OTLP ข้อสังเกต 20
dbm0 = 10 LOG 100/1 แอมป์ริฟายเออร์อาจต้องการ การชดเชยสำหรับระดับพลังงานที่ลดลง

ในการสื่อสารด้วยเสียงผ่านทาง AUDIO TRANSMISSION, มาตรฐานที่ยุงยากมาก ๆ
ได้ถูกกำหนดขึ้น เพื่อวัด VOLCE TO - NOISE LEVEL สายชนิดต่าง ๆ ก็จะมีค่า VOLCE -
TO -NOISE TRANSMISSION ไว้ให้อ้างอิงต่างกัน ตัว REFERENCE ที่ใช้ในการวัดยังมี aBN,
dBRN, dBA, dBRNC และ dbrnc0 ตัว REFERENCE รวบรวมใช้เป็นดัชนี ซึ่งมีค่าอธิบาย พร้อม
ทั้งตัวอย่างสำหรับการใช้ โดยได้รับการอนุมัติจาก RCA SOLID - STATD DIVISION
LINE BALANCE

กระแสที่ไหลผ่าน LOOP ทำให้เกิดสนามหรือ VOLTAGE TO TENTIAL รูปที่ 7 - 2
แสดงให้เห็นกระแสในแต่ละสาย กระแสที่ไหลผ่านคู่ขนาดอาจจะออกนอก PHASE หรืออยู่ใน
PHASE ก็ได้ สำหรับสัญญาณเสียง และ BALANCE LINE กระแสในแต่ละสายจะมีค่าเท่ากัน และ
ทิศทางกระแสจะเป็น 180 ออกนอก PHASE การไหลของกระแส เป็นผลจาก DIFFERENTIAL
POTENTIAL ที่ให้เข้าไปกับสาย 2 สาย โดยทำให้เกิดขึ้นได้จากการที่ CARBON MICROPHONE
จ่ายกระแสไปผ่าน HYBRID TRANSFORMER สัญญาณ AUDIO จากศูนย์ทำให้เกิดการไหลของกระแส
OUT -- OF - PHASE ที่เหมือนกัน ถึงแม้ว่า POTENTIAL ของสัญญาณเสียง และกระแสจะ
ต่างกัน แต่การเหนี่ยวนำจากภายนอกก็จะทำให้กระแสอยู่ใน PHASE จากความจริงที่ว่านี้ สาย
ต่าง ๆ ควรที่จะทำให้เกิดสมดุลย์เมื่อเทียบกับ GROUND ในเรื่องของ RESISTANCE,
INDUCTANCE และ CAPAEITANCE ถ้าเกิดการไม่ BALANCE ในสายต่าง ๆ จะทำให้เกิด
PHASE SHIFT และสัญญาณ DELAY POTENTIAL ภายนอกอื่น ๆ เช่น NOISE และสัญญาณจาก
LOOP ที่อยู่ใกล้ ๆ ก็ทำให้เกิดการเหนี่ยวนำกระแสได้ด้วย เนื่องจากสนามภายนอกคร่อมสายทั้งคู่
กระแสที่อยู่ใน PHASE ก็จะถูกเหนี่ยวนำ ในสายทั้งคู่ กระแสที่เกิดจากการเหนี่ยวนำนี้จะไม่ทำให้เกิด
DIFEGRTIAL SIGNAL แต่จะเกิด LONGTUDINAL SIGNAL ขึ้นแทน COMMONN - MODE
SIGNAL นี้จะไม่เกิดขึ้นในระบบที่ BALANCE รูป 7 - 3 แสดงให้เห็นถึงสายที่ได้รับ
DIFFERENTIAL และ LOGITUDINAL จากตัวกำเนิดกระแสสองตัว

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น เมื่ออนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆทั้งสิ้น อีกทั้งห้ามมิให้ดัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

สัดส่วนของ DIFFERENTIAL - SIGNAL CURRENT กับ COMMON - MODE CURRENT (IDIFF/ICM) ใช้อธิบาย COMMON - MODE REJECTION RATION (CMRR)

$$CMRR = 20 \text{ LOG } 10 \text{ IDIFF/ICM}$$

VOLTAGE OUTPUT " EO " สามารถเอามาใช้คำนวณ ค่า CMRR ได้ด้วย

$$CMRR = 29 \text{ LOG } 10 \text{ EDIFF/Ecm}$$

การคำนวณนี้จะบอกถึงความสามารถของระบบที่จะทำให้มีการสูญเสียที่น้อยที่สุดเมื่อมี DIFFERENTIAL SIGNAL ไหลผ่าน ในขณะที่เดียวกับที่ COMMON - MODE หรือ LONGITUDINAL SIGNAL มีน้อย ดังจะเห็นได้จากเมื่อทำการศึกษาที่ศูนย์ในเรื่องของ LINE INTERFACE โดยอ้างถึง SLIC LONGITUDINAL SIGNAL จะลดลง 40 - 50 dB เมื่อเกิดความไม่สมดุลย์ในสายอื่น เนื่องมาจากมีอุปกรณ์ใดมาต่ออยู่ อาจเป็นสาเหตุที่ทำให้ LONGITUDINAL SIGNAL VOLTAGE เพิ่มขึ้น สัญญาณที่เกิดจากการเหนี่ยวนำเหล่านี้ทำให้เกิดระดับของสัญญาณรบกวน NOISE เพิ่มขึ้น ด้วยเหตุนี้ทำให้ SIGNAL - TO - NOISE RATIO ลดลง

SIGNALING ON THE SUBSCRIBER'S LOOPS

ชนิดของการส่งสัญญาณเมื่ออยู่ 3 ชนิด ซึ่งเป็น

- SUPERVISION
- ADDRESSING
- CUSTOMER ALERTING

ทั้งสามชนิดนี้ใช้ BATTERY 48 V แบบธรรมดาซึ่งใช้ร่วมกับ VOICE SIGNAL

ขั้วบวกของแบตเตอรี่ต่อเข้ากับ RING BRIDGE RECTIFIERS ในที่ RECEIVER STATION เพื่อให้ปรับ โพลาร์ลิตี้ ของ VOLTAGE เมื่อจำเป็น แบตเตอรี่ ซึ่งอาจจะประกอบไปด้วยสายจากกำลังไฟ และ แบตเตอรี่ฉุกเฉินไว้ให้กับ VOICE TRANSMISSION, DIAL TONE, DIALING OF LINE SWITCHES, RINGING AND OFF HOOK ALERTS SUPERVISION จะเกี่ยวข้องกับค่าความต้านทานของ LOOP ความต้านทานของอุปกรณ์, ค่าที่เสียไป และ VOLTAGE SUPPLY ที่ต้องการ เพื่อเป็นการทำให้แน่ใจถึงการทำอย่างถูกต้องค่า LOOP RESISTANCE จะทำให้ความถี่ที่ 1.3 K หรือน้อยกว่า

ADDRESS SIGNACING เกิดขึ้นจาก DIAL PULSE หรือ TOUCH - TONE DIALING DIAL PULSER เป็น MAK - BREAK CONTACT ของ MECHANICAL SWITCH 1 หรือ อุปกรณ์ SOLID - STATE TOUCH - TONE DIALER ส่ง DIAL TONE ซึ่งแทนตัวเลข 12 ตัว TONE ที่มี 2 ผ่านควาถี่ คือ 697 - 941hz และ 1.21 - 1.48 khz ถูกส่งไปยัง RECEIVER แบบ DUAL - TONE MULTI FREQUENCY (DTMF) TONE พวกที่มีความถี่ต่ำ ถูกส่งผ่านที่ระดับ 6 dBm และพวกความถี่สูงถูกส่งผ่านที่ - 4dBm เนื่องจาก TONE ถูกส่งผ่านในย่าน VOICE NETWORK เหมือนกับข้อมูล DIGITAL ก็ได้วิธีการหมุนหมายเลข และกระแสที่เกิดจากการหมุนจะมีรายละเอียดที่มากกว่าอยู่ในการทดลองอื่นๆ ซึ่งรวมถึง การหมุนหมายเลขแบบ DTMF ด้วยจะโยชน์ด้านการค้า

CUSTOMER ALERTING รวมเอา RINGING, DIAL TONE, การรับสัญญาณ ยกหูโทร
คัท OFF HOOK SIGNAL และสัญญาณไม่ว่าง RINGING ที่เกิดขึ้นที่ศูนย์เป็นการรวมกันของ DC
และ AC VOLTAGE AC ที่อัตรา 20 Hz ถูกส่งไปยังผู้ใช้เพื่อออกให้ทราบว่าสามารถติดต่อได้
เสียงเรียกจะดังอยู่ 2 วินาที และเวียนไป 4 วินาที ในระบบ PBX อาจใช้ 1 วินาที ดัง 3 วินาที
ที่เว้น

RECEIVER OFF - HOOK (ROH) ALERT เป็นสัญญาณซึ่งประกอบไปด้วยการรวมกัน
ของความถี่ 1.4 kHz, 2.06kHz, 2.46kHz และ 2.6 kHz เสียงดังนี้ถูกออกแบบมาเพื่อดึง
ความสนใจของผู้ที่อยู่ใกล้ ๆ จะดังติดต่อกันเป็นเวลา 50 วินาที หรือ อาจถูกยับยั้งด้วยอัตรา 5
ครั้งต่อวินาที

ยังมีการส่งสัญญาณแบบต่าง ๆ อีกมากทั้งที่อยู่ในและนอกย่านสัญญาณเสียง การส่งสัญญาณ
ในย่านนี้อาจถูกเปลี่ยนให้เป็นสัญญาณ DIGITAL และส่งผ่านด้วย PCM - VOICE DATA ภายใน 1 เฟรมของ 24 - SLOT FRAME

อุปกรณ์ SLIC ที่ต่ออยู่กับ SUBSCRIBER'S LINE CARD ใน LOOP ประกอบไปด้วย
หน้าที่การควบคุมที่ใช้ในการกำหนดหลายอย่าง เช่น ความคุมกระแสของ LOOP (SUPERVISION),
OFF - HOOK STATUS, RINGING STATUS, RING - TRIP CONTROL IDLE - CURRENT
SHUTDOWN หน้าที่การทำงานเหล่านี้ ก่อนหน้านี้ใช้ RELAY แบบกึ่งอิเล็กทรอนิกส์ แต่ในปัจจุบันใช้
อุปกรณ์ SOLID - STATE ใน SLIC CARD ความคุม
สรุป

1. ผู้ใช้ติดต่อกับศูนย์ด้วยคู่สายขนาด 22 ถึง 26 GAGE
2. ลวดเส้นที่มีค่าเป็นลบมากที่สุดจะถือว่าเป็น RING (R) เส้นที่เป็นบวกถือว่าเป็น TIP (T)
3. คู่สายจะเรียกว่า LOOP ด้วยจะทำให้ BALANCE ด้วยการเทียบกับ EARTH-GROUND
4. สัญญาณเสียงเกิดขึ้นจากความแตกต่างของ VOLTAGE ใน LOOP
5. สัญญาณรบกวน (NOISE) และ POWER - PICKUP ก่อให้เกิด COMMON - MODE SIGNAL ที่เรียกว่า LONGITUDINAL VOLTAGE
6. LOOP ก็ถือว่าเป็น INTERFACE แบบ LINE - SIDE ค่ากระแสใน LOOP มีค่าประมาณ .20mA
7. การทำให้เกิดสัญญาณประกอบด้วย SUPERVISION, ADDRESSING และ CUSTOMER ADDRESSING.


REVIEW QUESTIONS

1. The subscriber's loop is generally a twisted pair of number _____ gage wires.
2. The tip has a potential which is more _____ than that of the _____.
3. The -48 V talking battery is connected to the _____ line, which may also be marked L2.
4. The twisted wire pair is _____ with respect to a ground.
5. In a balanced loop, the talking current is _____ and _____ in each line.
6. A longitudinal voltage produces a current in each line which is _____.
7. The ratio of the talking signal to the longitudinal signal is a measure of the _____.
8. A carbon-button microphone requires a current of _____ mA.
9. The K-500 model telephone set has an equivalent impedance of _____ ohms.
10. The subscriber's loop is generally considered to have a _____ ohm resistance.
11. When on-hook, the same dc current flows in the loop as _____.
12. The subscriber's loop is also referred to as a _____.
13. BORSCHT includes:
1 _____, 2 _____, 3 _____,
4 _____, 5 _____, 6 _____,
7 _____.
14. SLIC refers to the _____ which is located in the _____.
15. In electronic telephones, the loop current is likely to be higher than 50 mA. True/False? _____
16. The level of signals on the line is generally referenced to _____ on a _____ ohm line.
17. The unit for power measurements on the line is in _____.
18. OTLP means _____.
19. In ringing, the signal is on for _____ seconds and off for _____ seconds.
20. The three main types of signaling are _____

_____.
21. Dialing is carried out by two methods _____ or _____.
22. In touch-tone, _____ ranges of frequencies are transmitted.
23. The standard dialing rate is _____ pulses per second.
24. The ringer has a frequency rate of _____ Hz.
25. The receiver off-hook alert consists of _____ different frequencies.

ANSWERS TO REVIEW QUESTIONS

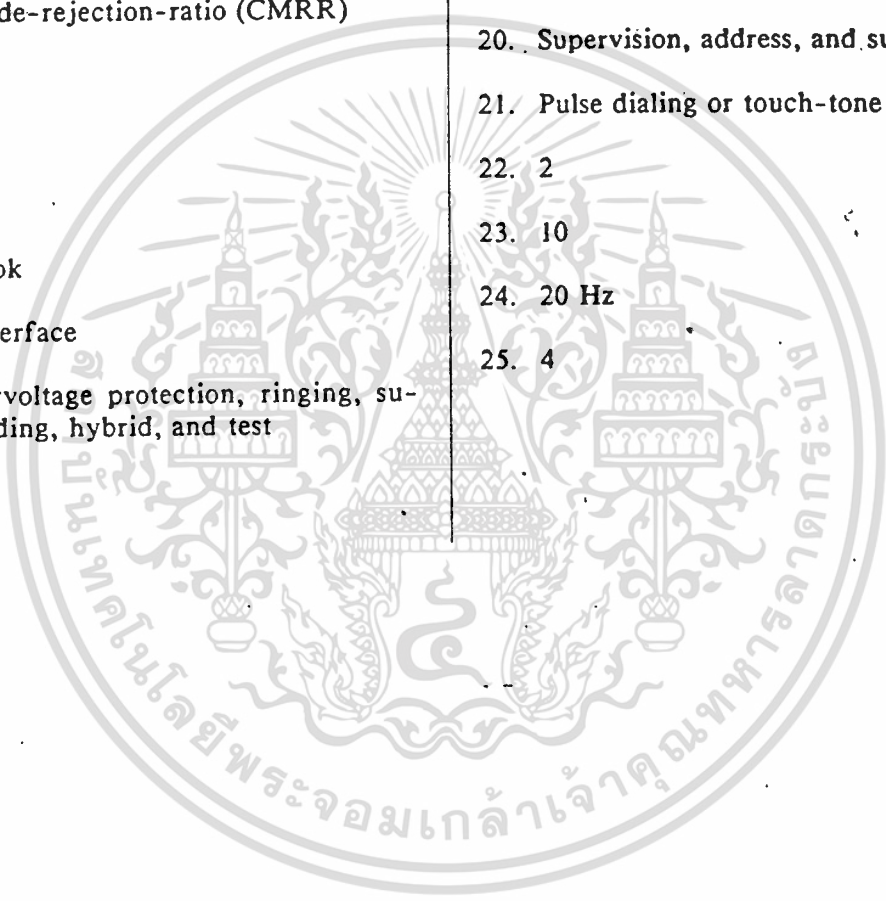1. 22-26
2. Positive, ring
3. Ring
4. Balanced
5. Equal and opposite
6. Inphase
7. Common-mode-rejection-ratio (CMRR)
8. 23
9. 400
10. 1.3 k
11. When off hook
12. Line-side interface
13. Battery, overvoltage protection, ringing, supervision, coding, hybrid, and test
14. Subscriber's loop interface circuit in the central office
15. True
16. 1 mW, 600
17. dB's
18. Zero transmission-level point
19. 2 seconds, 4 seconds
20. Supervision, address, and subscriber alert
21. Pulse dialing or touch-tone
22. 2
23. 10
24. 20 Hz
25. 4




TONE DIALING (DTMF) AND PULSE DIALERS

จากรูป 8.1 แสดงให้เห็นโครงร่างแบบง่าย ๆ ของการเชื่อมต่อกันระหว่าง MIC กับหูฟัง ซึ่งจะให้ กระแส Dc - 45V ซึ่งจะไหลผ่าน CARBON MIC แรงดันที่เกิดจากเสียงบนแผ่น DIAPHRAM จะกดผงถ่านซึ่งทำให้ ค.ต.ท แรง MIC ลดลง และเพิ่ม VOICE CURRENT การเปลี่ยนแปลงแรงกระแสจะถูกล่งผ่านคู่สาย, ทางด้านผู้รับ พลังงานที่ผ่านหูฟังจะถูกเปลี่ยนจาก พลังงานไฟฟ้า เป็นพลังงานเสียง

มี SW อยู่ 3 ตัว ที่ใช้ตั้ง SI จะเป็น Dialing SW หรือ Pulser S2 และ S3 เป็น cardle SW, เมื่อหูโทรศัพท์วางอยู่บนแคร่ S2 S3 จะถูกเปิดอยู่ ซึ่งเรียกว่า " ON HOOK " และเมื่อ S2 S3 ถูกปิดวงจรจะเรียกว่า " OFF HOOK "


เมื่อหูโทรศัพท์ถูกยกขึ้น กระแส Loop ก็เพิ่มขึ้นอย่างทันทีทันใด ซึ่งจะทำให้ RELAY ที่อยู่ใน Central Exchange ตอวงจรซึ่งหมายความว่าคู่สายพร้อมที่จะใช้งานได้ โดยมีสัญญาณ Dialer Tone กลับมายังผู้ใช้

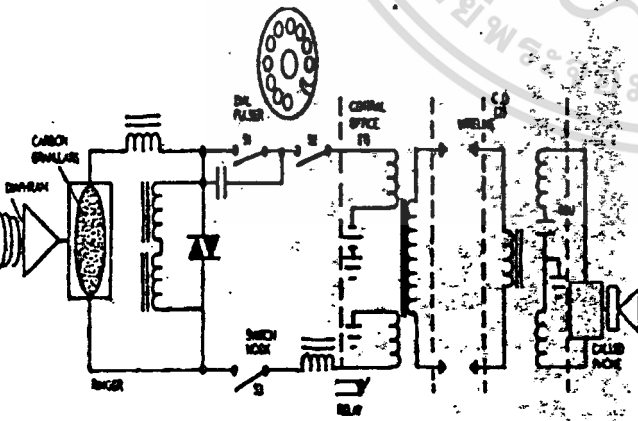การเรียกสายประกอบไปด้วย การเปิดและการปิด Pulsing SW หรือ คือ การทำให้เกิด DIAL TONE ซึ่งปัจจุบันใช้ Dial - Pulser SW.




Basic Circuit Between Subscriber, Central Office, and a Second Subscriber

FIGURE 8-1

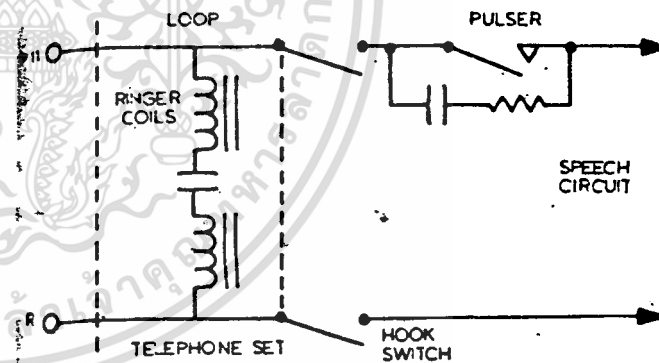

The Ringer Circuit of the Telephone

FIGURE 8-3

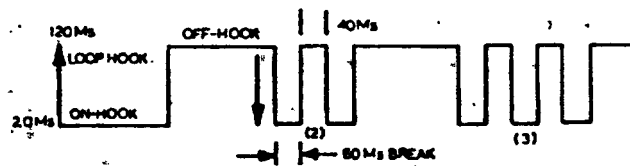

Make-Break Periods for Dialing

FIGURE 8-2

PULSE DIALER

รูปที่ 3.4 แสดงให้เห็นวงจรของ pulse dialer รูปที่ 8.5 แสดงถึงการต่อวงจร DIAL-TONE MULTI FREQUENCY เข้ากับโทรศัพท์

TRANSISTORS VI4, VT5 ต่อกับวงจร SPEECH CIRCUIT เมื่อ VT5 CUT OFF, IC 5098 เป็น LOGIC FUNCTION ซึ่งจะรับข้อมูลจาก KEY PAD (3 COLUMN, 4 LOW) แล้วเปลี่ยนเป็น SERIES PULSE ภายในตัวสามารถเก็บตัวเลขได้ 17 ตัว, สามารถ REDIAL หมายเลขสุดท้าย, มี 2 OUTPUT คือ.


1. DIGIT PULSING
2. MUTING THE RECEIVER

คุณสมบัติ

ทำงานที่ 1.7 V กินกระแส 150 MA, C1 จะ CHARGE ประจุเมื่อโทรศัพท์วางอยู่บนเครื่อง (ON HOOL) ซึ่ง Voltage นี้ จะเป็นตัวรักษาข้อมูลใน MEMORY


การทำงานของภาค PULSE DIALER

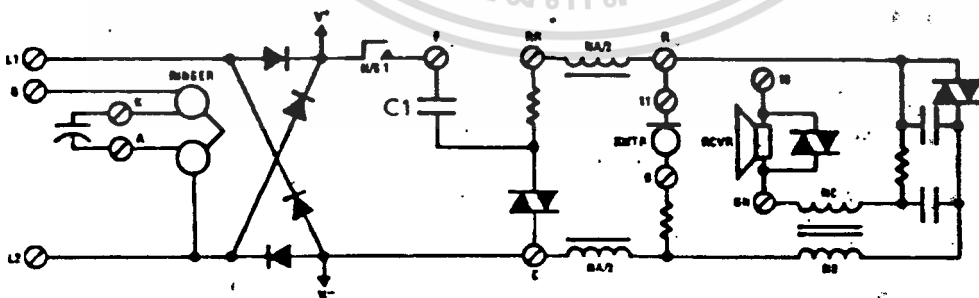เมื่อเรายกหูโทรศัพท์จะมี สัญญาณ ความถี่ 500 HZ SCAN ที่ KEY PAD เมื่อมีการกด KEY ก็จะถูกบันทึกเก็บไว้ในสวิตช์ MEMORY พร้อมทั้งให้ OUT PUT เป็น SERIES PULSE ออกไปจำกัดแค่ 17 ตัว ส่วนการ REDIAL ก็โดยการกดปุ่ม เครื่องหมาย * O/P ก็จะทำให้ชุดตัวเลขชุดสุดท้ายสุด




Basic Wiring of Subscriber Telephone Circuit

FIGURE 8-4

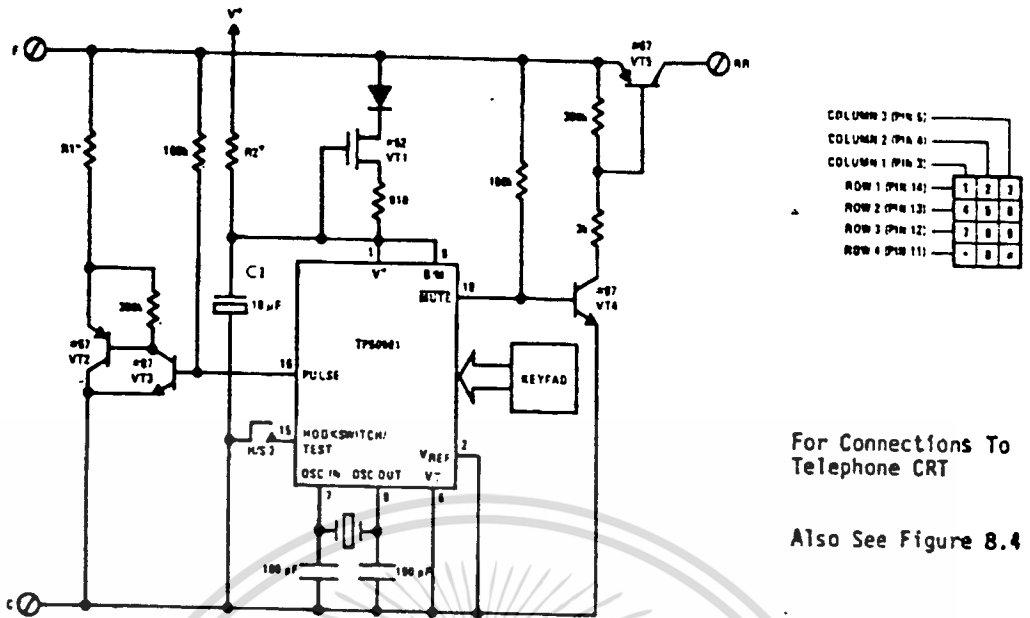

Pulse Dialer Buttons - TP5098
 (Circuits courtesy of National Semiconductor Corp.)

FIGURE 8-5

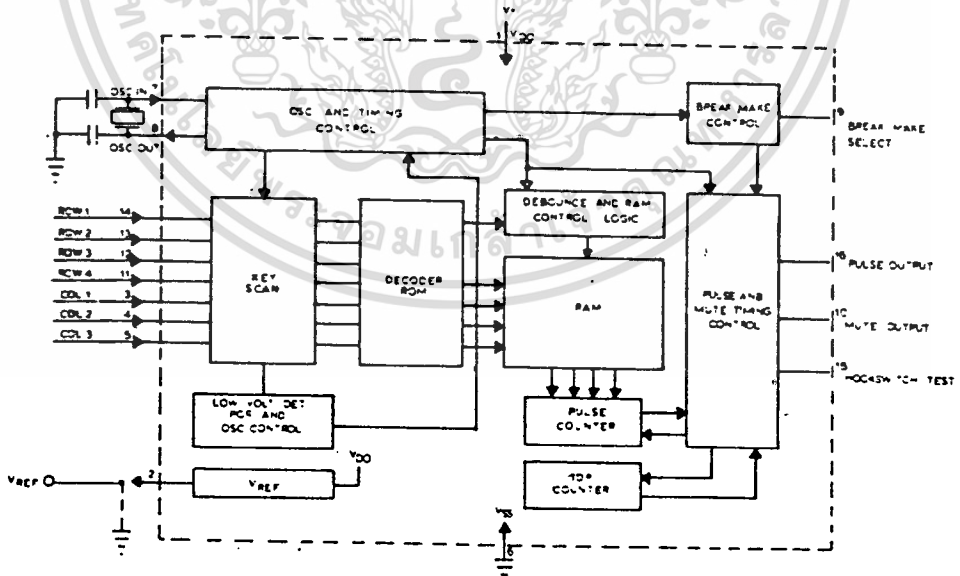


Block Diagram, TP50981 Pulse Dialer

FIGURE 8-6


เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

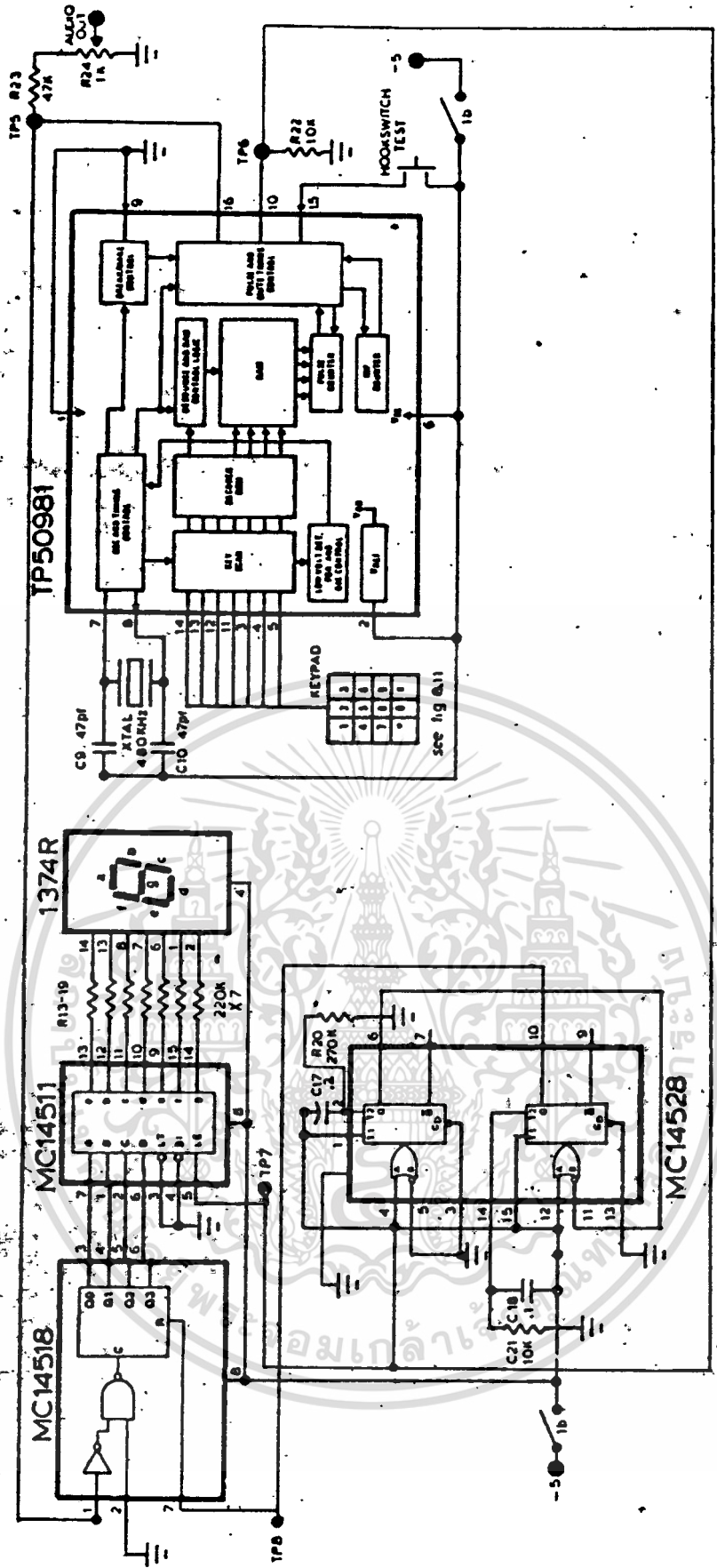ไม่ว่ากรณีใดๆทั้งสิ้น อีกทั้งห้ามมิให้ตัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้



Pulse-Dialer Experimental Circuit

FIGURE 8-12

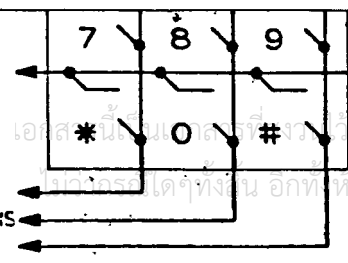

Keypad Wiring

FIGURE 8-7

Tones by Rows and Columns

Row	Tone	Column	Frequency
1	697 Hz	1	1200
2	770	2	1300
3	852	3	1400
4	941	4	1500

Laboratory Experimentation

TEST AND MEASUREMENTS

In the laboratory study, touch-tone calling and dial-pulser circuits will be investigated. In the first experiment, both dual and single tones are produced. The focus of the second IC experiment is on a memory-redial feature.

MATERIALS REQUIRED

SIP397-2 and 300 PSB or 300 B.

MISCELLANEOUS

Keypad (S390 KP)

EXPERIMENTAL PROCEDURES

DUAL-TONE MULTIFREQUENCY DIALER:

1. A dual-tone multi-frequency IC (5089) is evaluated first. Power up a prewired circuit 397-2 section P, and refer to Figure 8.11. The circuit can operate on 3-10V. Since the central office supplies -48 V, the IC is operated on the negative supply of -5 V to -10 V. Close the voltage supply switch 3b.
2. The IC produces both dual and single tones. When switch 2b is closed, both types of tones are available at TP2. Close 2b.

FUNCTIONAL DESCRIPTION

With no key inputs to the device, the oscillator is inhibited, the output transistor is pulled OFF, and the current consumption of the device is reduced to a minimum. To insure that no modulation of the line occurs when tones are not being generated, key closures are sensed statically. Any key closure will activate the MUTE output, start the oscillator, and set the high-group and low-group programmable counters to the appropriate divide ratio. These counters sequence two ratioed-capacitor D-A converters through a series of 28 steps of equal duration per sine wave cycle.

The values of the two groups of tones are added together by a mixer amplifier, with pre-emphasis applied to the tones of the high group. The resultant output is a negative-positive-negative (NPN) emitter follower, requiring the addition of an external load resistor to Vss. This resistor facilitates adjustment of the signal current flowing from Vdd through the output transistor.

Connect an oscilloscope to TP2 and a counter to TP3; to this point also connect a second oscilloscope channel. The 100 k Ω resistor (R27) and 560 pfd capacitor (C12) form a filter which permits the counter to function properly. The audio output may also be connected to an audio amplifier and speaker. A volume control (R24), is shown in section O, Pulse Dialer Circuit.

3. By pressing two buttons at a time: 1 and 2; 2 and 3; or 1 and 3, a single-row tone is produced. Repeat this procedure for rows 2, 3, and 4. Complete the chart.

TONE LOW GROUP	ENCODER OUTPUT	MEASURED OUTPUT
Row 1	697	
2	770	
3	852	
4	941	

NOTE: Measured values may differ from encoder output.

4. Test the columns by repeating this procedure; press two buttons at a time.

TONE HIGH GROUP	ENCODER OUTPUT	MEASURED OUTPUT
Col. 1	1209	
2	1336	
3	1477	
4 (optional)	1633	


NOTE: Measured values may differ from encoder output.

5. At TP2 observe the dual-tone wave shape when 1, 2, 3 and 4, etc. are depressed one at a time. Is a staircase approximation of a sine wave present? _____

6. Check the frequency of the clock at TP1 (Note: TP1 is located to the right of the 3.579 crystal and may not be labelled), using a low-capacity probe to prevent interference. Clock Frequency = _____ when key is depressed.
7. When a tone key is depressed, the IC has the capability of turning on another circuit, such as a transmitter or a recorder. Measure the voltages at TP4 when a key is not depressed and again, when it is depressed. Record both

voltages. Key open _____ V. Key closed _____ V. Does the keyboard's active control shift levels with all keys? _____

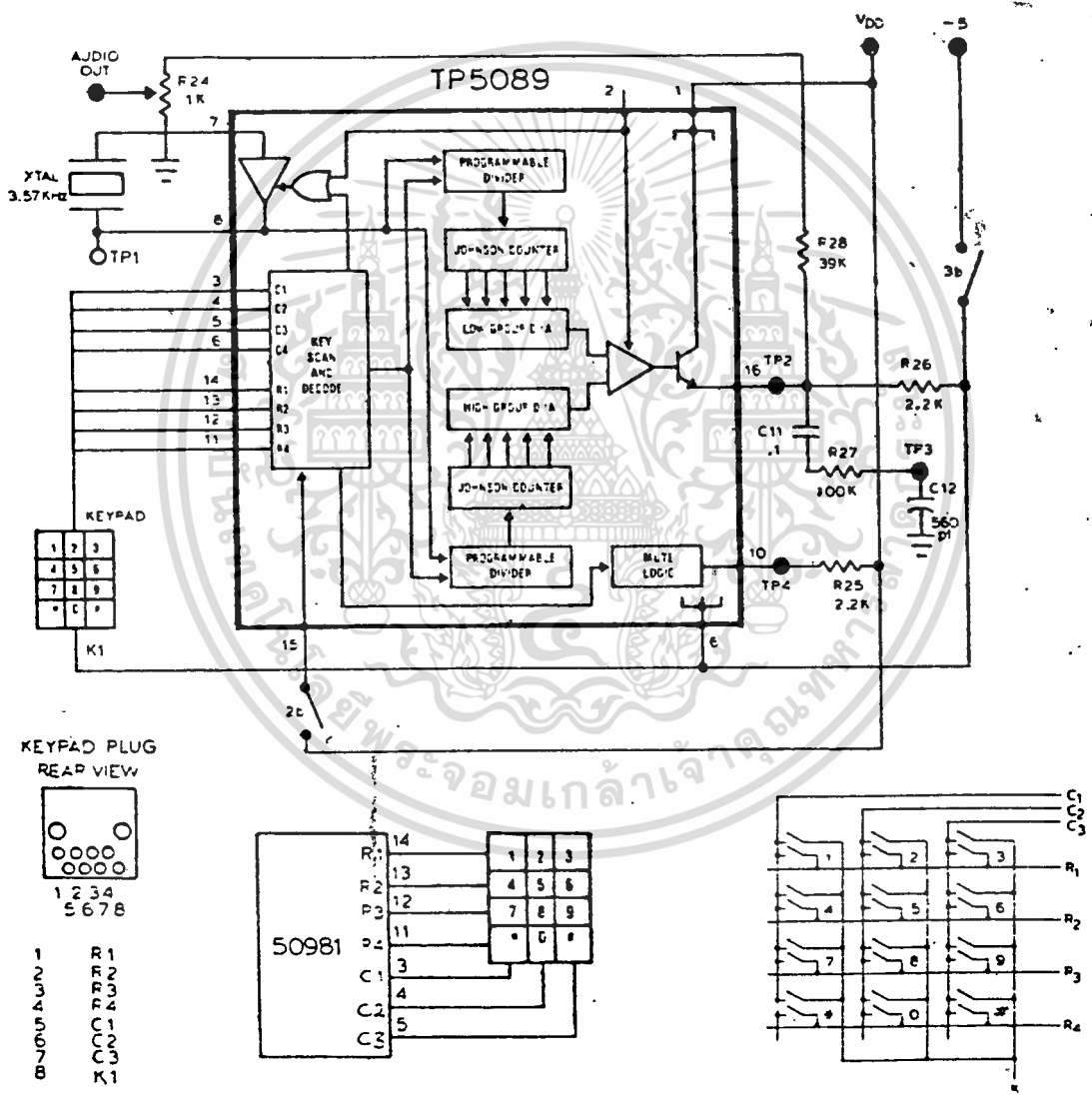8. Distortion measurements are not included; however, the student may be interested in measuring the third harmonics content, a measurement which may be accomplished using almost any distortion meter. Reference should be made to the technical data supplied in the Appendix.



Functional DTMF Dialer (Encoder)

FIGURE 8-11

REVIEW QUESTIONS

Alan B. Strowger invented the _____.

The carbon-microphone mouthpiece was invented by _____.

The current for operating the subscriber set comes from the _____.

The dc voltage for operation of a subscriber set is _____ V.

Off hook means _____.

The mechanical rotary dial produces _____ for each number.

The mechanical dial activates its contacts during its _____ motion.

There are _____ wires between the subscriber set and the central office.

Central offices can handle _____ subscribers with only a 4-number assignment.

The dial speed of the rotary dial, is _____ pulses per second.

11. In a push-button tone system, 7 tones can produce _____ digits.

12. Dial pulsing can be transmitted either in series or parallel with the _____.

13. Touch-tone can also be transmitted either in series or parallel with the _____.

14. During the time that tone pulses are being transmitted, the receiver circuit is _____.

15. Varistors are used in the subscriber set to _____.

16. The word RAM means _____.

17. The electret microphone operates on a _____ changing principle.

18. Cordless telephone sets have a range of _____ to _____ feet.

19. Standard memory on a DTMF IC can store up to _____ digits.

20. The term 2 of 7 means _____.

EXPERIMENTAL ANSWERS

1. Procedural

2. Procedural

Row	TONE	ENCODER OUTPUT	MEASURED OUTPUT
1		701.3	763 Hz
2		771.4	833 Hz
3		857.2	909 Hz
4		935.1	1 kHz

High Group

Column			
1	1215.9	1.32 kHz	
2	133.7	1.43 kHz	
3	1471.9	1.56 kHz	
(optional) 4	1645.0	1.65 kHz	

5. Yes

6. Clock frequency is 3.579 MHz.

7. Key open, -2.4 V; Key closed, -6.4 V; Yes

8. Procedural

9. Procedural

10. Observation

11. Observation

12. Pulse duration approx. 40 ms.

13. Procedural

14. 0 V, -5 V (supply)

15. "On", 42 ms; "Off," 64 ms

16. Observations: TP7 for the number 5, 5 seconds; TP8, 200 microseconds.

ANSWERS TO REVIEW QUESTIONS

1. Rotary dial and central station switching system.

2. Thomas A. Edison

3. Central office

4. 48 V

5. The handset is out of its cradle :

6. Digital pulses

7. Return

8. 2

9. 10,000

10. 10

11. 12

12. Voice circuit

13. Voice circuit

14. Muted

15. Absorb voltage spikes

16. Random-access memory

17. Capacitive

18. 50-700

19. 17


20. Two tones out of 7 possibilities are produced when any 1 key is pressed.

THE ELECTRONIC RINGER

ทุกวันนี้ ELECTRONIC RINGERS อาจ เป็น O S C ตัวหนึ่งซึ่งเป็น TRANSFORMER COUPLED ตัวเล็ก ๆ หรือลำโพงขนาด 2 นิ้ว ที่ผ่านความถี่ต่ำ ๆ 300 - 500 HZ ลำโพงจะมีประสิทธิภาพ มากกว่า CERAMIC และ CRYSTAL DRIVERS แต่ถ้าเกิน 1.5 KHz CERAMIC หรือ CRYSTAL จะดีกว่า


รูปที่ 9.1 แสดง IC ของ TEXAS INSTRUMENTS

Figure 9-1 shows the use of an IC from Texas Instruments.

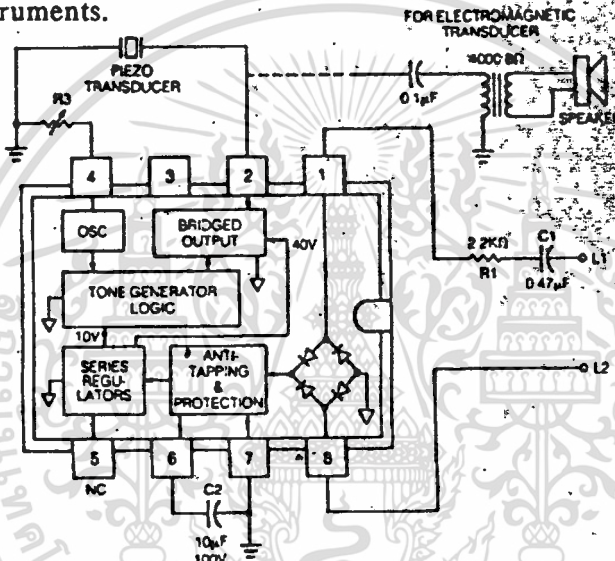

Ring Detector Driver-Speaker Output (TCM 1506A)

FIGURE 9-1

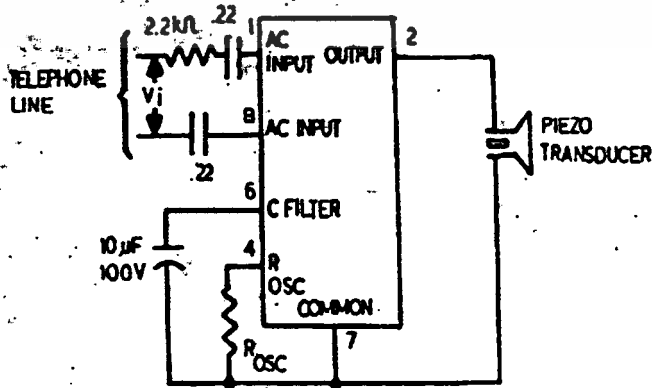


Ring Detector Using a Piezoelectric Transducer

FIGURE 9-2

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเฉพาะเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า
ไม่ว่ากรณีใดๆทั้งสิ้น อีกทั้งห้ามมิให้ตัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

VATAGE (40 - 150 Vac) ถูก RECTIFIED ด้วย FULL - WAVE BRIDGE และมี DIODE ภายในเพื่อป้องกัน อันตรายจากฟ้าผ่า และมีวงจร ANTI - TAPPING เพื่อกำจัด PULSE ที่ไม่สมบรูณ์ ที่เกิดจากการหมุดโทรศัพท์, ความถี่ ของ O/P จะปรับได้ ตั้งแต่ 450 Hz ถึง 1 KHZ (ถ้าเป็น เบอร์ TCM 1501 จะปรับตั้งแต่ 1.8 - 4 khz)

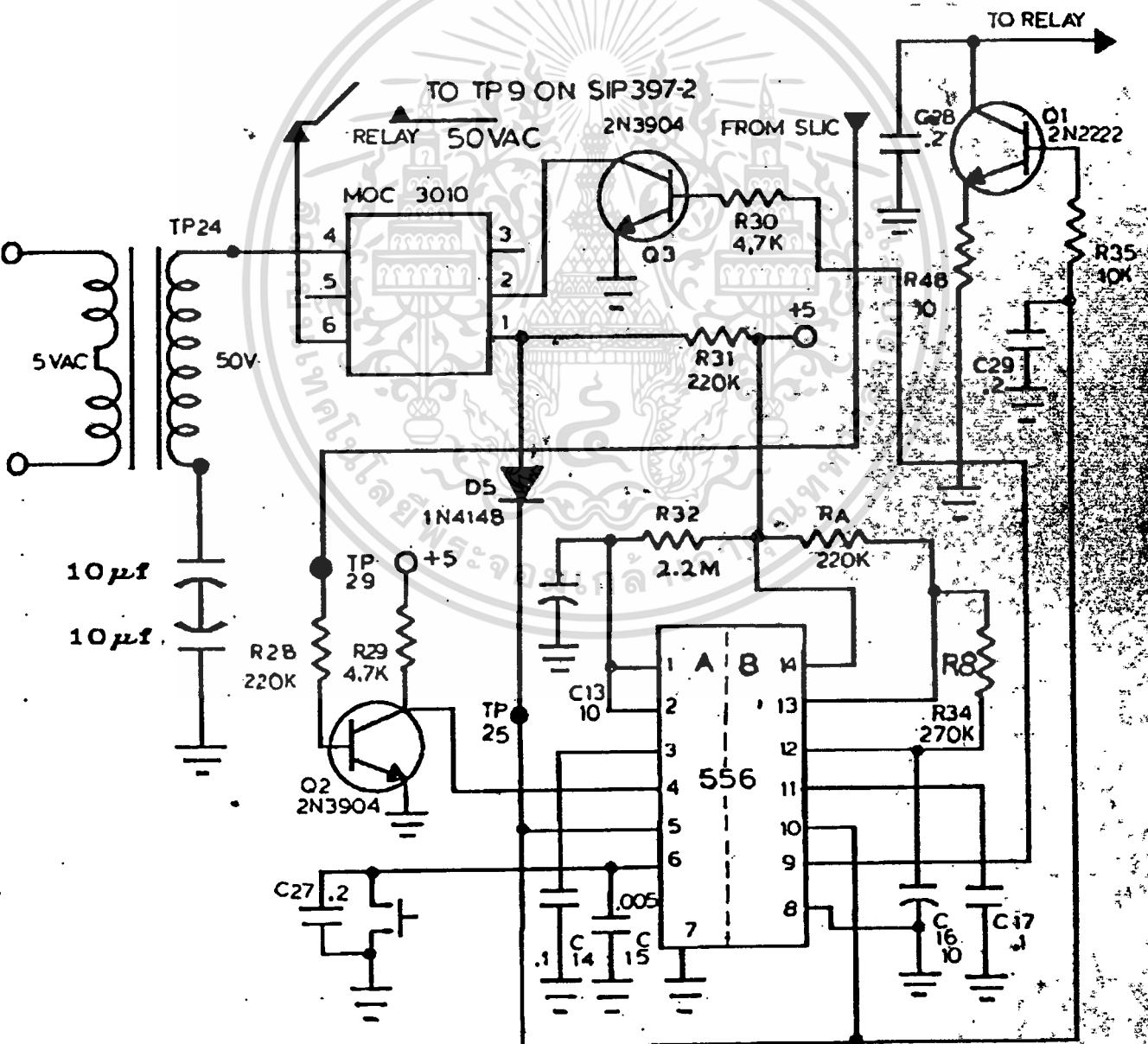แม้ว่าระดับของ VOLTAGE จะเปลี่ยนไป แต่ ความดังของเสียงจะคงที่ ตลอด, ต้องใช้ VATAGE 40 V เป็นอย่างน้อยในการป้องกัน LOW VOLTAGE ที่ทำให้เกิดเสียงรบกวนและ IC RINGER นี้ จะมี I/P IMPEDANCE ประมาณ 100 K หรือมากกว่าและ IC นี้จะไม่เป็นตัว LOAD เพราะว่ามี RC เป็นตัวจำกัด กระแสให้อยู่ภายใน 8 MA



เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

Ringer-Generator Experimental Circuit

RINGER GENERATOR

RINGER จะทำงานได้โดย AC VOLTAGE ที่ส่งมาจาก CENTRAL OFFICE ซึ่ง VOLTAGE นี้ จะเปลี่ยนแปลงได้ในช่วง 50 - 150 V ขึ้นอยู่กับความยาวของ LOOP วงจร RELAYS จะทำให้เกิด RINGER VOLTAGE ใน LOOP สายหนึ่งจะมีสภาพคล้าย GND ส่วนอีกข้างหนึ่ง (RING) จะได้รับ AC POTENTIAL.


RINGER GENERATOR จะประกอบด้วย

1. แหล่งจ่าย AC
2. TIMER ที่มี และเปิด 2 วินาที ปิด 4 วินาที หรือ เปิด 1 ปิด 3
3. DURATIMER
4. LOOP - CURRENT RELAY
5. LOOP - CURRENT SUPERVISOR SENSE VOLTAGE


วงจร RINGER GENERATOR ในรูป 9.4 สามารถอธิบายได้ดังนี้

เมื่อกด RINGER SW จะทำให้เกิดสัญญาณ ความคุม RINGER GEN ในส่วน A, IC556 เป็น วงจร MONOSTABLE ซึ่งให้คาบเวลาที่ 10 - 20 วินาที โดยใช้ $R = 2.2\text{ M}$ และ $C = 10\text{ MF}$, PULSE ของ O/P สามารถวัดได้ที่ TP 25 ซึ่งใช้เป็น TRIGGER " ON " PIN 10 เป็น RESET ในวงจร ASTABLE ในส่วน B, เมื่อ PIN 5 เป็น HIGH วงจร ASTABLE จะ ถูก RESET, ครบของการ ON - OFF จะถูกกำหนดโดย อัตราส่วนของ RA กับ RB ($R\ 34$) และ $T = 1.44 / (RA + 2RB) C17$

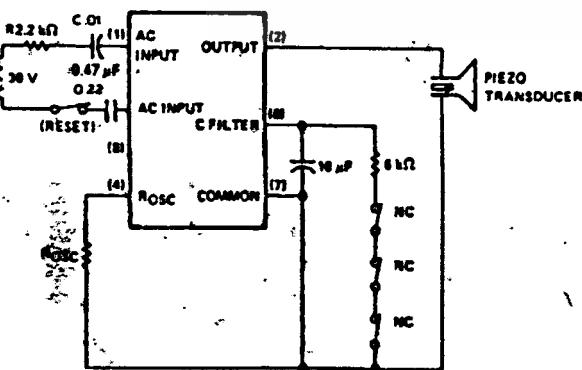เมื่อวงจร ASTABLE เปิด จะเกิด PULSE ไปกระตุ้น TRANSISTOR DRIVER RELAY ($Q1$) ซึ่งเป็นตัวต่อ สาย TIP ด้วย $R\ 5.6K$ ลง GND ชั่วขณะแล้วกลับมาต่อสาย RING



Security Alarm Circuit

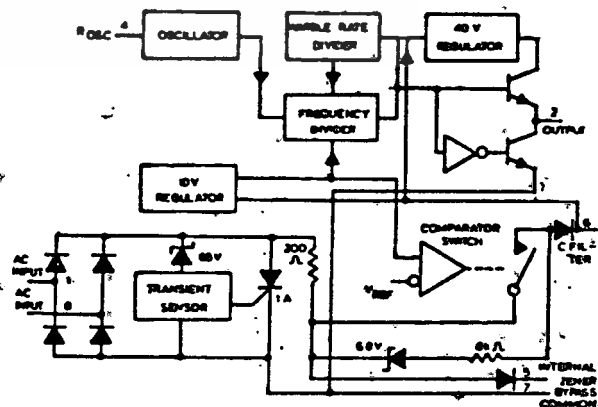


Functional Block Diagram - Ringer

OPTOISOLATOR จะเป็นตัวจ่ายกระแสให้ RING LINE SW ซึ่งแยกการใช้งานระหว่าง AC และ DC และ LED ของตัว ISOLATOR จะติดสว่างเมื่อ PULSE บวกเข้ามาแต่ละครั้ง (จาก PIN 9) เพื่อ COUPLING AC VOLTAGE ไปจ่ายให้ RELAY ในแต่ละคาบเวลา

เมื่อ RINGER GENERATOR ทำงานจะเกิดเสียงดังที่จวบจร RINGING เมื่อโทรศัพท์ถูกยก ขณะดังจะทำให้ กระแส DC เพิ่มขึ้น และ HSO เปลี่ยน STATE จาก LOW ไป HIGHT ซึ่งจะทำให้ Q2 ทำงานเกิดสัญญาณไป RESET IC TIMER ที่ PIN 4 ถ้าโทรศัพท์ไม่ถูกยกสัญญาณจะหยุดเองในที่สุด เหมือนกับผู้เรียกวางหู

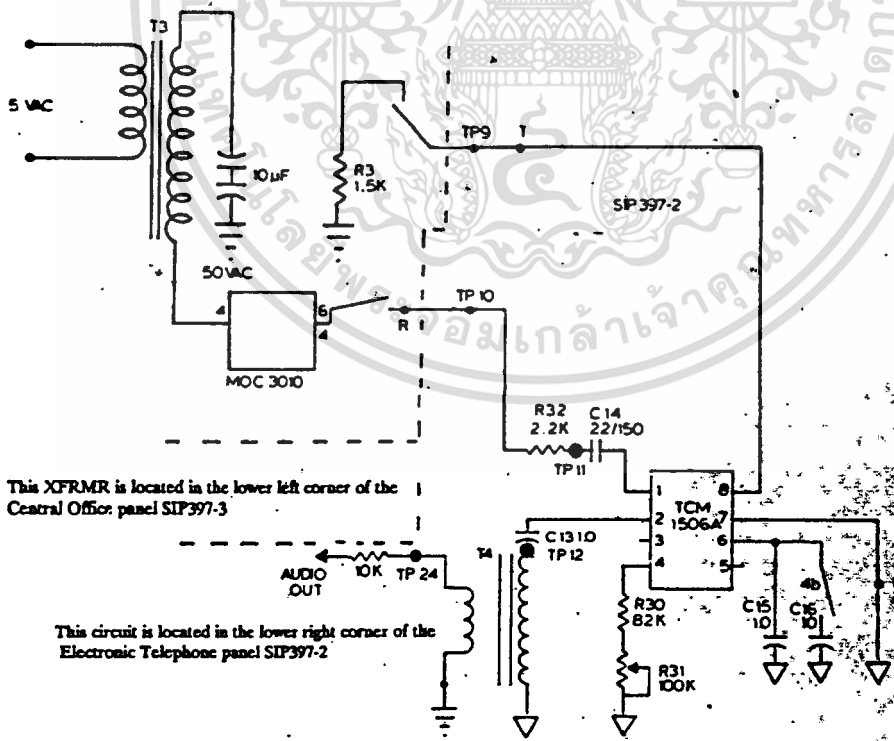หม้อแปลงที่อยู่ใน RING GEN จะให้ 50 V AC เท่านั้นถ้าต้องการมากกว่าก็สามารถทำได้โดยการเปลี่ยน หม้อแปลง



This XFRMR is located in the lower left corner of the Central Office panel SIP397-3

This circuit is located in the lower right corner of the Electronic Telephone panel SIP397-2

Tone - Ringer, Speaker Driver

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้ FIGURE 9-6 เท่านั้น โปรดอย่าให้นำไปใช้ประโยชน์ด้านการศึกษา

ไปว่ากรณิดังนั้นสืบ ลึกซึ้งหาวิธีให้ดัดแปลงปัญหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีกรณีนำไปใช้

SUMMARY

1. The electromechanical ringer can be replaced by a low-voltage IC (electronic) ringer.
2. The electronic ringer's output sound can emanate from a speaker or a piezoelectric transducer.
3. The electronic ringer can also be used in security applications.
4. The electronic ringer uses less current than the electromechanical ringer.
5. The frequency and volume levels of the electronic ringer are adjustable.
6. A ringer generator generally produces a voltage of 50-100 V. The duty cycle is 2 seconds on and 4 seconds off.
7. The ringer generator relay grounds the tip line and feeds the ring line.
8. Since the subscriber set needs dc to operate, it should not be removed from the loop during ringing.
9. When the hook switch is lifted, the hook-sense output of the SLIC device goes high, and the ringer generator is switched off.
10. In the same manner as the ringer generator is brought on the line by closing the hook switch, a dial-tone generator can be brought on the line.

Laboratory Experimentation

MATERIALS REQUIRED

SIP397-2 and 300 PSB or 300 B.
SIP397-3 and 300 PSB or 300 B.

TEST AND MEASUREMENTS


Three types of ringers are available: namely, the old-fashioned electromechanical bell; the piezoelectric transducer, which possesses a frequency range of 1-2.5 kHz, and the speaker driver, which possesses a range of 300 Hz to 1 kHz. In this experiment, the speaker driver will be evaluated.

DESCRIPTION - TCM 1506A

The TCM1506A is a monolithic, integrated-circuit, telephone-tone ringer driver that, when coupled with an appropriate transducer, replaces the electromechanical bell. Using BFET technology, these devices have been designed for use with an inexpensive, transformer-coupled speaker to produce a pleasing tone composed of a high frequency (f_1) alternating with a low frequency (f_2), resulting in a warble frequency. The device is powered and activated by telephone-line ring voltage, which may vary from 50-150 Vrms at frequencies from 15-68 Hz.

Interference from telephone DTMF or voice signals can be prevented without the use of expensive mechanical switches by relying upon a typical input impedance greater than 1 M Ω during low-voltage (off-hook) standby. This high standby impedance is achieved with the Zener diode, which is an integral part of the IC, and it is activated below a differential input voltage of typically 8.9 V (at pins 1 and 8). A differential voltage level of typically 17 V at pins 1 and 8 deactivates the internal Zener diode, allowing for a more efficient power transfer to the load when the device is in the operating mode.

During ringing, the impedance of the applied circuit, which varies from 8-30 k Ω over the Class B ring signal, is reasonably independent of the output load. Figure 9-5 shows a block diagram of a ringer and appropriate external protective circuitry. These devices incorporated lightning-protection features designed to allow the ringer to withstand lightning strikes of 1.5 kV for up to 200 μ s duration and transient protection, as well. In addition, the internal circuitry will reject dial pulses from parallel telephones in order that false ringing, or "tapping," does not occur.

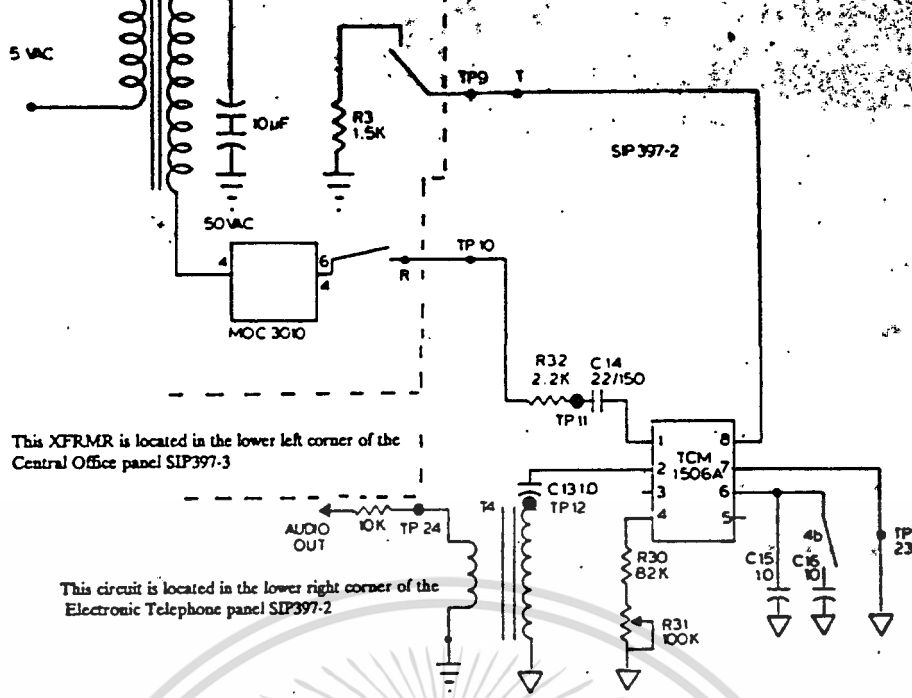


This XFRMR is located in the lower left corner of the Central Office panel SIP397-3

This circuit is located in the lower right corner of the Electronic Telephone panel SIP397-2

Tone - Ringer, Speaker Driver

FIGURE 9-6

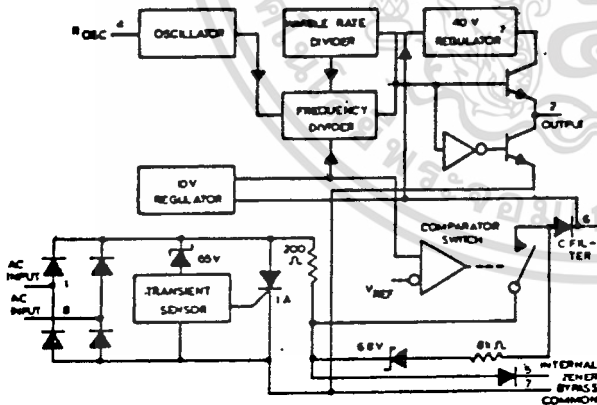This telephone-tone ringer driver can be used in nontelephone communications applications. For example, the devices can be used with a few external components to produce an inexpensive and highly efficient security alarm.



Functional Block Diagram - Ringer

FIGURE 9-5

The experimental ringer circuit to be tested is shown in Figure 9-6.


In the experimental circuit diagram, components R32 and C14 provide two functions. The capacitor blocks the dc current from the -48 V supply and the 2.2 kΩ resistor limits the line current. The bridge rectifier within the IC provides the operating dc voltage from the phone lines. The capacitor from pin 6 to the ground is used to filter the dc. Increasing the value of C14 causes the ringer delay in start up and close down.

The value of C14 also determines the minimum ringing voltage. The capacitor and the internal resistors reduce "tapping." A telephone which has a rotary dial or an electronic pulse dialer may cause the partial ringing of a second telephone on the same line. This ringing is referred to as "tapping."

The IC is "off" until an ac voltage, which appears at the internal bridge -- pins 1 and 8 -- reaches 8.9 V. Because in the "off" state the input impedance exceeds 1 MΩ, the ringer does not affect voice signals.

For high-voltage transient protection, a sensor and thyristor (SCR) are utilized.

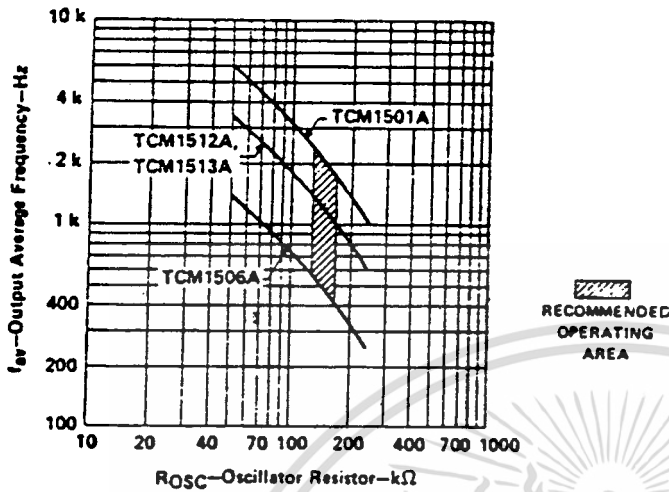The transformer-coupled output impedance is driven by a push-pull stage -- pin 2. A transformer with a turns ratio of 4 k Ω - 8 k Ω is recommended. Although a 1.2 k Ω transformer is more readily available and has been used, some power loss takes place.



Oscillator Frequency vs. R

(Circuits and Graphs Courtesy of Texas Instruments)


FIGURE 9-7

The resistors R30 (82 k Ω) and R31 (potentiometer) determine the frequency of the ring. R30 sets the upper frequency limits. Figure 9-7 shows a graph of the ROSC -- Oscillator Resistor -- k.

EXPERIMENTAL PROCEDURES

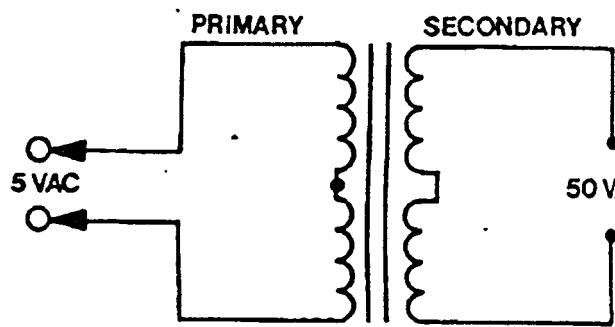1. Power up the prewired circuit of the ringer, shown in Figure 9-6. An ac voltage of 50-100 Vac is required to activate the ringer. On the SIP 397-3 panel this voltage is obtained from a pre-wired transformer located in the lower left corner. V_{in} (5 Vac) is automatically supplied to the transformer primary whenever the panel is inserted into a powered-up Master Builder (S300B) or a Power Supply Base (300 PBS). When measuring the transformer's voltages, remember to connect both leads of your ac voltmeter to the transformer's terminals. Do not connect the common lead of your ac voltmeter to chassis ground. To do so would result in erroneous voltage values. Figure 9-8 shows the transformer circuit arrangement.

The transformer shown is designed for a 110-230 V primary. The turns ratio provides 50-65 Vac



Wiring an Isolation Transformer for 50 Vac

FIGURE 9-8

The Electronic Telephone, SIP 397-2 panel, and the Central Office, SIP 397-3 panel, are moved close together. A jumper wire should be connected from the T terminal on the left hand edge of the Central Office board to the top "line" terminal on the right hand edge of the Electronic Telephone panel. Note that this terminal is directly connected to TP9 on the Electronic Telephone (SIP 397-2) panel. Next connect a jumper wire from the R terminal on the left hand edge of the Central Office (SIP 397-3) panel to the bottom "line" connector on the right hand edge of the Electronic Telephone (SIP 397-2) panel. Note that this connector is directly connected to TP10 on the Electronic Telephone (SIP 397-2) panel.

Two jumper wires are required for the tip (T) and ring (R) connections.

The Hook Switch on the Electronic Telephone (SIP 397-2) panel must be in the on-hook position for the ringer voltage coming from the Central Office to activate the ring detector circuit. Opening the Hook Switch (Hook Switch OFF) will stop the ringing signal. This action duplicates what happens on your home phone when your phone rings. When you pick up the handset (take the handset off hook) the ringing stops. Do not connect an outside ac voltage to the telephone panel.

When the RINGER-START button is depressed the ringer voltage will cycle on and off (4 seconds on and 2 seconds off). The ringing voltage appears at "T" and "R" on the Central Office panel.

2. Apply the 50 Vac to the "T" and "R" of the ringer, by pressing the ringer-generator start switch. Record the frequency of the sound heard. Vary the 100 k Ω potentiometer between its limits. f_1 _____, f_2 _____. The frequency is measured at audio out, Section O. Sketch the wave shape present.

3. Determine the line current used for ringing by measuring the voltage drop across the 2.2 k Ω line resistor. $I_L =$ _____ rms. The line voltage present at TP9 and TP10 is _____ V.

Notes:

A. The ringer can be interfaced with a voice circuit so that the tone is processed by the receiver which may be a speaker-type transducer. This circuit arrangement is not included in the experimentation.

B. In actual application, the ringer is located in front of the hook switch, and the ac line voltage is produced in the central office. As the loop length increases, the available voltage and the ringing level at the subscriber's set decreases.

RINGER-GENERATOR CIRCUIT

Refer to Figure 9-4. The 50 Vac voltage, which is cycled on and off, is used to control the ringer on a separate electronic telephone.

4. The student should connect a telephone to the central-office experimental system and initially evaluate the action of the ringer generator. Wave shapes should be observed for both monostable and astable circuits. The time periods should be recorded. Period ON _____, period OFF _____. ac-ringer voltage (rms) _____.

5. Relay action should be observed, both during ringing, and when the hook switch is lifted. Describe your observations of the circuit's operation. _____

REVIEW QUESTIONS

1. An electromechanical bell operates on _____ to _____ Vac.
2. The preferred ringer tone range is _____ to _____ Hz.
3. The ringer tone range also includes a low-frequency shift of _____ or _____ Hz.
4. Electronic ringers are basically _____.
5. A ringer is placed _____ the hook switch.
6. A ringer circuit derives its voltage from _____.
7. Piezoelectric transducers generally operate at frequencies above _____ kHz.
8. A ringer must be protected against _____.

9. Telephone "tapping" occurs when a telephone _____ as another phone on the same line is being dialed.
10. The electric ringer has an input impedance of _____.
11. When the ac ringer is on the loop, the loop also contains a _____.
12. The total ringer-generator period is _____ seconds.
13. The monostable time period is less than 10 seconds. True/False? _____.
14. HOS refers to _____.
15. AC ring voltage is applied to the _____ side of the loop.

EXPERIMENTAL ANSWERS

1. Procedural
2. FL 500 Hz; F_b 1 kHz; (square wave.)
3. $I_L = 1.3$ mA, rms; line voltage: TP9 - TP10 = approximately 65 V.*
4. Period on is 4 seconds; period off is 2 seconds. AC ringer voltage (rms) = 60.
5. When the ring-start button is pressed, the generator voltage pulses on and off. When the hook switch is closed, the supervising voltage from the SLIC interrupts the ringer relay. The hook-switch output (HSO) has a -15 volt swing.


ANSWERS TO REVIEW QUESTIONS

1. 80-120 Vac
2. 300-800 Hz
3. 3-6 or 9-13 Hz
4. Oscillators
5. In front of
6. Bridge rectifiers
7. 1 kHz
8. High-voltage spikes
9. Clicks or tinkles
10. Over 100 k Ω
11. DC current
12. 6 seconds
13. False
14. Hook-sense output
15. Ring

TELEPHONE - SET VOICE CIRCUITRY

INTEGRATED VOICE CIRCUITRY

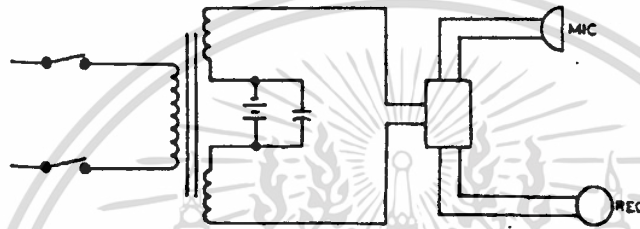โทรศัพท์แบบเก่าจะใช้ 2 สาย, ภายในโทรศัพท์สาย 2 เส้นจะถูกเปลี่ยนแปลง 4 สายโดยผ่าน HYBRID TRANSFORMER ดังแสดงในรูปที่ 10-1



Two- to Four-Wire Line Connection

FIGURE 10-1

ในวงจร 2 TO 4 LINE นี้ จะประกอบไปด้วยวงจร SIDE-TONE เพื่อผู้เรียกจะสามารถได้ยินระดับเสียงของตัวเองและเป็นส่วนประกอบของ LINE-BALANCING

CARBON-MIC จะกินกระแสประมาณ 20-25 MA, หูฟัง ซึ่งทั้ง 2 อย่างนี้ไม่สามารถ CONTROL อัตราการขยายได้ เราสามารถใช้อุปกรณ์ที่ทันสมัยกว่าแทนได้ในรูปที่ 10-2 แสดงให้เห็นถึง IC VOICE CIRCUIT เบอร์ TCM 1705 A ซึ่งนำมาใช้แทน HYBRID TRANSFORMER และเลิกใช้ CARBON-MIC อุปกรณ์นี้ผลิตโดยบริษัท TEXAS INSTRUMENTS และถูกออกแบบมาเพื่อใช้กับ MIC แบบ DYNAMIC หรือ ELETRET

การนำ IC นี้มาใช้แทน 2 TO 4 WIRE ทำให้ไม่ต้องใช้ MIC และเครื่องรับขนาดใหญ่, AMPLIFIER ที่ใช้กับ MIC และ EARPHONE จะเป็นแบบ FLAT และทำงานที่ VOLTAGE ต่ำๆ ที่ 4.3 V 12 MA ซึ่งมีอยู่ภายใน IC นี้ ระดับความดังของ SIDE TONE สามารถปรับได้

ทั้ง IC VOICE-CIRCUIT และ RINGER ที่แทนที่อุปกรณ์ MECHANICAL ขนาดใหญ่ๆ นี้จะให้ความเชื่อถือที่ดีกว่า IC RINGER ใช้แทนกระดิ่งไฟฟ้า อุปกรณ์ทั้ง 2 นี้สามารถทำงานได้อย่างดีด้วยราคาที่ต่ำกว่า

LINE REGULATOR

DC REGULATOR จะ SINKS กระแสจาก LOOP และ รักษา ค.ต.ท. DC ให้เหมือนกับโทรคั่นที่ทั่วๆ ไป RDC จะเป็นตัวปรับค่า ค.ต.ท.

MICROPHONE AMPLIFIER

สำหรับ IC TP 5700 มี AMPLIFIER เป็นแบบ SINGLE ENDED ใช้ร่วมกับ ELECTRET MIC ราคาต่ำได้ AMPLIFIER ชนิดนี้เมื่อเทียบกับ CARBON MIC แบบเก่าแล้ว จะให้ระดับสัญญาณรบกวนต่ำ อุปกรณ์เหล่านี้สามารถที่จะ COUPLED เป็น I/P ให้ AMPLIFIER ได้

MIC ที่มีคุณสมบัติที่ไวต่อเสียงควรมีย่านอยู่ในช่วง -60 ถึง -70 dBV / Bar ถ้าต้องการชดเชย LOSS ที่เสียไปสามารถทำได้โดยการเพิ่ม RESISTIVE POTENTIOMETER ที่ MIC INI หรือต่อระหว่าง PREAMPLIFIER O/P และ I/P DRIVER.

DRIVER STAGE ความคมชัดรายการแบบโดยอัตโนมัติซึ่ง GAIN จะลดลงเมื่อ LOOP LENGTH ลดลง AGC นี้สามารถปรับได้โดยค่าของ RAGC เพื่อกำหนดค่าสูญเสียมากที่สุดให้อยู่ใน $0-5$ dB

RECEIVER AMPLIFIER

ตัว AMP BUFFER นี้จะทำหน้าที่เพิ่มหรือลดสัญญาณที่รับเข้ามา, REVIN เป็น COUPLED AC ที่ PIN 4 และ AGC ภายใน AMPLIFIER เป็นตัวลด GAIN เช่น LOOP LENGTH ที่ลดลง AGC RANGE จะเป็นการปรับโดยอัตโนมัติขึ้นอยู่กับสัญญาณที่ส่งเข้ามา, PUSH-PULL COMPLEMENTARY O/P เป็นตัว BALANCED DIRECT DRIVE ของ DYNAMIC TRANSDUCER ซึ่งจะมีค่า IMPEDANCE ต่ำมาก ๆ ประมาณ 150 เกอห์ของเครื่องรับสามารถลดลงได้อีกโดยการต่อ ค.ต.ท. อนุกรมกับ TRANSDUCER เกอห์ของเครื่องรับจะลดลงอัตโนมัติ 20 dB เมื่อ MUTE I/P เป็น HIGH

SIDE TONE CIRCUIT

ระดับของ SIDE TONE CANCELLATION อาจปรับโดยการต่อค่า IMPEDANCE ที่ BALANCE จากภายนอกเข้าที่ PIN 4 และ COPLING จุดนี้ให้เป็น V+ สำหรับ CANCELLATION ที่ดีนั้น BLANCED IMPEDANCE ควรจะมีค่าประมาณ 10 เท่าของ I/P IMPEDANCE ของ SUBSC RIBER LINE I/P IMPEDANCE

DTMF AMPLIFIER

เป็น AMPLIFIER ที่เพิ่มเข้ามาเพื่อ ENABLE O/P ของ DTMF เพื่อเชื่อมต่อสายของ O/P สายนี้รวมทั้งสาย AGC ด้วยเมื่อ MUTE I/P เป็น HIGH I/P DTMF จะทำงานและ I/P MIC จะไม่ทำงานถ้า MUTE I/P เป็น LOW DTMF I/P SW จะ OFF และ MIC I/P จะ OFF ด้วย

VOLTAGE REGULATOR OUT PUTS

ค่าความคลาดเคลื่อนของ BAND-GAP VOLTAGE ของ IC จะเป็นตัวควบคุม REGULATOR ซึ่งทำหน้าที่ BIAS วงจรภายในและมี O/P ช่วยอีก 2 ตัวที่เพิ่มเข้ามา VREG1 จะเป็นตัวให้พลังงานกับ LOW VOLTAGE DTMF GENERATOR เพื่อเป็นการป้องกัน O/P ชนิดนี้ในสภาวะ LOW VOLTAGE ที่เกิดขึ้นมี VOLTAGE ตกคร่อมที่ SPEECH CIRCUIT และ VOLTAGE นี้อาจจะ SWING ต่ำกว่า O/P ของ VREG1 และ SW ภายในจะเป็นตัวควบคุม MAX CURRENT O/P ใน SPEECH MODE, MUTH IN จะเป็น LOW VREG1 จะมีค่าประมาณ $\frac{1}{2}$ ของ TIP-RING VOLTAGE และ กระแส O/P จะถูก LIMITED ที่ 200 MA


ค่า VOLTAGE นี้ก็พอดีที่จะจ่ายให้แก่ DTMF GEN ใน MODE STAN BY เมื่อ MUTE IN เป็น HIGH เพื่อ SWITCH จาก SPEECH CIRCUIT เป็น DTMF VREG1 จะถูกเปลี่ยนเป็น 2.7 V และจะมีกระแสเพียง 2 MA เท่านั้นที่จะจ่ายให้แก่ DTMF GEN

ถ้าเป็น TP 5700 O/P REGULATED จะประมาณ 1.2 V

TONE-DIALING TELEPHONE

รูปที่ 10-4 แสดงการ INTERFACING โดยตรงกับ LOW-VOLTAGE DTMF GEN VREG1 ให้ BIAS ที่จำเป็นน้อยที่สุด 2 V ซึ่งยอมให้ TP 5087 A รับรู้การกด KEY และจะดึง O/P MUTE เป็น HIGH, VREG1 จะเปลี่ยนเป็น 2.7 V จ่ายให้แต่ TP 5087A ระหว่างกำเนิด TONE I/P ของ TP 5700 DTMF จะรวมกับ LOAD RESISTOR ที่จำเป็น เป็น V- และให้ GAIN ออกมาและวงจร AGC จะทำงานโดยการ COMPENSATES เพื่อเปลี่ยน LOOP LENGTH ระดับของ MUTED TONE จะได้ยินที่เครื่องรับสำหรับ DTMF GEN ตัวอื่นที่ให้ระดับ O/P สูงกว่าตระกูล TP 5087A เราต้องใช้ RESISTOR ปรับค่าได้ต่อที่ I/P DTMP ของวงจร SPEECH เพื่อลดระดับสัญญาณลง

การใช้ TP 5700 สามารถลดอุปกรณ์ต่างๆ สำหรับการสร้าง PULSE-DIALING TELEPHON ดังแสดงในรูป 10-4 เราสามารถใช้ VREG1 แทนแหล่งจ่ายกระแสทั่วไปเพื่อจ่าย LOW-VOLTAGE 1.7 V แก่ TP 5098 โดยผ่าน BLOCKING DIODE และจะมี DIODE อีกตัวหนึ่งจ่าย VOLTAGE ให้แก่ TIPRING ถ้ากรณี VOLTAGE ของ TIP-RING น้อยกว่า 5 V จะมี C 100 MF สำหรับรักษาระดับ VOLTAGE ที่จ่ายให้แก่ PULSE-DIALER ในระหว่างหมุนสัญญาณ DIAL C ตัวนี้ต้องการเวลา 1 วินาทีสำหรับการประจุ เมื่อโทรศัพท์ถูกหมุนครั้งแรก แต่หลังจากนั้น R 20 M จะรักษาแรงดันที่ C เอาไว้ PARTIAL MUTING ได้จากการต่อ O/P MUTE โดยตรงกับ PULSE DIALER และ PIN 9 ของวงจร SPEECH ของ IC TP 5700 บางทีอาจพบว่าเครื่องรับโทรศัพท์จะประกอบด้วย IC 3 ตัว โดย TOUCH-TONE DIALING, VOICE CIRCUITRY และ INTERFACING จะอยู่ภายใน IC ตัวเดียวส่วน IC ตัวอื่นที่จะศึกษาต่อไปจะเป็นตัว INTERFACE กับเครื่องมืออื่นๆ

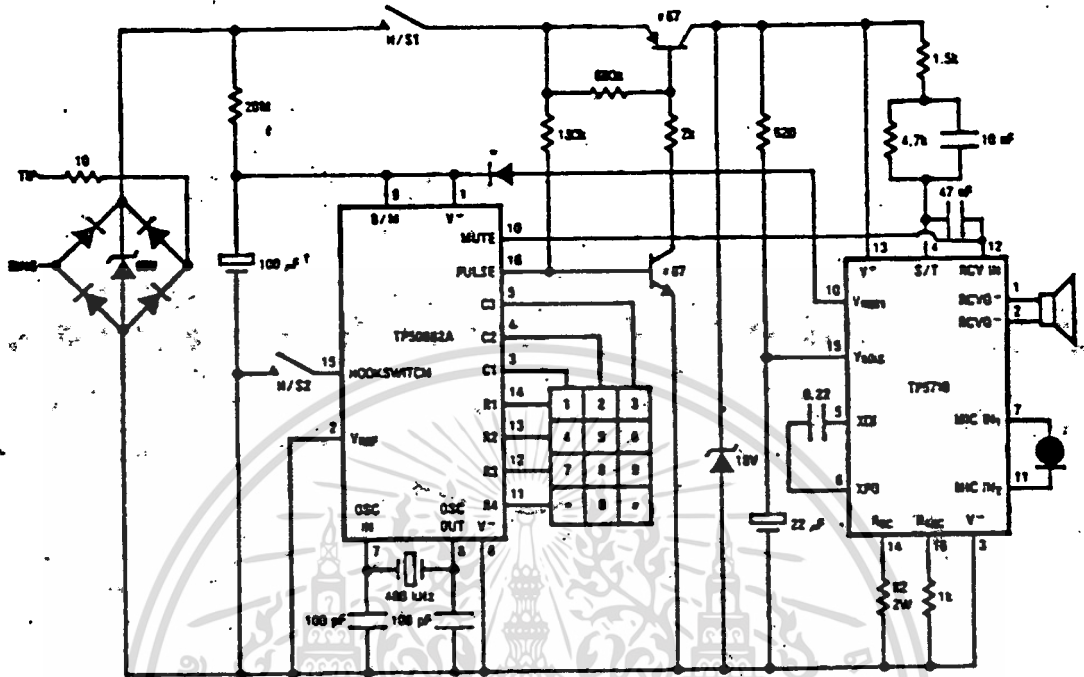

Pulse-Dialing Telephone

FIGURE 10-4

รูปที่ 10-4

ในการทดลองจะใช้ IC TCM 1705 ซึ่งผลิตโดยบริษัท TEXAS INSTRUMENTS วงจรโทรศัพท์จะดึงกำลังงานจาก LOOP แม้ว่า VOLTAGE SUPPLY จะเป็น 48 V และวงจรจะต้องการเพียง 3.5-5 V ในรูปที่ 10-6 แสดงวงจร I/P ซึ่งได้รับ SUPPLIED จาก SUBSCRIBER, วงจร BRIDGE จะทำให้เข้าถูกต้อง และ DI จะเป็นตัวจำกัด VOLTAGE ไว้ภายใน 12 V

ความต้านทานในโทรศัพท์ที่ไม่เป็น ELECTRONIC จะมีค่า 400 เมื่อกระแสของ CARBON MIC เท่ากับ 23 mA และ SUPPLY VOLTAGE เท่ากับ 48 V ความต้านทานใน LOOP รวมกับ ค.ต.ท. ที่หน้าสัมผัสของ REALY ที่ CENTRAL OFFICE จะเท่ากับ 48/.023 (เท่ากับ 2.09 K) เมื่อโทรศัพท์ที่มีความต้านทานตกคร่อมเท่ากับ 800 ความต้านทานในสายจะเท่ากับ 2.09 K - 800 ซึ่งเท่ากับ 1.289 K (ใช้จริงเท่ากับ 1.30 K) ด้วย VOLTAGE 48 V, ZENER 12 V และ ค.ต.ท. 1.3 K ของสายจะให้กระแส 28 mA ซึ่งเพียงพอสำหรับ IC VOICE

ในเครื่องรับ, โทรศัพท์จะถูก DECOUPLED จากสายด้วยค่าของ R1 และ R2 และเครื่องขยายคือ R-A5 จะรับสัญญาณจาก C2 และ C5, TRANSMITTER ป้อนสายผ่าน AMP A1, AT และ A3, AMP AT และ AR สำหรับเพิ่ม GAIN และค่าที่เพิ่มมานี้จะชดเชยค่าที่เสียไป เนื่องจากความยาวของสาย, R6, R7 และ C5 คืออุปกรณ์ SIDETONE-BALANCING ความถี่สามารถผ่านวงจร HYBRID ได้โดยผ่าน C ที่คร่อม R1 และ R2

REGULATOR จะทำหน้าที่รักษา VOLTAGE ที่ว่างให้ AMP และควบคุมกระแสที่จ่ายให้แก่ AT และ AR AMP A1 จะให้ GAIN แก่ MIC และ T ค่า GAIN ของ T และ R จะถูกปรับตลอดสายโดย AMP ที่อยู่ใน REGULATOR, R13 มีไว้เพื่ออ้างอิงแก่ AMP และ ค.ต.ท. ของ R2 ที่ได้จาก VOLTAGE DIVIDER

เนื่องจากกระแสในสายมีการเปลี่ยนแปลงเพราะฉะนั้น GAIN ในสายจะถูกปรับไปด้วยเมื่อ R12 SHORT, GAIN จะถูกทำให้ขึ้นอยู่กับ การเปลี่ยนแปลงของสายวงจร AGA คือตัวหนึ่งของวงจร AGC, GAIN ของ TRANSMITTER สามารถปรับได้ด้วย R4 และ ระดับของ MIC GAIN ของ TRANSMITTER จะถูกควบคุมด้วย R5 ส่วน C7 จะเป็นตัว BYPASS สัญญาณค่าของความต้านทาน และ R FEED BACK สามารถปรับ GAIN ของ T ถ้าให้ค่า R5 น้อยๆ จะเป็นการลด GAIN สภาวะทาง O/P ของ TRANSMITTER จะเป็นตัวจ่ายกระแสให้สาย, ระดับของกระแส และ ค่า IMPEDANCE ที่เห็นสามารถปรับได้ด้วย R13

AMP AR และ A5 จะเป็นตัวควบคุม GAIN ของเครื่องรับ และ ระดับของ AGA O/P จะเป็นแบบ PUSH-PULL ซึ่งจ่ายแก่ R10 และ R11 และจะเป็นตัวควบคุมกระแสที่ไหลใน RECEIVER COIL สัญญาณ I/P จาก LINE จะส่งผ่าน C2, R6, R7 และ C5 อัตราส่วนของ R2 และ R1 จะเป็นตัวกำหนด RECEIVER GAIN

Laboratory Experimentation

MATERIALS REQUIRED

SIP397-2 and 300 B or 300 PSB.
SIP397-3 and 300 B or 300 PSB.
Variable Resistor Wheel

TEST AND MEASUREMENTS

In the laboratory experimentation, a TCM1705 speech-circuit IC will be evaluated. Because specialized telephone testing instruments may not be available, certain tests are omitted and changes in procedures are necessary. Isolation transformers T1 and T2 are 600 Ω , 1:1, isolation.

EXPERIMENTAL PROCEDURES

1. Power up the prewired circuit 397-2 section N (TCM1705 amplifier). Be sure to use the correct supply voltages as indicated on bottom of the board, and refer to Figure 10-6. The tip and ring inputs can be fed with up to 48 V from a power switch set to the central-office supply (397-3). For a local voltage source, set the power switch to "local," and the hook switch to "off." In this position, the tip is placed at ground and the ring at -10 V. Measure the input voltage at TP13 _____ and TP14 _____.
2. On the telephone panel, check the effects of the bridge when the line voltage is reversed. Measure the voltage between TP15 and TP16 when the loop wires from the central office to the telephone panel are reversed. Voltage TP15-TP16 _____.

AMPLIFIER TESTS

3. Since most function generators do not have a differential output, a 600:600 Ω line transformer is used to develop the differential signal. Open switch 1a and close 2a. Set the power switch to "local," disconnecting the microphone and connecting in the signal transformer. Set the generator to a 1 kHz sine wave, at a 2 mV level. Feed the signal into transformer T1, and connect one channel of the oscilloscope to the secondary of transformer T2. (Make sure that no saturation of the amplifiers occurs).
4. View the input signal at the input of T1 and the transmitter output at TP17. Is there a gain or loss? Record _____.
5. While feeding the signal to the transmitter, record the output from the receiver (across T2) _____. How much signal would be present if the sidetone circuit were completely balanced?

RECEIVER GAIN MEASUREMENTS

6. Simulate an incoming receiving signal by connecting a 2 V, 1 kHz signal to transformer T3. The receiver output at TP20 is _____ and input of TP28 is _____. The receiver gain is _____.
7. The receiver gain is dependent on the ratio of R12, the resistance, in steps, down to 47 Ω 's. Observe the speaker output at T2. What happens to the signal? _____.


SIDETONE

8. Return the generator to the transformer T1, and record the transmitted input at TP19, _____ and at the output, TP2 _____.
9. Place a resistance box across the sidetone resistors R6 to TP18. Reduce the value by paralleling a resistor. Start at 60 k Ω , and determine what happens when the resistance value is reduced.
10. Close switch 1a and open 2a, in order to connect the microphone. View the output at TP13, and speak toward the microphone. Try distances of up to 10 feet. This exercise provides an idea of microphone and amplifier sensitivity.

OPTIONAL

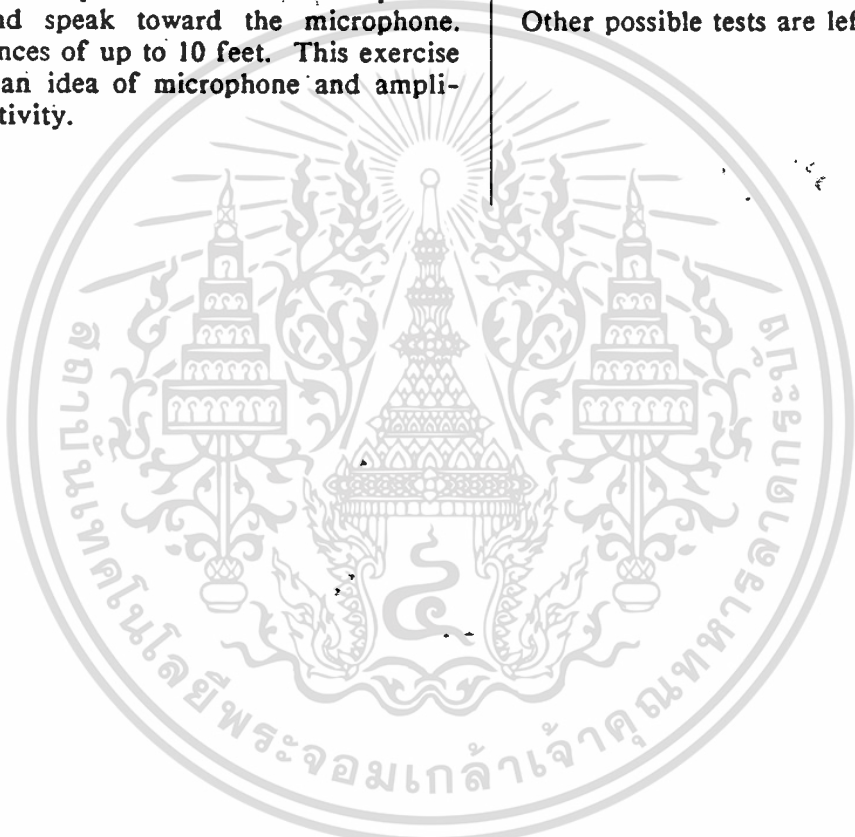11. It is also suggested that the pass-band be evaluated.
12. Feed the line with 48 V, and at the supply couple in an audio signal, thereby simulating the central-office feed.
13. Connect an electret microphone and a receiver from an electronic telephone. Tap into the microphone and listen to the receiver's sidetone level.

Other possible tests are left to the student.



REVIEW QUESTIONS


1. The sidetone circuit enables a speaker to _____ himself.
2. A transmitted voice signal is a differential voltage between the loop lines. True/False? _____
3. Although the speech circuit is _____ of the receiving circuit, the sidetone circuit enables the speaker to adjust the volume level of his voice.
4. A voice-circuit IC functions similarly to a _____ wire transformer.
5. A voice-circuit IC is designed for an _____ microphone.
6. Voice circuitry includes a form of _____ to compensate for line changes.
7. Muting is used to _____
8. A DTMF generator can be fed through _____ to the line. True/False? _____
9. A voice-circuit operates on a _____
10. A UDLT is used to feed both _____ and _____ to a loop. The voices must first be converted into a _____ format.
11. In the telephone a _____ transformer converts a 2-wire incoming line into a _____-wire connection for use by the microphone and receiver.
12. The sidetone amplifier enables the person speaking to _____

EXPERIMENTAL ANSWERS

1. Procedural
10 V supply
TP13 = -2 V
TP14 = -7.8 V (to ground)
2. -4.25 V (TP15-TP16)
3. Procedural
4. T1 = 2 mV
TP17 = 2 V
Gain = 1000
5. Across TP2 = 1.6 V
Completely bal. = 0
6. TP20 = 2 V
TP28 = 2 V
Rec. G = 1
7. The gain is reduced.
8. TP19 = 1.6 V
TP2 = 1.7 V
9. The sidetone decreases.
10. Observation
11. Optional Tests
12. Optional Tests
13. Optional Tests

ANSWERS TO REVIEW QUESTIONS

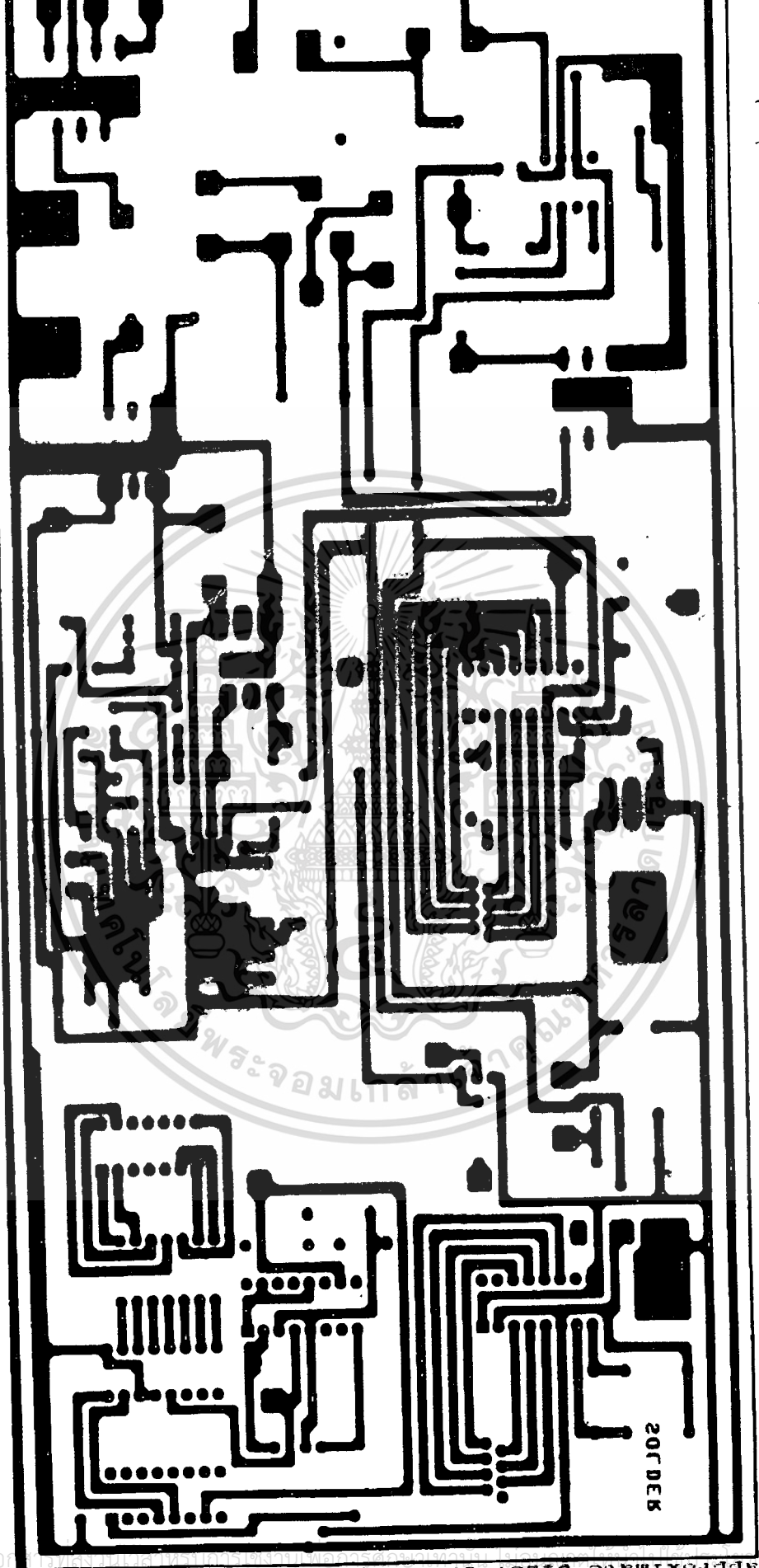1. Hear
2. True
3. Independent
4. Two
5. Electret
6. AGC
7. Cut off the speaking voices
8. Transmit amplifier
9. False
10. Voice and data; pulse
11. Hybrid; 4.
12. Hear his/her own voice




SOLDER

เอกสารนี้เป็นเอกสาร
ที่จัดทำขึ้นโดย
ไม่ว่ากรณีใดๆ

สงวนลิขสิทธิ์
และต้องอ้างถึง
ชื่อของ
ผู้จัดทำ
เอกสารนี้
ไว้ด้วย
ถ้ามีการ
นำ
ไป
ใช้
โดยไม่
ได้รับ
อนุญาต
ก่อน
จะ
ใช้
จะ
ถือว่า
ผิด
กฎหมาย
ลิขสิทธิ์
และ
ต้อง
อ้าง
ถึง
ชื่อ
ของ
ผู้
จัดทำ
เอกสาร
นี้
ไว้
ด้วย
ถ้า
มีการ
นำ
ไป
ใช้
โดยไม่
ได้รับ
อนุญาต
ก่อน
จะ
ใช้
จะ
ถือว่า
ผิด
กฎหมาย
ลิขสิทธิ์

ด้าน
การ
ค้า

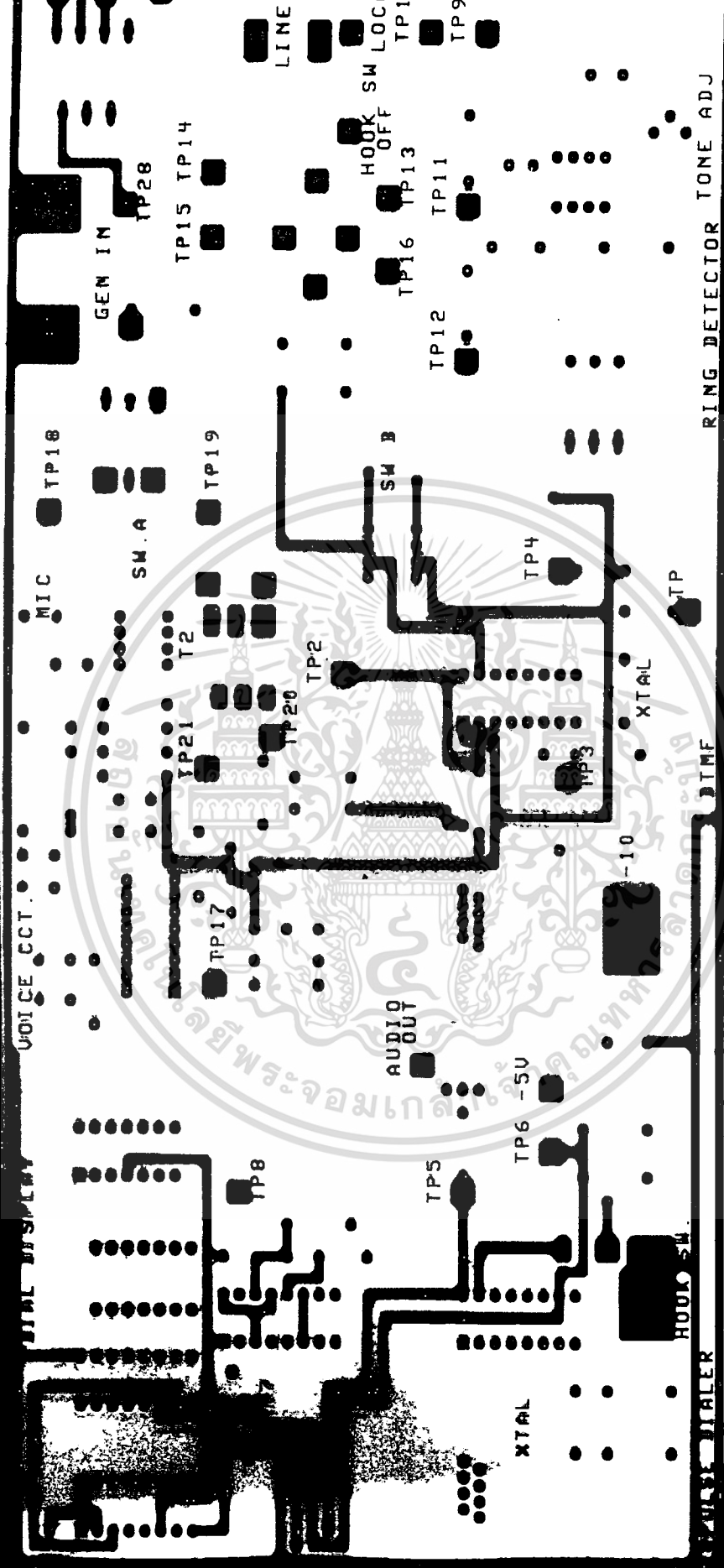

VOICE CCT

DIAL DISPLAY

MIC

GEN IN

SW A

TP15 TP14

TP8

LINE

TP2

AUDIO OUT

LOC

HOOK SW OFF

TP5

TP16

TP13

TP12

TP11

TP1

TP9

TP6 -5U

TP4

XTAL

-10

XTAL

HOOK SW


TP

COURSE TUNER

DIMF

RING DETECTOR TONE ADJ

ELECTRONIC TELEPHONE

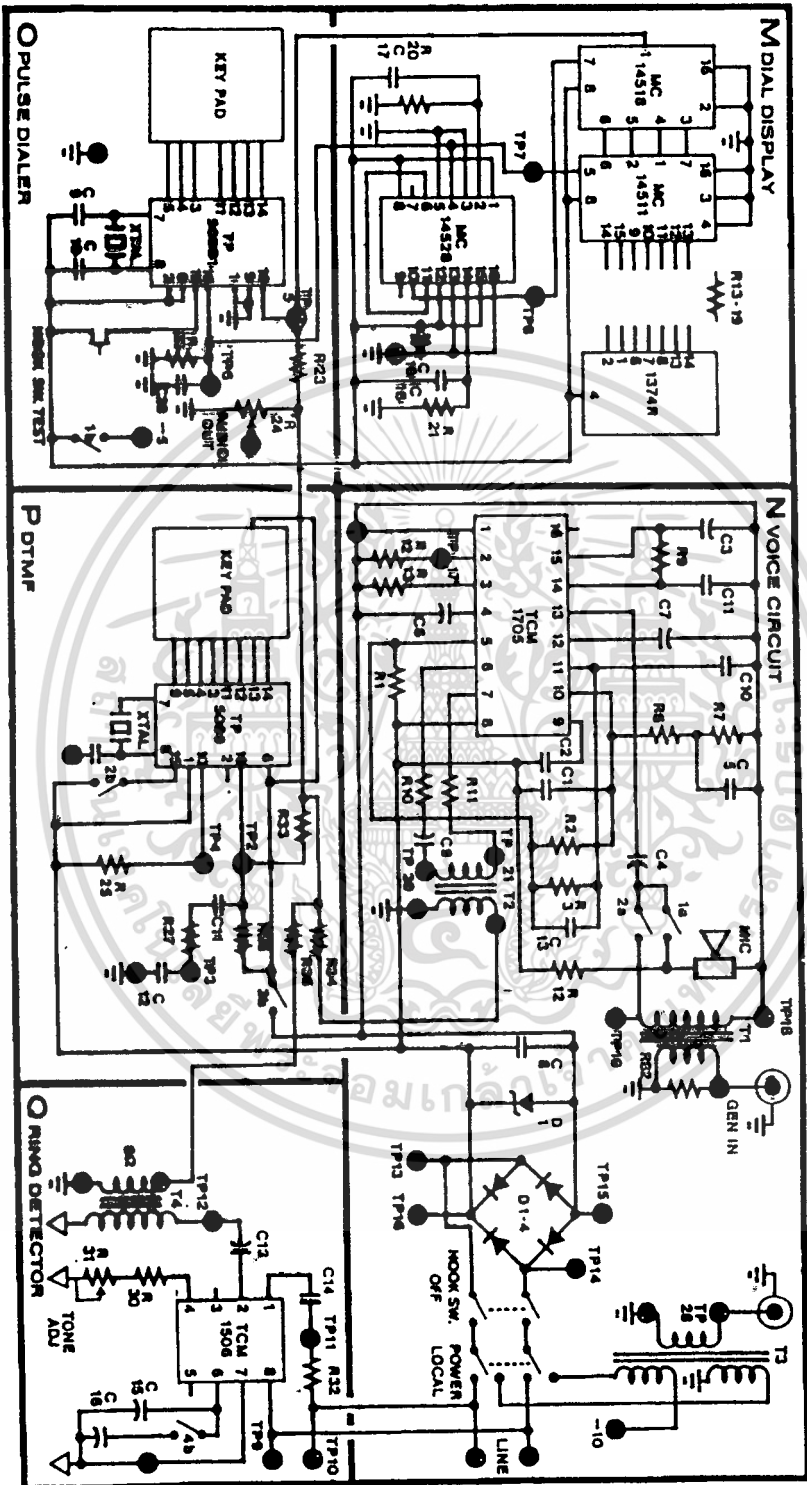

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆ ทั้งสิ้น อีกทั้งห้ามมิให้ดัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

" The Central Office "

Central office คือจุดเชื่อมต่อระหว่าง ผู้ใช้ 2 คน โดยมันจะเป็นตัวจัดเตรียม เลขหมาย และรวมไปถึง การเข้ารหัส และการถอดรหัส สัญญาณ analog เพื่อต่อสาย ของผู้ใช้เข้าด้วยกัน ซึ่งข้อมูลต่าง ๆ เกี่ยวกับ Subscriber's loop และสัญญาณนั้น รวม อยู่ใน การทดลองเรื่อง telephone set แล้วรวมทั้งการปฏิบัติการของ โทรศัพท์ แหล่งจ่ายไฟ และ การส่งผ่าน สัญญาณ

หน้าที่รับผิดชอบของ Central office คือ

1. The telephone power source.
2. Switching.
3. Digitizing.
4. Addressing.
5. Supervising Signals.
6. Alerting Signals.
7. Test Signals.

Central office จะเตรียมไฟ 48 v ให้สำหรับ C.O. และ Subscriber's phone รวมทั้ง power สำหรับ office Switching และ lamp illumination อุปกรณ์บางตัวของ C.O. อาจจะทำงาโดย supply แยกต่างหาก, battery ส่วนกลางจะทำหน้าที่ป้อนไฟเลี้ยงวงจรสำหรับปรับแต่ง Signal จาก โทรศัพท์ ให้ดี

สัญญาณจะถูกห่อหุ้มโดยตรงและถูกควบคุมโดย Signal Current และ Switching equipment เพื่อส่งข่าวสารที่ผู้ใช้ต้องการ ผู้ใช้สามารถรู้ได้ว่าสายว่างหรือไม่จากสัญญาณ dial tone

Subscriber's Line Interface Circuitry

SLIC คือ subscriber's line interface circuitry ซึ่งอยู่ใน central office แต่จะมีบางส่วนอยู่ใน subscriber's handset, subscriber's card ประกอบด้วยอุปกรณ์มากมาย ที่เกี่ยวกับการพูด ส่วนประกอบที่สำคัญอื่น ๆ ก็มี battery feed,

วงจรป้องกันไฟเกิน, กระดิ่ง, การควบคุม, การเข้ารหัส, ผสมกับการ test ซึ่งใช้ตัวย่อว่า "BORSCHT"

วงจรทั้งหมดนี้จะรวมอยู่ใน IC ตัวเดียวที่ใช้ใน subscriber's handset ส่วน IC ตัวอื่น ๆ ก็คือ UDLT (UNIVERSAL DIGITAL LINE TRANSCEIVER) ซึ่งจะกล่าวถึงในส่วนของการพูด

เป้าหมาย

เมื่อเสร็จสิ้นบทเรียนนี้พร้อมกับการทดลอง นักศึกษาจะสามารถ :

1. อธิบายแต่ละหน้าที่การทำงานของ BORSCHT.
2. อธิบายการทำงานของ SLIC.
3. ตรวจสอบ และประมาณการทำงานของ SLIC ได้ 2 วิธี คือ
 - การควบคุมกระแส
 - วิธีการจัดการ

BACKGROUND DISCUSSION

โรงงาน IC ทั่ว ๆ ไป จะผลิตแบบแยกหลาย ๆ วงจรรวมอยู่ในตัวเดียวกัน คือ LSI ซึ่งจะมีทั้งวงจรถ่าย, coder, decoder, voice circuit, วงจรป้องกันอุปกรณ์ และสายควบคุมซึ่งในความเป็นจริงผู้ใช้อาจเลือกใช้วงจรถ่ายเล็ก ๆ นี่วงจรเดียวก็ได้การทบทวนเรื่องโทรศัพทศาสตร์มาก่อน หน้าที่ จะอธิบาย ถึงตัวที่ใหม่กว่าก็เพื่อให้ นักศึกษาได้เรียนรู้เกี่ยวกับ พื้นฐานการทำงานของมัน

สาย 2 สายซึ่งต่อระหว่าง subscriber กับ central office นั้นต่อโดยตรงกับ DCCURRENT เพื่อสำหรับการพูด และการส่งสัญญาณเมื่อยกหูโทรศัพท์, กระแสสลับสำหรับกระดิ่ง dial tone, และสัญญาณไม่ว่าง, สัญญาณ pulse, หรือสัญญาณเสียง, สัญญาณ การจัดการและสัญญาณยกเลิก การติดต่อ ซึ่งสัญญาณทั้งหมดนี้จะต้องเรียกกันเป็นลำดับ และ ส่งออกและต้อง คำนึงถึงวงจรถ่าย Voltage เกิน วงจรทั้งหมดนี้เรียกย่อ ๆ ว่า "BORSCHT"

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆ ทั้งสิ้น ลึกซึ้งหาปริทัศน์ให้ชัดเจนก่อนอ่าน และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

ความหมาย คือ

1. Battery feed.
2. Overvoltage protection.
3. Ringing.
4. Supervision.
5. Coding.
6. Hybrid.
7. Test.

อุปกรณ์ทั้งหมดนี้จะประกอบอยู่บน SLIC (subscriber's loop interface card) ซึ่งอยู่ที่ส่วน Central office

Battery feed เกิดขึ้น เมื่อ 48 v battery ใน central office จ่ายกระแส 20 ma. ออกมาซึ่งสามารถเพิ่มเป็น 100 ma. ได้, กระแสนี้จะกระตุ้นอุปกรณ์ใน central office ซึ่งจะแนะนำให้ปิด hook ที่ subscriber's phone.

อุปกรณ์ป้องกันไฟเกิน จะทำหน้าที่ลดสัญญาณรบกวนซึ่งเกิดจากรinger และแหล่งจ่ายอื่น ๆ ลงให้เหลือต่ำที่สุด และเป็นการป้องกัน การรบกวนจาก Hybrid Transformer ใน Subscriber's telephone ด้วย ในรูปที่ 12-1 แสดงถึงวงจรใน Subscriber's handset Capitor C1 ป้องกัน กระแส จาก Ringer

วงจร filter ซึ่งประกอบด้วย R1 และ C2 จะป้องกันการเกิด spikes จากการหมุนสัญญาณ dial ที่ switch S3, ในแต่ละ pulse SW4 ซึ่งแยกจากตัวเครื่องจะทำหน้าที่ทำให้เจียน RV1, RV2, และ RV3 เป็นตัวกรองสัญญาณ spike ซึ่งเกิดจากการ over voltage

หม้อแปลง hybrid ถูกติดตั้งในรูปแบบนี้จนกระทั่งเกิดสัญญาณเสียงขึ้นที่วงจร sidetone ของ เครื่องรับ ซึ่งก็คือการลด Volume นั้นเอง, กระแสผ่านสัญญาณจะถูกทำให้เข้ากับ balance line โดยใช้ balancing net work ซึ่งประกอบด้วย L4, C3, C2 และ C4

หม้อแปลง hybrid มีใช้ใน central office เพื่อเปลี่ยนระบบจาก 2 เป็น 4 สาย หม้อแปลง hybrid นี้จะสามารถเตรียมคู่สายให้ซึ่งทั้ง 2 สายสามารถพูดและฟังได้. ในระบบ 4 สายจะใช้ในหน้าที่การเชื่อมโยง กระดิ่งไฟฟ้าจะรับ voltage 90 Vac 20 HZ ซึ่งจะต้องวางให้ห่างจากหูฟัง เพราะจะเกิดการ OSC ได้, ไฟ 90 V นี้ ในอดีตใช้ แต่ในปัจจุบัน ไม่ต้องการใช้แล้ว Coil คู่ใน Central office จะทำหน้าที่เพิ่มกระแสเมื่อผู้ช่วยโทรศัพท์ซึ่งจะทำให้ Relay ทำงานโดยต่อสัญญาณ dial tone, การให้รหัส และถอดรหัส หมายถึงการ Mod Code รวมถึง การทำงานของ BORSCHT ด้วย BORSCHT นี้ถูกออกแบบสำหรับ balance สายซึ่งสามารถทำให้บรรลุเป้าหมายได้โดยไม่ต้องการ Transformer ซึ่งต้องใช้เนื้อที่มาก

บริษัททั่ว ๆ ไปมักประสบปัญหาการติดต่อสื่อสารโดย subscriber's handset ดังนั้นในปี 1987 บริษัท Motorola จึงได้คิด ULDT ขึ้นเพื่อที่จะสามารถ ถอดรหัส, เข้ารหัส เตรียม คู่สาย และ ผสมสัญญาณ analog กับ digital อุปกรณ์ SLIC จะทำหน้าที่เตรียม คู่สายที่ Central office ซึ่งมีเบอร์ MC 3419 ของ Motorola ซึ่งถูกออกแบบมาเฉพาะหน้าที่นี้

IC MC 3419 สามารถที่จะเชื่อมต่อกับวงจร CODEC สำหรับการเข้ารหัส และต่อกับ microprocessor controllers ในระบบที่สมบูรณ์

รูปที่ 12-2 แสดงถึงวงจร IC SLIC ซึ่งถูกออกแบบให้ใช้ในระบบโทรศัพท์

1. As presented herein the SLIC refers to the subscriber's loop interface circuit or card, located at the central office. Some of the functions of this card can be replaced by an IC.
2. BORSCHT, located in the CO, refers to key interfacing requirements between the subscriber's set and the central office.
3. In older equipment, the hybrid transformer is used to convert a 2-wire line into a 4-wire line. This conversion permits the placement of the microphone and the receiver in the handset, as well as the separation of the transmit and the receive in the SLIC.
4. The SLIC device replaces the 2- to 4-wire transformer.

Laboratory Experimentation

Whenever you use the SIP397-3 panel with the Master Builder or the Power Supply Base be sure to set all voltage sources to maximum V_{out} . This panel requires maximum V_{out} for the ringer circuit.

MATERIALS REQUIRED

SIP397-3 panel and 300 B or 300 PSB.

TEST AND MEASUREMENTS

A SLIC performs the function of a hybrid transformer and contains many of the BORSCHT operations. The SLIC will be evaluated for talking, batter control, line balance, longitudinal-mode measurements, stage gain, and supervisory functions.

EXPERIMENTAL PROCEDURES

Figure 12-4 shows both an experimental circuit, which can be constructed, or a prewired test circuit, which can be evaluated. Several different measurements are to be made. The IC normally operates from a -48 V supply, but the IC can operate down to -20 V. Minus 20 V is obtained from the Master Builder by connecting the +5 V supply in series with the -15 V supply such that -20 V with respect to ground is obtained.

GAIN MEASUREMENTS

1. Gain is measured by feeding a signal into the line input and viewing the output at V_{TX} . Since a differential source is required, a transformer is connected to the input. The capacitor C30 prevents dc current from flowing through the windings. R1, the 470 Ω resistor, provides a dc

load, and the loop current is in the range of 20 mA. When switch 1a is closed, resistors R2 and R3 simulate the resistance of the wire lines. The loop resistance is approximately 1.4 k Ω , not counting the SLIC input.


Close 1a, 2a, 3a and open 4a to connect the transformer, and feed a 1 kHz sine wave into TPI. All other SIP397-3 switches can be ignored until further notice. Use a voltage of 0.1-0.3 V_{pp} , which is referred to as V_{in} . View the output at V_{TX} . (The operating supply is +5 V and -15 V.) Minimum operating voltage is -20 V.

The power-up switches, 2a and 3a, should be closed. How much gain is provided? _____

2. Gain is controlled by the 220 k Ω feedback resistor R15 and R13 (the 20 k Ω resistor). Place a resistor decade box across R15.

Start with 1 M Ω and reduce to 220 k Ω . What happens to the forward gain? _____

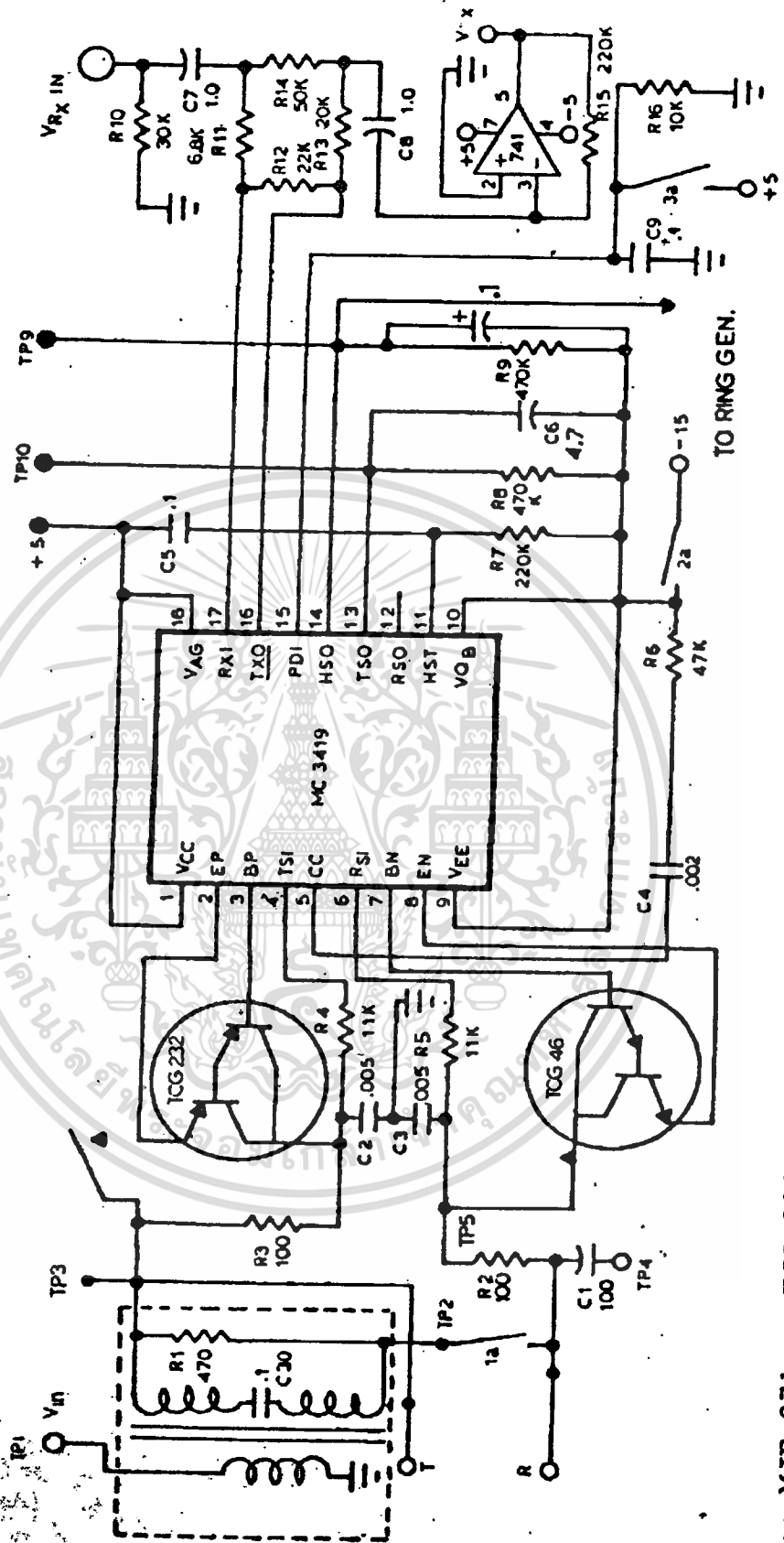3. Remove decade box from R15. Try feeding the same generator signal through the IC in the opposite direction. Connect the signal to V_{RX} (input) and view the output at TPI. How much gain is provided? _____ (Reverse gain is controlled by R11. The IC is bi-directional and acts as a transformer with a turns ratio of 1:1.)



SLIC Experimental Circuit

FIGURE 12-4

Note: MJE 271 or TCG 232
 MJE 270 or TCG 46

4. Check the static voltages for each PIN and the gain in both directions.

Pin		Pin V	
ON	OFF	ON	OFF
1. _____	_____	10. _____	_____
2. _____	_____	11. _____	_____
3. _____	_____	12. _____	_____
4. _____	_____	13. _____	_____
5. _____	_____	14. _____	_____
6. _____	_____	15. _____	_____
7. _____	_____	16. _____	_____
8. _____	_____	17. _____	_____
9. _____	_____	18. _____	_____

Forward Gain = _____, Reverse Gain = _____.
If the loop current is too far from its proper operating level, the SLIC will power down.

LONGITUDINAL VOLTAGE MEASUREMENT (V_{LON})

This is the common-mode measurement, which is used to determine how well the SLIC IC will reject power-line pickup and other noises common to both lines.

5. The generator settings will be essentially the same as for gain measurement. Set switch A1 high. Clip leads TP2 and TP3 together, and feed a 1 kHz signal into TP4. The clip lead shorts out the transformer, and the loop leads are fed in parallel. Record the signal output V_{TX} . If the output voltage is very small, increase the generator's output and obtain at least a 0.1 V_{PP} V_{TX} signal. Record the voltage at the output and at TP4. _____ V_{TX} _____ TP4. Compute the reduction in voltage in dB; this measurement is known as the common-mode ratio (CMR). It is computed from $\text{dB} = 20 \log V_{LON}/V_{TX}$ _____. Note: Since the output will be smaller than the input, use the reverse ratio V_{LON}/V_{TX} and call this a negative gain, -dB.
6. Compare the V_{LON} with the unity gain amplifier. Unity gain is equal to 0 dB. Note: Since the input and output are not equal in impedance, an error may exist.

If the V_{TX} output recorded in the V_{LON} measurement was 0.1 V, set the signal input into TP1 (jumper removed), in order that the V_{TX}

remains 0.1 V. Compare V_{LON}/V_L . V_{LON} measured at TP4. _____ V_L : use a value of 0.1 V. The output is stated as a negative dB value. Typical values listed in the data sheets (MC 3419L) are -45 to -50 dB. State your computed value. _____ This measurement is also referred to as the common mode rejection ratio (CMRR).

POWER UP/DOWN

7. This is a simple test. As long as a signal is being processed by the SLIC, a power-up condition must exist. Terminal 15 (PDI) must be high, +1 or 5 V. With no signal, the IC can be powered down (PDI = 0 or -V).

Pass a signal through the IC (V_{TX}/V_L), and open 3a to change PDI from +5 to ground. This is a current-saving procedure. Does the signal cut off when in power down? _____. Slide 3a to +5 V for power up.

LOOP CURRENT

8. The loop current should be the same in both wire lines. The current in both loops can be determined by measuring the voltage directly across resistors R2 and R3. Switch 1a must be closed. Use a DMM to record the differential voltage drop. The current $i_1 =$ _____ $i_2 =$ _____. (Use Ohm's law.)
9. When the line currents are not equal, what is the effect on the CMR? _____

TRANSYBRID REJECTION

10. Transhybrid rejection refers to the leakage of signal between the forward and the reverse amplifiers. It is the ratio of V_{TX}/V_{RX}

Feed a slightly less than 3 V_{PP} , 1 kHz sine wave signal into TP1, and record the outputs at V_{TX} _____ and V_{RX} _____. (Note: If V_{TP1} is greater than or equal to 3 V_{PP} , serious distortion and loss of amplitude will occur. This effect will cause no problems, but you may find it easier to use nondistorted wave shapes.) If V_{RX} is too small to record, increase the input signal level. (Note: V_{RX} may be so small as to be unmeasurable. If this is the case, you may want to use approximately 10 mV as a value for V_{RX} .) The ratio is recorded as a negative dB. Compute the -dB of separation. _____ Technical data values range from -23 to -55 dB.

SUPERVISORY STATUS

Several supervisory controls are available:

- a) Hook-status output (HSO)
- b) Ring-sense current (RSO)
- c) Ring-trip detect (TSO)
- d) Hook-status threshold (HST), resistor R7, determines the value of the loop resistance and the ON-OFF hook-switching level.
- e) Since V_{OB} sets the voltage for R_{SI} , the loop feed source, V_{OB} determines the current level in the loop. Loop voltage is 4 V less than V_{OB} . (Note: Since V_{OB} is +5 V and not at ground, its usual connection, the loop feed voltage source is approximately $16\text{ V} + 5\text{ V} = 21\text{ V} - 4\text{ V} = 17\text{ V}$. The source resistances R_{SI} and T_{SI} are in the order of $600\ \Omega$ each.

11. Test the hook-status output (HSO). When an on hook condition exists, loop current is low, loop resistance is high, and HSO stays high (positive). When the hook is returned to the -15 V line via the 47 M resistor, the HSO performs a logic change from high to low. This action can be used to activate a dial tone or perform some other function. Record the voltage at TP9 when the loop is open _____ (open 1a). Off hook exists when loop current is flowing. Close switch 1a and again record TP9. _____

12. The ring-trip detect or tip sense (TSO) can be used to sense an ac ringing voltage present at

the tip. Close switch 3a, and open 1a, which returns the tip to ground. Between ground and the tip, connect a 5 or 6 Vac while observing the TSO at TP10. The TSO voltage with ringing is _____ V; and without ringing the TSO is _____ V.


Formal experimentation is hereby completed. For further information, the student should consult the technical data sheets supplied by Motorola, located in the Appendix. Additional measurements, such as band-pass, audio distortion, loop resistance vs. loop current, and the interfacing of supervisory controls with optoelectronic isolators can be investigated.

Attention is also called to the fact that in the interest of clarity, high-voltage protection diodes (bridge) and current-limiting resistors have been omitted from the circuitry. Although these protective devices are shown in the manufacturer's literature their function is external to the operation of the SLIC. However, they do serve to protect the SLIC from potential hazards.

Since a number of the measurements made in this section relate to the subscriber's loop, Experiment 7, which is concerned with the loop, should be reviewed.

Values shown are approximate. The quantities obtained may differ by ± 10 percent or more.

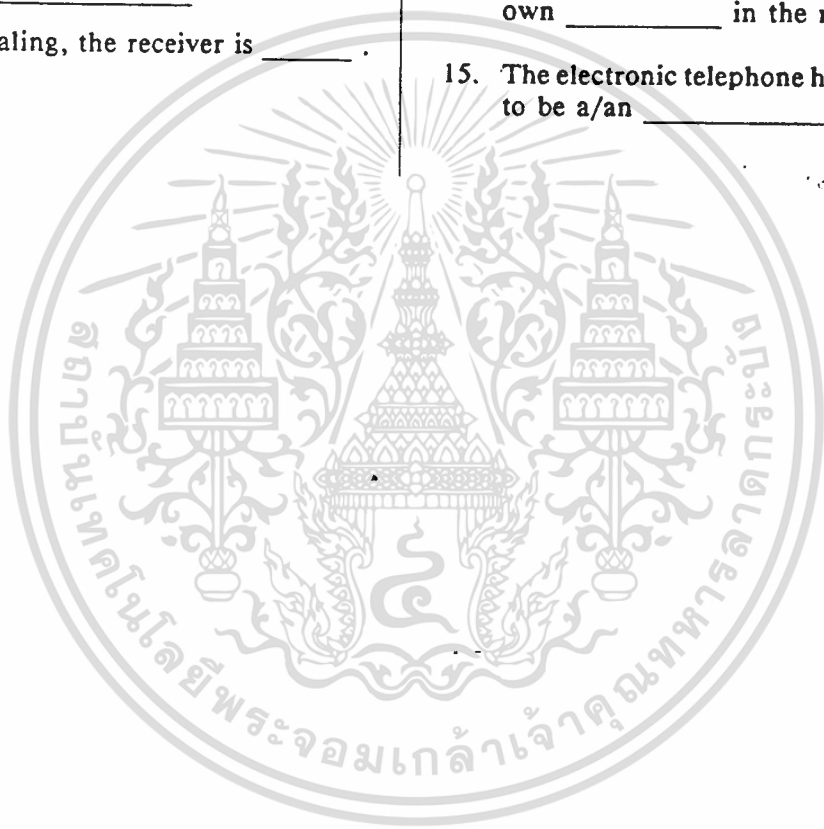1. The hybrid transformer converts a 2-wire line into a _____ wire line.
2. SLIC stands for: _____.
3. The central office dc supply voltage is generally _____ V.
4. The subscriber's loop current ranges from _____ to _____ mA.
5. In a subscriber's handset, the ringer is located _____ the hookswitch.
6. The voice sound in the receiver is reduced by the cancellation of coil _____.
7. The transmitter requires a 2-wire line separate from the _____.
8. During pulse dialing, the receiver is _____.
9. Overvoltage protection is provided by input _____ and _____.
10. Line-sensing circuitry detects whether the hookswitch is _____.
11. In speech circuit IC's, the carbon microphone is replaced by the _____ or _____ microphone.
12. Speech circuits derive their operating power from the _____.
13. Monolithic speech circuits operate in the: a) 2-4, b) 5-8, c) 10-12, d) 48-60 V range.
14. The sidetone allows the speaker to hear his/her own _____ in the receiver.
15. The electronic telephone handset is considered to be a/an _____ terminal.



เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆ ทั้งสิ้น ลึกทั้งห้าปีให้ตัดแปลงเนื้อหา และต้องอ้างถึงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

1. Sine wave output; unity gain (0.9V)
2. It decreases
3. Unity or less, depends on side tone control. Feeding R_x with 1 mv sine wave at 1 kHz, V_{out} at TP1 was approximately 0.4 V. Signal loss is about 8 dB.
4. Static voltage provided in tests with off to on hook positions (open or closed switch 1a).

<u>Pin</u>		<u>Pin V</u>	
ON	OFF	ON	OFF
1. + 4.98	+ 4.98	10. - 16	- 16
2. + 4.58	+ 4.98	11. + 1.35	- 15.6
3. + 3.37	+ 4.98	12. + 2.95	0
4. + 3	+ 3.79	13. - 0.8	- 15.3
5. - 6.20	- 15.6	14. + 4	- 13.4
6. - 14	- 14.6	15. + 4.98	+ 4.98
7. - 14.4	- 16	16. - 2.83	+ 3.21
8. - 15.6	- 16	17. + 0.2	+ 3.06
9. - 16	- 16	18. + 4.98	+ 4.98

Gain is unity in both directions.

5. $TP4 = 1.4 V_{PP}$
 $V_{TX} = .1 V_{PP}$
 $20 \log 0.1/1.4 = -24.7 \text{ dB}$
 $\text{dB} = -24.7$
6. $CMRR = -23 \text{ dB}$. Since the amplifier has unity gain, $CMRR = CMR$
7. Yes
8. $i_1 = i_2 = 18 \text{ mA}$ (Appendix resistance tolerance)
9. CMR would decrease
10. $V_{TX} = 1.2 V_{PP}$
 $V_{RX} = 10 \text{ mV}$
11. On hook, $TP9 = 12.84$;
 Off hook, $TP9 = +4.33$
12. Ringing $TSO = +2.7 \text{ V}$;
 With no ring, $TSO = -14.7 \text{ V}$

1. Four
2. Subscriber's loop interface circuit or card.
3. -48 V
4. 20 to 120 mA
5. In front of hook switch, parallel to the line
6. Voltage
7. Receiver
8. Shorted or muted
9. Rectifiers and back-to-back diodes
10. On or off
11. Electret or dynamic
12. Loop lines
13. 2-4 V range
14. Voice
15. Active

ขอบเขตของการศึกษา

ทำการศึกษาการเปลี่ยนสัญญาณแอนะล็อกให้อยู่ในรูปของรหัสดิจิทัล โดยใช้อุปกรณ์ที่เป็นทั้ง CODER และ DECODER ที่เรียกว่า CODEC อุปกรณ์ตัวนี้ถูกออกแบบมาโดยเฉพาะเพื่อใช้กับ โทรศัพท์ในระบบ ดิจิตอล

วัตถุประสงค์

หลังจากได้ทำการศึกษา, ทดลองให้ห้องปฏิบัติการและทำการประเมินผลแล้ว ผู้ทำการศึกษา จะมีความสามารถที่จะ

1. อธิบายถึงการเปลี่ยนสัญญาณเสียงโทรศัพท์ให้อยู่ในรูปรหัสดิจิทัลได้อย่างไร
2. เขียน BLOCK DIAGRAM ซึ่งแสดงถึง ENCODER ของ CODEC IC
3. บอกถึงประโยชน์ที่ได้จากการใช้ PCM เทียบกับ MODULATION แบบอื่น ๆ

PLUSE-CODE MODULATION และวงจรที่เกี่ยวข้องถูกนำมาใช้อย่างแพร่หลายกับ โทรศัพท์ ที่มีเสียง PCM และ DELTA MODULATION ยังนำมาใช้การสังเคราะห์เสียงด้วย FILTER COMPANDER และ ENCODER แบบพิเศษ ซึ่งคล้ายคลึงกันในเรื่องการออกแบบถูกนำมาใช้งานทั้งสองอย่าง ด้วยเหตุนี้อุปกรณ์ CODER จึงถูกนำมาใช้ในการทดลองหลายแบบ

ในการทดลองนี้ ระบบ CODER ที่สมบูรณ์จะประกอบไปด้วย IC หลายตัวแทนที่จะเป็นตัว เดียวซึ่งประกอบไปด้วยฟังก์ชันหลายอย่าง โดยการนำ IC หลายตัว แต่ละส่วนของระบบ CODEC ก็สามารถที่จะถูกค้นคว้าได้โดยตลอด วงจร CODEC มีที่ให้อยู่ใน ศูนย์ โทรศัพท์

AUTOMATIC BRANCH EXCHANGE (PABX) ส่วนต่อโทรศัพท์แบบอัตโนมัติในส่วนของ ผู้ให้บริการ, และในโทรศัพท์มือถือ

บทนำเกี่ยวกับ PCM CODEC

ก่อนที่จะเริ่มต้นในรายละเอียดเกี่ยวกับ PLUS CODE MODULATION CODER-DECODER, (PCM CODEC) มีความจำเป็นอย่างยิ่งในการที่จะดำเนินธรรมชาติของการสื่อสารด้วยความถี่ ของเสียงโดยเฉพาะอย่างยิ่งในเครือข่ายโทรศัพท์แบบดิจิตอล ภายใน เครือข่ายนี้วางอยู่บน การใช้งานขั้นมูลฐานของ PCM CODEC โดยพื้นฐานแล้ว เครือข่าย โทรศัพท์แบบดิจิตอลใช้การ SWITCHING ที่เหมาะสม คอมพิวเตอร์แบบ ดิจิตอลมากกว่า, เครือข่ายการสื่อสารทางโทรศัพท์ดิจิตอลลวจิตความเร็วสูง, หน่วยการคำนวณทางคณิตศาสตร์, การใช้งานอย่างกว้างขวางของหน่วยความจำแบบดิจิตอล และอื่น ๆ มีความสำคัญต่อโทรศัพท์ แบบดิจิตอล แต่ความสำเร็จของ ทางดิจิตอล ในการ SWITCHING และ TRANSMITTING สัญญาณเสียงจะขึ้นอยู่กับ ความสามารถที่จะใช้งานได้อย่างมีประสิทธิภาพและผลกระทบในเรื่อง ราคาของ ANALOG TO DIGITAL และ DIGITAL TO ANALOG อินเทอร์เฟส ถ้าไม่มี

เครือข่าย โทรทัศน์ในการแลกเปลี่ยนข่าวสารก็ยังคงต้องมีอยู่อย่างน้อยเป็นบางส่วนในรูปเครือข่ายแบบอนาล็อก PCM ไม่ได้ใช้ในทางการค้าจนกระทั่งในปี 1950 ถึงแม้ว่าจะได้รับสิทธิบัตรในฝรั่งเศสในปี 1937 โดย ALEX H. REEVES. ในขณะนั้น ในระบบของเบล ใช้ PCM ในระบบ TRANSMISSION ซึ่งถูกออกแบบเพื่อความสามารถในการ CARRY ข่าวสารของสายเคเบิลแบบ SHORT-HAUL เพื่อการใช้งานในกรณีที่การทำงานของ FDM (FREQUENCY-DIVISION MULTIPLEXING) ไม่ถูกต้องตัวอย่างเช่น ช่วงคลื่นเสียงที่มีช่วงจำกัดที่ 4 KHz ถูก CODE ให้เป็น DIGITAL SIGNAL ซึ่งถูกทวิคูณด้วยสัญญาณที่เหมือนกันทุกประการจาก 23 CHANNEL และถูกส่ง ผ่านทางสายเคเบิลคู่แบบ SINGLE-TRANSMISSION ไปยังผู้รับปลายทาง การติดต่อระหว่างกันเกิดขึ้น และการทำให้การสนทนาเสร็จ สมบูรณ์ได้วงจรที่สมมาตรกันได้ถูกจัดวางไว้ในทิศทางตรงกันข้ามเพื่อให้เกิดทางสื่อสารทางเสียงระบบนี้เรียกว่า "CHANNEL BANK" และถูกเรียกว่า ระบบ "D1" ซึ่งใช้กับสายเคเบิลที่ถูก เรียกว่า "T1" ทางปลายของผู้ใช้. ระบบ D1 CHANNEL-BANK เป็นแบบ 24 VOICE CHANNEL ที่แต่ละ ปลายของ T1 ต้องการ ความดูแลจากผู้ใช้เพียงเล็กน้อย อันที่จริงแล้วการทำงานแบบ SWITCHING ที่ไม่อาจเห็น ได้ชัดต่ออยู่กับเครื่องรับโทรทัศน์ ที่ต่อกับศูนย์ผ่าน D1 CHANNEL BANK บ่อยครั้งที่ผู้ใช้ไม่ รู้ว่าทางศูนย์โทรทัศน์ได้ให้บริการอะไรบ้าง ระบบ D1 และระบบที่ ตามมาจนถึง D4 ก็ยังคงเป็นระบบ TRANSMISSION ที่ใช้ DIGITAL CODING และระบบ TIME-DIVISION-MULTIPLEXING ในการเพิ่มความสามารถของ SHORT-HAULCALL HANDLING ประโยชน์ที่ได้รับจากการนำ PC มาประยุกต์ใช้งานนั้นยังไม่เป็นที่แพร่หลายจึงทำให้การนำ ของ PCM ในการใช้งานในเรื่อง LONG-HAUL TRANSMISSION, NOISE-FREE SIGNAL มาแทน ELECTROMECHANISM CIRCUIT ไม่เคยประสบความสำเร็จ อย่างสมบูรณ์ อันเนื่องมาจากค่าใช้จ่ายมากกว่าเมื่อพิจารณาในเรื่องราคาแล้วประโยชน์ที่จะได้รับจากการใช้ PCM ยังไม่มีการรับประกัน ถึงอย่างไรก็ตามแนวโน้มก็เริ่มมีการเปลี่ยนแปลงการเริ่มต้น ทำ ความรู้จักกับ CODEC IC เพิ่งจะเป็นการเริ่มต้น SILICONIZATION โทรทัศน์แบบ DIGITAL การประยุกต์ DIGITAL กับประโยชน์ที่มากมายของโทรทัศน์แบบ PCM ซึ่งนำ เอา CODEC มาใช้ในทุกระยะเครือข่าย TELECOMMUNICATION ทำให้อุปกรณ์ CODEC มี ค่าอย่าง เห็นได้ชัด

โทรทัศน์แบบ DIGITAL

ถึงแม้ว่าระบบเครือข่ายโทรทัศน์แบบ DIGITAL จะสามารถจัดวางได้หลายวิธี แตกต่างกัน ก็ตาม ความต้องการแบบพื้นฐานของวิธีการใดก็ตาม คือการเปลี่ยนสัญญาณที่เกิดขึ้นครั้งแรกให้อยู่ในรูปของ DISCRETE TIME SAMPLE เพื่อที่จะเพิ่ม CHANNEL CAPACITY ของ อุปกรณ์ TRANSMISSION SAMPLE เหล่านี้สามารถทำให้อยู่ในรูป MULTIPLEX ได้ โดยเพิ่ม CAPACITY ในการรับด้วยการใช้วิธี MULTIPLEXING โดยการนำเอา DIGITAL รหัส ไม่ว่ากรณีใดๆทั้งสิ้น อีกทั้งห้ามมิให้ตัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

PLUSE ซึ่ง สร้างเพิ่มขึ้นได้อย่างง่าย ๆ ด้วยวิธีการนี้ มาทำให้แน่ใจว่า ต้นกำเนิดของ สัญญาณเสียงจะไม่ เสียหายไปเนื่องจากการ DEGRADATION เมื่อถูกเปลี่ยนไปยังระบบอื่น ที่มีความแตกต่างกันถึงแม้ว่า TIME SAMPLING และ DIGITAL ENCODING เพียงจะถูกนำมาใช้เพียงเพื่อวัตถุประสงค์ ส่งค้ในการเชื่อมต่อโดยเฉพาะ MULTIPLEXING ก็สามารภที่จะนำมาใช้งานได้ตามจุดต่าง ๆ ภายในเครือข่าย ในระบบที่ใช้ CODEC ร่วมกัน ขั้นตอนแรก ของขบวนการ MULTIPLEXING ก็คือการเปลี่ยนสัญญาณ ANALOG ไปอยู่ในรูปของ PLUSE-MODULATION ที่เลือกแล้วอย่าง เช่น PLUSE-AMPLITUDE, PLUSE-WIDTH, หรือ PLUSE-POSITION MODULATION (PAM, PWM หรือ PPM) FILTERED, COMPANDED และ SAMPLED SIGNAL จะถูกเปลี่ยน โดย CODEC ไปเป็นสัญญาณดิจิตอล แบบ 8 บิต ส่วนที่สองของ IC นี้จะทำการ DECODE สัญญาเหล่านี้ไปเป็นสัญญาณ อนาลอก OUTPUT จาก ENCODER หลายตัวสามารถทำให้เป็นแบบ TIME SHARE ได้ TIME SAMPLE ของ 24 หรือ 30 CHANNEL จะถูก MULTIPLEX เข้าด้วยกันในสาย แบบเดี่ยวหรือ HIGHWAY และถูกส่งผ่านไปยัง SYNCHRONIZED RECEIVING CODEC เพื่อทำการ DECODE ก่อนที่จะทำการ DIGITAL MULTIPLEXING กับ VOICE CHANNEL อื่น ๆ ที่เหมือนกัน VOICE-BAND-LIMITED SIGNAL อาจจะเป็น TIME SAMPLE และถูกเปลี่ยนโดยตรงไป เป็น DIGITAL SIGNAL การจัดวางแบบนี้ทำให้ไม่ต้องใช้ เทคนิคของ PLUSE-MODULATION MULTIPLEXING ซึ่งบ่อยครั้งที่มีปัญหา และ ยอมให้มีความยืดหยุ่นในการ INTERFACING แบบ DIRECT กับทั้ง VOICE และ DATA CHANNELS ภายใน DIGITAL NET WORK เดียวกัน ใน การเลือกการจัดเรียงแบบ CODEC แนวความคิดที่ใช้ TIME SAMPLE เป็นตัวแทนของ ORIGINAL SIGNAL จึงเป็นกฎพื้นฐานของโทรศัพท์แบบ DIGITAL ด้วยวิธีการ SAMPLING นี้จะยอมให้ CONTINUOUS ANALOG SIGNAL เปลี่ยนไปเป็น DIGITAL และถูก MULTIPLEX เป็น TIME-DIVISION ใน MUTI-CHANNEL TRANSMISSION AND- SWITCHING HIGHWAY

อาจกล่าวอย่างง่าย ๆ ได้ว่า, BAND-LIMITED ANALOG SIGNAL ที่เป็น TIME SAMPLE ที่ SAMPLING RATE สูงมากกว่า ๆ จะให้ผลเป็น SPACED SAMPLE แบบธรรมดา ที่ประกอบไปด้วยข้อมูลทั้งหมดของ ORIGINAL SIGNAL มันมีความสำคัญที่จะ BAND-LIMIT สัญญาณ INPUT เพราะว่า TIME SAMPLING จะเป็นสาเหตุของ ALIASING การถูกรบกวน เกิดจาก EXTRANEOUS HIGH FREQUENCIES DESCENDING เข้าไปใน AUDIO BAND การรบกวน เหล่านี้เกิดขึ้นจาก SWITCHED CAPACITOR FILTERS ในระบบโทรศัพท์, ย่านความถี่ ที่สนใจคือ 300 Hz - 3.4 KHz เพื่อที่จะให้ เกิดการส่งสัญญาณโทรศัพท์แบบดิจิตอลได้ทั่วโลกจะใช้ 8 KHz SAMPLING FREQUENCY ตามข้อตกลงระหว่างประเทศ ทำให้ กลุ่มของ VOICE SIGNAL 24-30 สัญญาณจะไปใช้ FRAME ในช่วงคาบ 125 MICROSCEONDS ถึงแม้ว่า TIME-SAMPLE SIGNAL จะต้องที่จะ ไม่ MULTIPLEX กับสัญญาณที่คล้ายกัน จะเป็นการเหมาะที่จะพิจารณาสัญญาณในรูปแบบของ

CODEC ในการ ENCODING ANALOG SIGNAL ไปเป็น DIGITAL-PCM ก่อนที่จะทำการ TIME-DIVISION MULTIPLEXING (TDM)

PLUSE-CODE MODULATION

ระบบ PCM นี้เป็น 1 ใน 2 ของการส่งผ่านข้อมูล แบบไม่ LINEAR โดยจะ เปลี่ยนสัญญาณ ANALOG ให้เป็นสัญญาณดิจิทัล 8 BIT

PCM TRANSMISSION

ความเร็วในกระแสส่งผ่านข้อมูลของ PCM จะถูกควบคุมโดย 2 ส่วนคือ SAMPLING PERIOD และ SAMPLING TIME ความถี่ของการส่งข้อมูลหาได้จาก BIT WIDTH (BITW)


$$BIT W = \text{FRAME TIME} (1/8 K)$$

$$\begin{aligned} & \text{BITS} \\ & = \frac{125 \times 10^{-6}}{8} \\ & = 15.625 \times 10^{-6} \end{aligned}$$

$$\begin{aligned} \text{THE TRANSMIT FREQUENCY (F}_t\text{)} &= 1 / \text{BIT W} \\ &= 1 / 15.6 \times 10^{-6} \end{aligned}$$

$$\text{TRANSMISSION FREQUENCY} = 64 \text{ KHz}$$

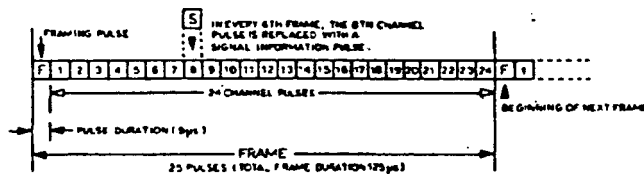รูปที่ 13-1 แสดงถึง ส่วนประกอบของ 1 MULTIPLEXED FRAME



The Framing of 24 Channels, with a Framing Pulse


FIGURE 13-1

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่นอนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆก็ตาม ลิขสิทธิ์เป็นของเจ้าของเอกสารฉบับนี้ และต้องอ้างถึงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

ในทุก ๆ 6 FRAME จะมี PULSE บวก INFORMATION อยู่ในลำดับที่ 8 ของ TIME SLOT เพราะฉะนั้นจึงใช้งานจริง ๆ เพียง 7 BIT แต่อย่างไรก็ตาม ใน 1 FRAME ก็จะมี 8 BIT ดังนั้นสัญญาณที่แตกต่างกันจะห่างกัน 6 FRAME เสมอ เช่น สัญญาณสายไม่ว่าง, สัญญาณ เสียงกระดิ่งดัง และสัญญาณการตรวจสอบ

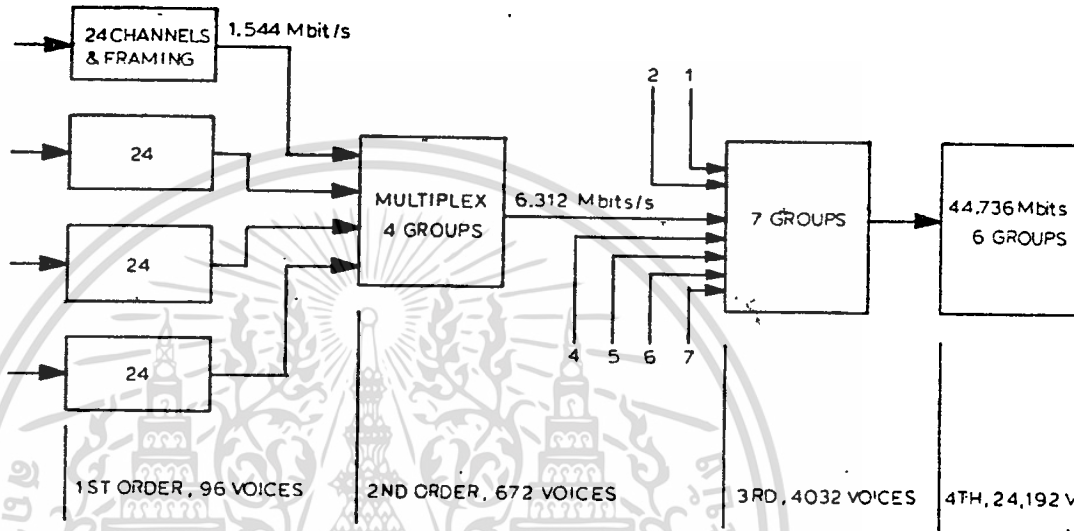
รูปที่ 13-2 แสดงถึงการส่งข้อมูลแบบ HIERARCHY โดยใช้ 24 CHANNELS MULTIPLEXER ORDER ยิ่งสูงขึ้นก็จำเป็นต้องใช้ CABLE ที่มีกระแสส่งผ่านให้ได้ตามต้องการ ดังนั้น FIBER OPTICS จึงมีความต้องการมากขึ้น



Hierarchy of PCM Multiplexing in the U.S.A.


FIGURE 13-2

BELL SYSTEM	BIT RATES	NUMBER OF VOICES
T1 SYSTEM	1.544 MBPS	96
T2 SYSTEM	6.312 MBPS	672
T3 SYSTEM	44.736 MBPS	4,032
T4 SYSTEM	274.176 MBPS	24,192

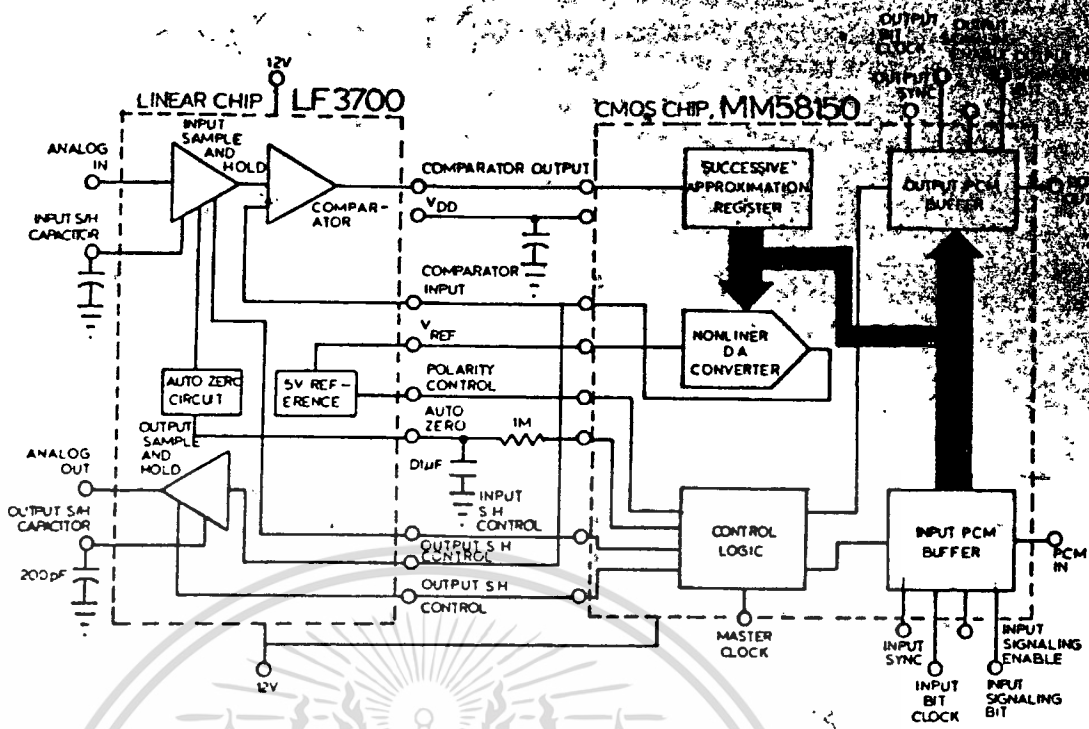


System (Mu-255 or A-law)

FIGURE 13-3

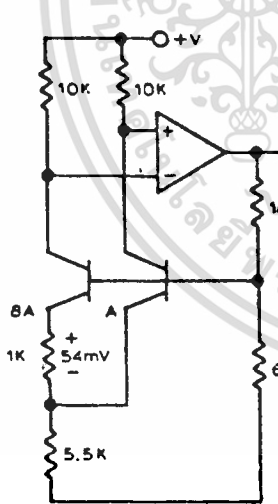

Voltage Reference

FIGURE 13-4

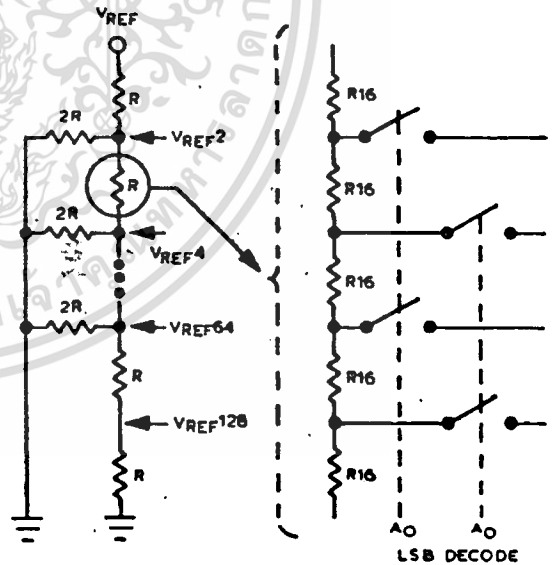

Digital/Analog Converter Using R/2R Ladder

FIGURE 13-5

ในระบบ PCM นี้แม้จะมีข้อดีมากมายแต่ก็ยังมีข้อเสียอยู่คือ การใช้ BAND PASS กว้างนั้นเอง การ MULTIPLEXING สัญญาณแบบนี้ถูกกระทำโดยวงจร TSAC (TIME SLOT ASSIGNER CIRCUIT) ซึ่งใช้ IC และสามารถ ASSIGNE ได้ถึง 64 SLOTS และยังสามารถใช้ MICROPROCESSER ควบคุมได้

THE PCM CODEC SYSTEM

รูป 13-3 แสดงให้เห็น CODEC SYSTEM ซึ่งใช้ IC ของ NS ซึ่งมี 2 ระบบ คือ MU-255 สำหรับ USA และ A-LOW สำหรับใช้ใน EUROPE ทั้ง 2 SYSTEM นี้ ใช้ LINEAR และ DIGITAL CHIP เหมือนกันทั้งยังต้องมี FILTERS ที่ I/P และ O/P ด้วย

ในส่วนของ LINEAR CHIP ประกอบไปด้วย I/P, O/P วงจร SAMPLE AND HOLD ซึ่งสามารถ SET "0" อัตโนมัติ, COMPARATOR และ VOLTAGE-REFERENCE SOURCE สำหรับ วงจร D/A

ในส่วนของ DIGITAL CHIP ประกอบด้วย SAR, DAC, CONTROL LOGIC, HIGH-SPEED I/P O/P PCM BUFFERS

การ SAMPLING แบบนี้จะทำให้เกิด "ALIASING" ซึ่งเป็นความถี่สูงและเข้าไปอยู่ใน VOICE PASS BAND ซึ่งเป็นย่านความถี่ต่ำ 4 KHZ เพราะฉะนั้นจึงต้องใช้ FILTERS ช่วย วงจร AUTO-ZERO มีไว้เพื่อให้แน่ใจว่า LSB ที่ I/P อยู่ใน LIMIT เพราะถ้าไม่มีจะทำให้เกิดสัญญาณรบกวนขึ้นส่วนใน O/P จะใช้วงจร LPF ที่วงจร CODEC แทนเทคนิคของการทำ AUTO-ZERO คือใช้ AVERAGE TIME ของ PCM-CODE SIGN BIT โดยใน 1 TOGGLING แบ่งเป็น 100 ถึง 1000 US และการปรับปรุ้ง DC OFFSET ของ SAMPLE-AND-HOLD เพื่อลดการไขว้ปรุ้ง DC DETECT ให้น้อยที่สุด. VOLTAGE REFERENCE คือ BAND-GAP 2 ขั้ว (ดูรูป 13-4) ซึ่งจะถูปรับโดย VOLTAGE ตกร่วม BASE-EMITTER

MATERIALS REQUIRED

SIP397-3 and 300 B or 300 PSB.

Reminder: When using SIP397-3 with the Master Builder or the Power Supply Base be sure to set all supply voltages to V_{max} . The ringer circuit requires this maximum voltage.

TEST AND MEASUREMENTS

CODEC

In the following experimental tests, the MC14402 Codec IC will be evaluated. The frequency responses of the two intrinsic voice filters and the encoders will be generally evaluated.

EXPERIMENTAL PROCEDURES

1. Power up the 397-3 panel (Sections H, J, K, L) turning both adjustable supply voltages to maximum. Then refer to Figure 13-11. This circuit includes a clock, a CODEC, and a TSAC. Begin by setting the switches as follows:

SWITCH	OPEN	CLOSE
A	1, 4	2, 3
B	2, 3, 4	1
C	1, 2, 3, 4	
D	1, 2, 3	4
E	1, 3	2, 4

Adjust the clock frequency while observing TP19 with a counter. Turn R36 to obtain a frequency of 1.2 to 1.5 MHz.

2. Inject a $3 V_{pp}$ 1 kHz sine wave into TP15 and view the output at TP16. Connect channel A to V_{IN} and connect channel B to V_{OUT} . This can be done by using two BNC cables. Record the wave shape and amplitude at TP15 and TP16.

Do you observe a chopping in the output signal?

(Note: An external sync may be required. The output can be made to vary as a function of R36. If signal output at TP16 is not a good sine wave try adjusting R36 for best sine wave.)

SIGNAL GAIN

3. How much closed-loop gain does the conversion circuit provide? $G =$ _____
What is the phase relationship between input and output? _____. The phase relationship between input and output is approximately zero, but this too is R36 dependent. Try adjusting R36 slightly clockwise then counterclockwise. Observe phase shift.

4. The gain of the input OP AMP to the transmitter is controlled by the ratio of the feedback resistor between pins 7 and 8 (R21) and the $k\Omega$ input resistor R22. By closing switch 2e thereby reducing 20 $k\Omega$ to 10 $k\Omega$, the ratio becomes 1:1. Again measure the gain between the input (TP15) and the output (TP16).
Gain = _____

SIGNAL PHASE

5. The signal output at pin 3 (RxO) is out of phase with pin 5 (RxO). Open switch 2e and close switch 2f. With a dual-trace oscilloscope, compare the output of the two signals use external sync or external trigger. Source of external sync (trigger) may be either RxO (pin 3), RxO (pin 5), or TP15. Are they in-phase? _____

POWER DOWN

6. When not in use, the circuit can be powered down by a computer signal. Simulate the power down procedure by opening switch 3a (POWER DOWN). Does the output signal disappear? _____. Return the switch to the UP position (POWER UP).

7. Check the frequency response of the complete circuit. Vary the function generator's frequency and determine the 3 dB points.
 f_h _____ Hz, f_L _____ Hz.
8. Try to determine the dB/octave roll-off of the high end of the bandpass. _____

DIGITAL STREAM

9. The digital stream is observed at TP20. Close 3b and 4d, and open 1b. With the clock set at 2.04 MHz (or as close to it as possible, record the time between framing pulses; $t =$ _____ (determined by clock rate).

stream. (If you external trig. on of $\kappa 20$, you might get a stronger trace.) _____

11. Without changing any switches inject a 3 V_{pp} 1 kHz signal into TP15 and scope TP20. (Leave sweep at 1 μ Sec. Increase amplitude of generator monitoring the serial stream (TP20). Describe your observation. _____

NOTE: When evaluating the TSAC circuit, additional tests will be performed with this circuit. Leave all switches in their usual operating settings.

REVIEW QUESTIONS

1. A CODEC system requires the use of ADC and DAC circuits. True/False? _____
2. How many sample-and-hold circuits are generally used in a CODEC system? _____
3. PCM (the CODEC) produces a serial or a parallel output? _____
4. An "antialiasing" filter prevents _____
5. The filters used in modern CODEC systems are called _____
6. One frame of data, in the United States, contains _____ channels.
7. Frame synchronizing takes place prior to the _____ bit.
8. Signaling is inserted in the _____ time slot of every _____ frame.
9. In a digital system all noise is removed. True/False? _____
10. The sample rate is _____ the highest frequency in the analog bandpass.
11. In a 24-channel frame, with 8 bits per channel, the frame is transmitting _____ bits per second.
12. The time period of a frame is _____ microseconds.
13. The assigning of time slots for multiplexing is performed by a _____ chip.
14. A disadvantage of PCM is the additional _____ that it requires.
15. Although 8 kHz is being transmitted on a line, 128 kHz is required for synchronization. What type of chip is suggested to acquire the higher rate of 128 kHz? _____

EXPERIMENTAL ANSWERS

1. Procedural
2. TP15 sine wave, $3 V_{pp}$; TP16 sine wave, approximately $5.6 V_{pp}$; yes.
3. $G = -6$ dB; phase depends on clock frequency.
4. Gain is 1. Gain of 1 equals 0 dB.
5. No, they are approximately 180° out of phase and are essentially equal in amplitude.
6. Yes
7. $f_h = 2.5$ kHz to 3.5 kHz, (depending on clock frequency); $f_L = 100$ to 300 Hz
8. Approximately 30-40 dB per octave
9. $125 \mu s = 8$ kHz
10. 3.3 to 3.9 μs (depends on signal present)
11. Pulses vary in width.

ANSWERS TO REVIEW QUESTIONS

1. True
2. One
3. Serial
4. Foldover, interferences from higher frequencies.
5. Switched-capacitor filters
6. 24
7. First
8. Eighth, sixth
9. False; noise results from A/D conversion.
10. Twice
11. 193 ($192 + 1$)
12. 125
13. TSAC
14. Bandwidth
15. PLL

DELTA MODULATION


DELTA MODULATION คืออีกวิธีหนึ่ง ของการถอดรหัส และการเข้ารหัสโดยนำสัญญาณ ANALOG มาทำเป็น BIT ได้โดยตรงระบบ DM นี้เครื่องกำเนิด PULSE จะกำเนิด PULSE ที่มีขนาดและขั้วแน่นอน เมื่อสัญญาณ ANALOG เข้ามาในวงจร DM สัญญาณ ANALOG จะเปรียบเทียบกับ PULSE ที่กำเนิดมา ถ้าผลต่างเป็น บวก จะให้ BIT 1 และถ้าเป็น ลบ จะให้ BIT 2

ข้อจำกัดของ ระบบ DELTA MODULATION คือ

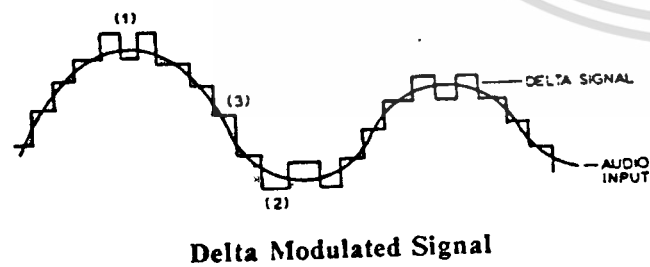1. อัตราการ SAMPLING เพียง 3-4 ครั้งเท่านั้น
2. สัญญาณ ANALOG ไม่ควรเปลี่ยนแปลงขนาดอย่างรวดเร็วเพราะจะให้ระบบ DM ไม่สามารถสร้าง PULSE ไล่ทัน
3. ในเมื่อ DM ขึ้นอยู่กับ BIT สุดท้าย ดังนั้น ระบบจะทำงานได้ดี เมื่อสัญญาณ หนึ่งเดียวเริ่มถูกกระทำ

รูปที่ 14-3 คือการเกิดภาวะ SLOPE OVERLOAD คือสัญญาณ ANALOG เปลี่ยนขนาดเร็วเกินไป การที่ระบบ DM จะสร้าง PULSE ไล่ทัน

เพื่อจัดการเกิดการ SLOPE OVERLOAD ให้สร้างระบบ DM ที่สามารถปรับขนาดขั้นบันได (STEP SIZE) ได้แทนที่จะเป็น ขั้นบันไดคงที่



Delta Modulated Signal

FIGURE 14-2



Slope Overload

FIGURE 14-3

ในรูป 14-8 แสดงวงจร ของ MC 3417 หรือ 3418 CUSD ENCODER IC M
3417 ใช้สำหรับการติดต่อสื่อสาร และ MC 3418 ใช้สำหรับ โทรศัพท์ในเชิงพาณิชย์ มีข้อควรร
7 ข้อ สำหรับ การออกแบบ CODEC คือ

1. การเลือก อัตรา CLOCK
2. การเลือก จำนวน BITS ของ SHIFT REGISTER
3. การเลือก LOOP GAIN
4. การเลือก STEP SIZE ต่ำสุด
5. การออกแบบระบบ FILTER
6. การออกแบบ การส่งผ่านแบบ SYLLABIC-FILTER
7. การออกแบบ LOW-PASS FILTER ที่เครื่องรับ


ในรูป 14-8 แสดงถึง วงจรพื้นฐานของ CVSD ในหลาย ๆ หน้าที่



สรุป

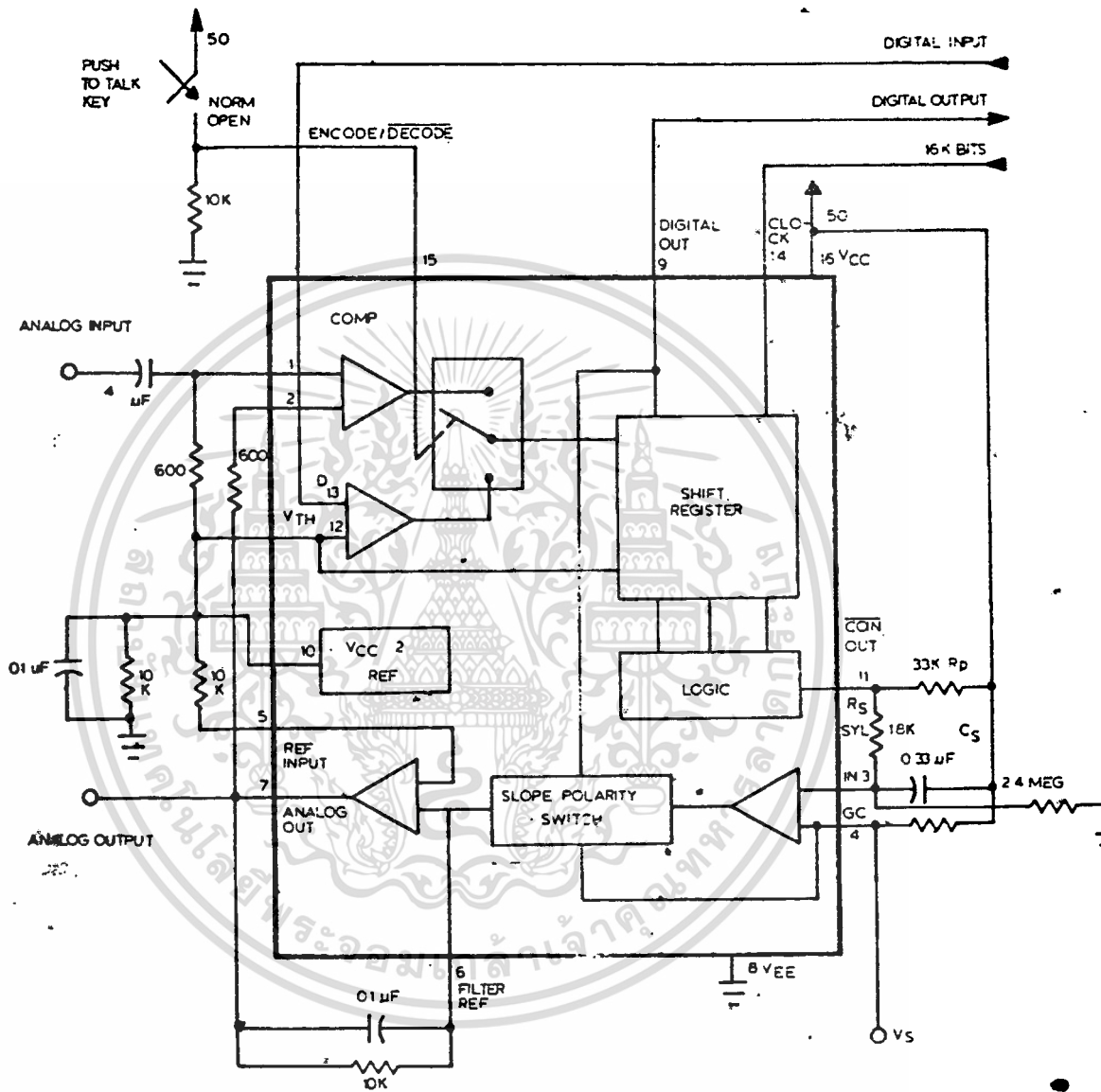1. ใน DELTA MODULATION ค่าจริง ๆ ของ SIGNAL VOLTAGE ไม่ได้ถูกเข้ารหัสความแตกต่างของสัญญาณเท่านั้น ที่ถูกนำมาเข้ารหัส
2. COMPANDER คือ ตัวอัดขยายซึ่งช่วงลระดับของสัญญาณ
3. OUTPUT ของ DELTA MODULATION คือ PLUSE แบบ อนกรม
4. SLOPE OVERLOAD เกิดเมื่อ อัตราส่วนการเข้ารหัสไม่สัมพันธ์กัน
5. ในเสียงพูดมีระดับเสียงซึ่งสามารถใช้เข้ารหัสได้
6. CVSD อ้างถึง อุปกรณ์ VARIABLE-STOP DELTA MODULATION





MC3417, Single Pole Compander and Single Integrator, 16 KHz Simplex CVSD Codec

FIGURE 14-8

Laboratory Experimentation

MATERIALS REQUIRED

SIP397-4 and 300 B or 300 PSB.

TEST AND MEASUREMENTS

In the experimentation, one CVSD device will be used as an encoder and another, similar device will decode the digitized signal. The circuits are evaluated in terms of their general operation, the gain of the system, frequency response, effects of clock frequency on performance, and granular noise. Filters are included.

EXPERIMENTAL PROCEDURES

The various test points referred to in this experiment are to be found on "Section C, Delta Modulation" on the signal converters SIP397-4 panel.

1. Power up the prewired circuit 397-4 (Section C) and refer to Figure 14-9. Make sure that you use the proper supply voltage as indicated on the lower left of panel. Set the clock frequency in the range of 32 kHz. Close 4b, and connect the oscilloscope or frequency meter to TP4 (pin 14). Adjust R17.

OVERALL OPERATION

2. Observe how the systems function by feeding the input, TP1, with a 1 V_{pp} sine-wave signal set at 1 kHz. View the signal output at TP6, and compare it with the original signal at the input, TP1.

TP1 _____, TP6 _____

3. How much gain or loss is present? _____
4. What is the bandpass between the 3 dB points? _____ to _____
5. By observing the output at TP3 (Section C), note that the signal is digitized. Observe the output when no input signal is present at TP3. Explain: _____

6. Reconnect the signal source. Observe the effects of the receiver's filter by viewing TP6 (unfiltered wave) and TP8, the filtered output. TP6 _____, TP8 _____

EFFECTS OF THE CLOCK FREQUENCY

7. The higher the clock frequency, the higher the SQR. View the output at TP6 while reducing the clock rate toward 20 kHz. Describe what is observed. Use a 1 kHz signal input to TP1. _____

Increase the clock to above 50 kHz, and again observe the output signal.

8. Connect the output at TP6 to an audio amplifier and speaker. Listen to the 1 kHz signal as the clock rate is reduced. Does the noise level increase? _____

What is the lowest clock rate you would suggest using? _____

9. Is the noise level greater at 32 kHz than at 100 kHz? _____
10. Commercial telephones use clock rates of 32 kHz and up. Set the clock at 32 kHz, and listen to the audio output while the signal source is varied between 300 Hz and 4 kHz. Describe the effects you observe. _____

11. Why shouldn't a clock rate of 200 kHz to 1 MHz be used on telephone lines? _____


12. When no audio signal is present at TP1, what digital sequence is transmitted (scope TP3)? _____

13. Is the transmitted data framed or unframed? _____

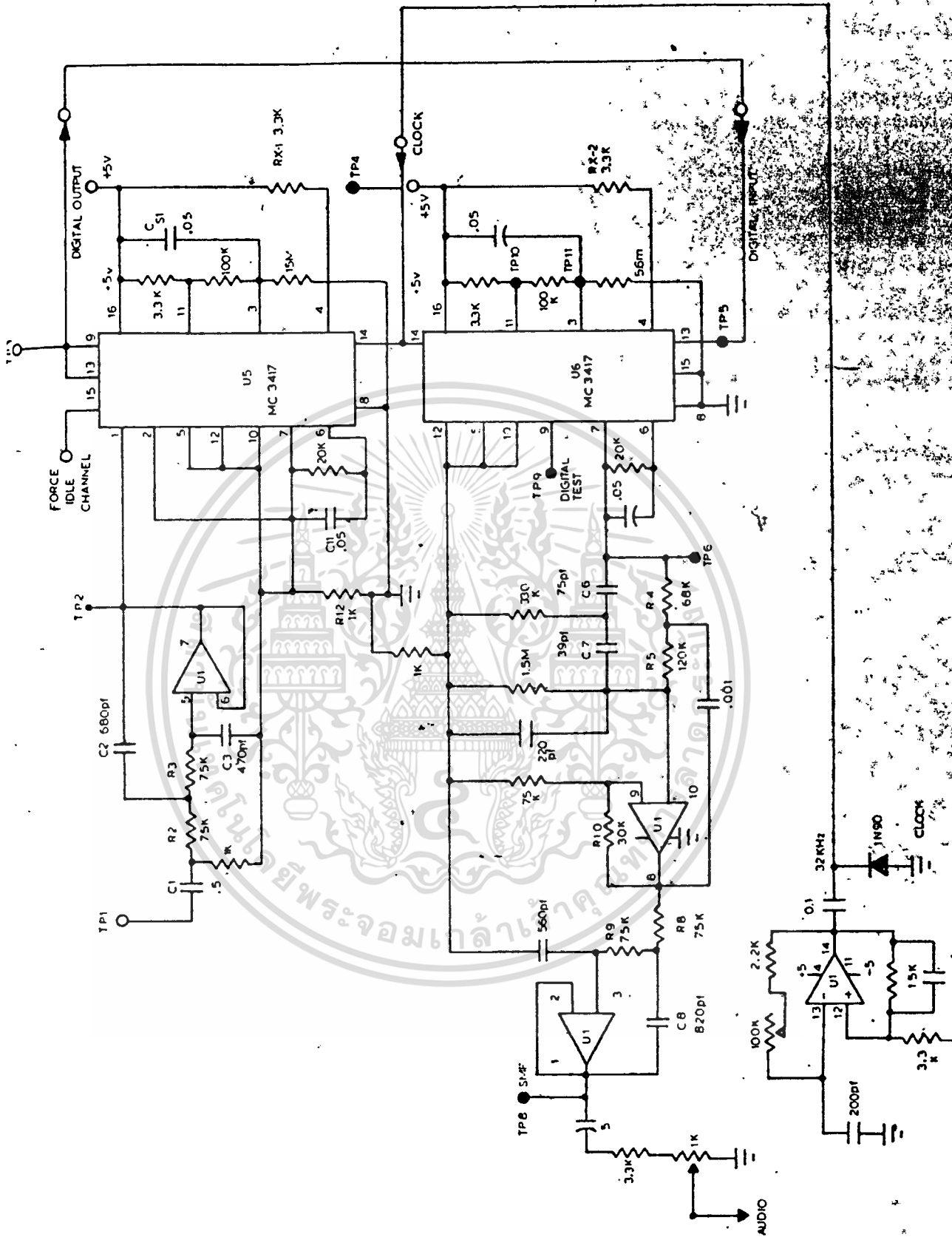14. View TP6. If the input audio to TP1 is decreased toward zero, does the output follow? _____

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆทั้งสิ้น อีกทั้งห้ามมิให้ดัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้



Delta Modulation/Demodulation

FIGURE 14-9

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆก็ตาม ลิขสิทธิ์นี้เป็นของเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

MINIMUM STEP SIZE

The quality of the transmitted signal depends upon the level of the signal, the noise level, and the alternate transmission of 1's and 0's. When the clock only (no signal) is viewed at TP6, the digital output will appear as a series of small triangles whose amplitude should be a minimum of 20 mV. Mismatches within the receiving IC, plus external component values, can alter the step size and hence the output's wave shape. The MC3417 is rated at 20 mV with a 16 kHz clock rate. The step size is set by the resistor between TP11 and ground. When the resistor is *reduced in value*, the step size is increased and the output becomes jumpy and distorted.

15. View TP6 when no signal input is present. Set the clock at 32 kHz. The triangular step amplitude is _____.
16. Feed into TP1 a 300 Hz signal of 60-70 mV, and view the output at TP6. How much signal is present? _____. Is the wave shape reasonably clean? _____.

17. Place a resistance decade box across the 5 M Ω resistor, TP10 to ground. How much voltage is present at TP6 (no signal)? _____. What happens to the output at TP6 when 300 Hz signal is inserted? _____.
18. Is the step size important in the reproduction of the signal? _____.
19. Try reducing the clock rate to 26 kHz and then to 20 kHz. Describe the effects. _____.
20. At higher clock rates, is the step size as much of a problem? _____. Increase the clock to 64 k and 100 kHz. Then observe the output at TP6 with a 300 Hz to 1 kHz signal present. Describe your observations. _____.

No experimentation is provided for in the areas of filter design and system gain. For additional design data, reference should be made to the technical data on the Motorola MC3517.

REVIEW QUESTIONS

1. In delta modulation, the digital output reflects the _____ of the input signal and its _____ from the last bit.
2. "Slope overload" occurs when the digital conversion cannot keep up with the _____.
3. The comparator of the encoder compares the _____ polarity (sign) with the _____ output.
4. When an analog signal is not present, the digital output consists of _____.
5. The sampling rate of a delta modulator is _____ higher than the upper audio band-pass.
6. PCM uses a sampling rate which is in the range of _____ the upper audio bandpass.
7. Delta modulation is used since it conserves the number of _____ in the output during analog conversion and transmission.
8. SQR refers to the _____.
9. In linear delta modulation, each step is the same _____.
10. Companding _____ the amplitude of the signal. In CVSD systems, the _____ of the step is also controlled by the amplitude of the signal input.
11. In speech, vowels are _____ in frequency than consonants.
12. Cyclic tones produced by men require a _____ period than is required by women.
13. Voice sounds are produced by the _____.
14. Cyclic resonant tones are called _____.
15. The three types of sounds produced are 1. _____, 2. _____, and 3. _____.
16. CVSD modulators require that the analog signal be frequency limited. True/False? _____.
17. Companding is not used in CVSD encoders. True/False? _____.
18. The dynamic range of the CVSD is increased by controlling the gain of the _____.
19. When no analog input signal is present, the CVSD produces noise known as _____ noise.
20. To form a duplex system, _____ delta CODEC IC's are required.

EXPERIMENTAL ANSWERS

1. Procedural

2. $TP1 = 1 V_{PP}$



$TP2 = 1 V_{PP}$




3. Unity

4. 250 to 3.4 kHz

5. At TP3, square waves exist at approximately one-half the clock frequency. The amplitude is 5 V. With an audio input, the output contains square waves of different widths. Yes.

6. TP6,

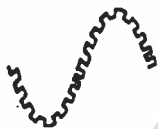

TP8



7. As the clock rate is lowered, the sine wave changes into a signal with rate pulses superimposed. As the clock frequency increases, the digitized sine wave is sampled more frequently and the wave shape shows fewer and fewer digitizing effects.

8. Yes; 15 kHz and up is adequate, but for fewer digitizing effects you might want to clock at 50 kHz or more.

9. Yes

10. The signal is present, but there is background noise. Wave shape and sound improves when

the audio signal is low (300 - 500 Hz). Deterioration occurs as audio signal goes towards 4 kHz.

11. The higher the clock rate, the more it costs to operate the telephone lines.

12. Hum modulated triangular wave at approximately 6-10 mV.

13. Unframed. Very simple method for data transfer.

14. Yes

15. 10 mV

16. 60 mV going in and out. Yes, but with delta steps.

17. With no input signal and with no shunt $V_{TP6} = 8$ mV triangle wave. With $1 M\Omega$ shunt $V_{TP6} = 200$ mV. As shunt goes towards zero ohms, V_{TP6} increases in magnitude to about 1.2 V.

18. Yes, smaller step size is desired.

19. The delta steps become fewer in number and greater in size. This causes more distortion in the output (TP6) waveform.

20. No, the higher the clock rate and the lower the input signal frequency, the better the output will be.

ANSWERS TO REVIEW QUESTIONS

1. Direction, difference

2. Analog input

3. Analog, integrator

4. 1's and 0's

5. 6-10 times

6. Twice

7. Bits

8. Signal-to-quantizing-noise ratio

9. Amplitude

10. Reduces, amplitude

11. Lower

12. Longer

13. Vocal cords

14. Formants

15. 1. formants, 2. fricatives, 3. plosives

16. True

17. False

18. Integrator

19. Granular

20. Two

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่าจะมีใครทั้งสิ้น อีกทั้งห้ามมิให้ดัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

ทั้งสัญญาณเสียงและข้อมูล COMPUTER จะต้องทำการเข้ารหัสก่อนส่งไปตามสายโทรศัพท์ เพื่อป้องกันการเกิด LOSS ของ DIGITAL PULSES และ SYNCHRONIZATION สาเหตุของการเกิด สัญญาณ LOSS ก็คือการใช้สายยาว ๆ ปกติในสายลวดธรรมดาทุก ๆ 1 MILE จะต้องใช้ตัว REPEATER 1 ตัว แต่สำหรับ FIBER OPTICS จากการทดลองของ BELL และ UNITED KINGDOM LAB สามารถที่จะส่งผ่านได้เกินกว่า 70 MILES โดยไม่ต้องมีตัว REPEATER


การส่งผ่านสัญญาณที่ได้ผลจะต้องทำดังนี้ คือ

1. เข้ารหัสข่าวสารโดยไม่มี ERROR
2. รักษาความสัมพันธ์ ของ PHASE ไม่ให้ SHIFT ออกไป
3. ต่อสัญญาณนาฬิกาเพื่อให้งานการทำงานเกิดขึ้นพร้อมกัน
4. ป้องกัน DC VOLTAGE ซึ่งเกิดจากการลดหรือเพิ่มระดับของ PULSE และ TRANSFORMER ไม่สามารถ COUPLE ได้

วิธีที่นิยมใช้ในการเข้ารหัส คือ PCM ซึ่งมีส่วนสำคัญ ดังนี้

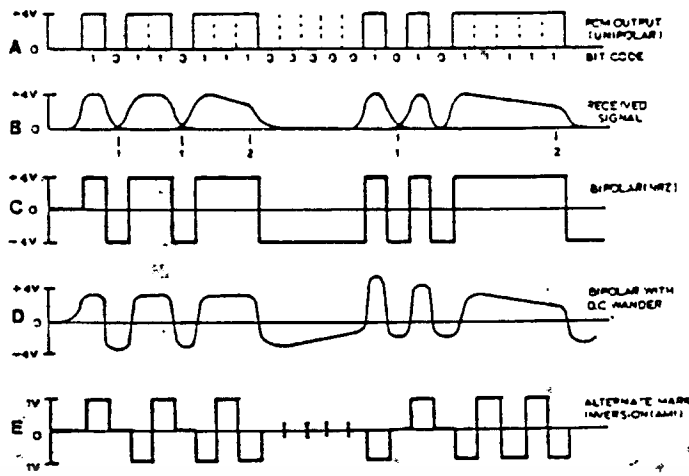1. CLOCK RATE
2. FRAMING OF DATA
3. VARIATION IN SIGNAL LEVEL OF THE ORIGINAL SIGNAL, WHICH HAS BEEN COMPANDED
4. SUPERVISION INFORMATION
5. FRINGING DATA
6. OTHER HOUSEKEEPING DATA
7. RELATIONSHIP BETWEEN THE TRANSMITTING CHANNELS

ทั้งหมดนี้ขึ้นอยู่กับระดับของ TDM ซึ่งอาจเป็น 24 หรือ 32 CHANNELS หรือ มากกว่า 10,000 CHANNELS อย่างไรก็ตามถ้า FRAME เกิดการ LOST การแยก CHANNEL ถูกทำลายนั้นหมายถึงว่า การส่งผ่านสัญญาณที่เหลือใน ตัวมันเองทุก ๆ PULSE จะถูกแบ่งตำแหน่งเมื่อมาถึงเครื่องรับ



Encoding of Digital Pulses

FIGURE 15-1

รูป 15-1 (A) แสดงถึง BIT-CODE O/P จาก PCM ของ TDM O/P "1" คือ สัญญาณ PULSE 4 V ซึ่งรู้ค่าเวลาแน่นอนรวมอยู่ใน FRAME, "0" คือสัญญาณศูนย์ V ซึ่งใช้คำว่า RZ ในสัญญาณการเข้ารหัสซึ่งเริ่มจาก "0"

รูป 15-1 (B) แสดงถึงสัญญาณที่ผิดเพี้ยนไปก่อนที่จะถึง REPEATER หรือเครื่องรับปลายทาง จุด เลข 1 แรก และ เลข 1 ต่อมาแสดงให้เห็นการเกิด OVERLAP เนื่องจาก PHASE SHIFT

เพราะฉะนั้น ระดับความแตกต่างของ VOLTAGE ระหว่าง "1" กับ "0" จะมีน้อยลงซึ่งทำให้เกิดการ ERROR ได้ง่าย ๆ ในแต่ละจุดที่รูป 15-1 B อาจเกิดการผิดพลาดในระดับได้เพราะว่า ในแต่ละ PULSE มี SLOPE มากเกินไป จึงทำให้ ระดับ 0 จริง ๆ มีน้อย

ในรูป 15-1 (C) แสดงถึงวิธีการ NRZ โดยระดับ 1 จะเป็น + และระดับ 0 จะเป็นอย่างอื่นก็ตาม การเข้ารหัสแบบนี้จะไม่สามารถหยุด VOLTAGE DC ได้ในระดับที่เราต้องการ

ในรูป 15-1 แสดงถึงการใช้สัญญาณนาฬิกาเป็นตัววัด ความแตกต่างของ PULSE ระหว่าง 0 กับ 1 โดยวัดที่ช่วงเวลาระหว่าง PULSE

ในรูป 15-1 (E) เป็นวิธีการที่ได้รับความนิยมมาก เรียกว่า "ALTERNATE MARK INVERSION" (AMI) โดยแต่ละ PULSE "1" จะทำให้ระดับลดลงอยู่ประมาณระหว่าง + และ -1 V เมื่อ PULSE "1" เกิดขึ้น 2 PULSES ตามกันมา PULSE หนึ่งจะมาเป็น + PULSE หนึ่งจะเป็น - ซึ่งจะแสดง 0 ในพื้นที่ ที่ไม่มี PULSE ใน AMI เมื่อ PULSE ถูกรวมเข้าด้วยกัน ความต้องการ PASS-BAND ก็ลดลง เพราะ PULSE WIDTH ของแต่ละ PULSE ลดลง ความต้องการพลังงานก็ลดลงตามด้วยทำให้ไม่เกิด CROSSTALK ที่เครื่องรับ PULSE ที่เป็นคลื่นจะถูก RECTIFIED และ ทำให้เกิดข้อผิดพลาดใหม่

ตัว REPEATER ในระบบต้องมีความสามารถเตรียมทั้งทำให้เท่ากัน และทำรูปคลื่นให้เหมือนกัน เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับวิชาการเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปเผยแพร่บนสื่อออนไลน์ หรือทำซ้ำโดยไม่ได้รับอนุญาต หากต้องการข้อมูลเพิ่มเติม กรุณาติดต่อฝ่ายบริการลูกค้า

หน้าที่การเข้ารหัสรวมอยู่ใน 1 หรือ มากกว่าความต้องการต่อไปนี้

1. สัญญาณ PCM หรือ TDM จะถูกเปลี่ยนเป็น 2 ขั้ว
2. IMPEDANCE MATCHING ของสัญญาณหนึ่ง กับ การส่งผ่านในสาย
3. ในทุก ๆ ความยาวสาย 5 K ถึง 6 K FEET ต้องมี ตัว REPEATERS
4. AMI คือ การเข้ารหัส โดยการส่งผ่านสัญญาณไปตามสาย



เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆ ทั้งสิ้น ลึกซึ้งห้ามมิให้คัดลอกไปเผยแพร่ และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้

Laboratory Experimentation

MATERIALS REQUIRED

SIP397-3 panel and 300 B or 300 PSB.

NOTE: When using the 397-3 panel, be sure the Power Supply V_{out} is set to "maximum."


TEST AND MEASUREMENTS

In this experiment, the basic operation of the TSAC will be evaluated. Although a channel selection of 1 of 64 slots can be performed by a microprocessor, for the experimental demonstration, switches are used instead. PCM pulses will be observed in different slot locations.

EXPERIMENTAL PROCEDURES

The time-slot assignment circuit (TSAC) is used for selecting a desired voice channel, which can operate within a 24, 30, 32, or 64 slot frame. The TSAC generates an enabling pulse which turns on the CODEC at the assigned time.

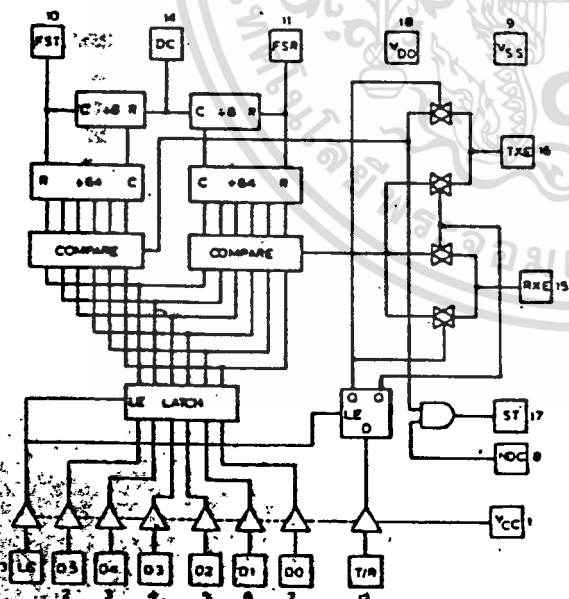The TSAC is activated by both a framing rate and a direct clock. Figure 15-2 shows a block diagram of a Motorola MC14417.



TSAC, MC14417, Block Diagram

FIGURE 15-2

The IC has two major sections, namely, the transmitter-controller and the receiver-controller. Because the transmitted (FST) and received (FSR) signals are tied together, they can be operated in the same slot, or the transmitter and receiver can be placed in different slots. In this experiment, both the transmitter and receiver operate in the same time slot.


A clock operating at 2.204 MHz is fed to pin 1 of the TSAC, which is the direct clock (DC) input.

Inside the IC are two sets of dividers, but when FST and FSR are tied together, they operate in unison. One counter provides a divide-by-64, which feeds a divide-by-64.

After the framing pulse has been activated, the binary input to the latch and comparators determines the slot location. The 8 kHz rate determines the length of the frame, at 125 μ s, and the DC clock, 2.04 MHz, determines the number of slots and the slot width. The MC14417 can produce up to 64 slots. Figure 15-3 shows the TSAC connected to the CODEC IC.

The operational slot is determined by the binary setting of switches 1-4c. The IC has a 6-bit input (D0-D5). When all switches (inputs) are low, the signal appears in the first slot after the framing pulse-zero position. When D0 (switch 1c) is made high, the enabling output, a positive pulse from $T_{x}E$ will turn on the CODEC as soon as the clock has reached the count necessary to change the state of the comparator. Closing switches 1c and 2c, and opening 3c and 4c, permits the CODEC to operate in slot 3. In Figure 15-3, the experimental circuit shows inputs D4 and D5 strapped to ground with this circuit configuration. The maximum number of channel selections is limited to 15 slots. The channel selection by the TSAC will be observed in the following procedures.

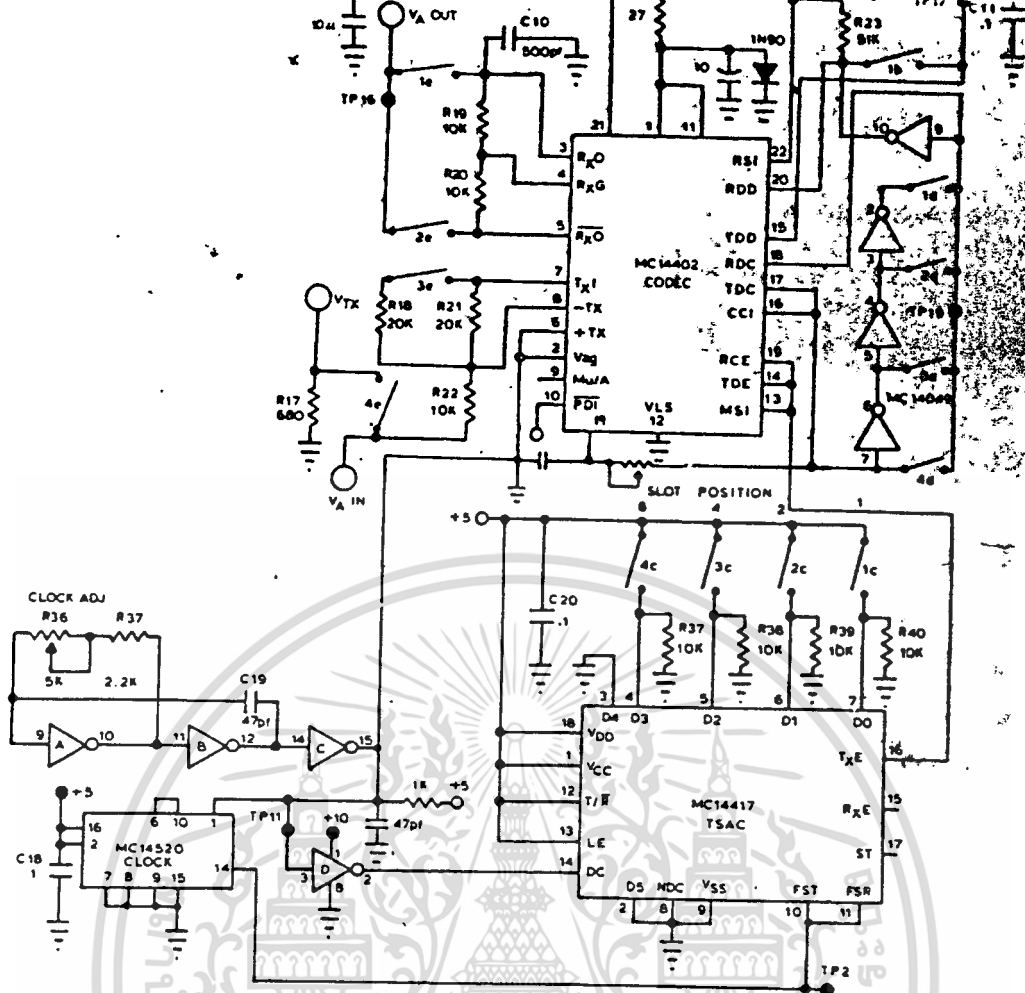The circuit used in the experiment is the same as the one used in Experiment 13, Pulse-Coded Modulation.



TSAC and CODEC Experimental Circuit

FIGURE 15-3

VIEWING THE TIME SLOT

1. Set the clock at TP11 to 2.02 MHz.
2. Record the frame rate at TP17 located in Section G of CODEC. Connect the external trigger input (sync) of your oscilloscope to TP26 (Section K).
3. Set switches 1-4c to the off position. Connect one of the oscilloscope's inputs to TP13 in order to view the enabling pulse. What is the pulse width of the enabling pulse? _____ Amplitude? _____
4. When all switches are low, the first pulse should appear at the triggering start. Set the oscilloscope sweep to 20 μ s.

5. The TSAC control switches are binary, 1-2-4-8. When the first switch is on (high), the pulse moves one position, which is _____ μ s. This is channel #1. NOTE: You should have switches 3a, b1, 4d closed, and scope probe on TP17.
6. Turn off switch 1, and make switch 2 (high). What channel is now turned on? _____
7. Turn on all switches. The enabling pulse is on channel _____, which is _____ μ s removed from the framing pulse.

VIEWING CODEC OUTPUT

8. Close switch 3b, which connects the PCM output to the light modulator. View TP17, and start with all "c" switches set at low (zero channel). Maintain the oscilloscope sync connection (TP2). Also close switch 4e, which loads the PCM input. Sketch pulses observed at TP17 -- expand sweep to 1 or 2 μ s. How many pulses are present? _____ .

ADDENDUM

An alternate method of observing this effect can be obtained by setting the switches as follows:

OPEN

1a, 4a
1b, 2b, 4b
2c, 3c, 4c
1d, 2d, 3d
1e, 3e

CLOSE

2a, 3a
3b
1c
4d
2e, 4e

Inject a 100 to 200 mV, 1 kHz, square or sine wave into Va in. (TP15). Scope TP17 and you will observe the eight pulses which are occupying channel #1 (switch 1c brings channel #1 on line). If you scope TP13 you will see the allotted space of channel #1. If you use alternate mode switching on your scope you will see the eight data pulses and channel #1 simultaneously.

9. Switch in slot 3 or 4 by making switches 1 and 2 or 3c high. Observe TP20. What happens to the position of the pulse? _____ . Are individual pulses still visible? _____ .
10. Return to the zero slot, and observe TP20 when the clock frequency is lowered. What happens to the period (width) of the slot? _____ .
11. If one slot were to be used for transmission and another for reception, what would be required of TxE (pin 16) and RxE (pin 15) of the TSAC? _____ .
12. Can the switches be replaced by logic gates, allowing the slot's microprocessor to be selected? _____ .


REVIEW QUESTIONS



1. The line repeater in PCM transmission is used to _____ the transmitted pulses.
2. Repeaters used in fiber optics lines are spaced _____ miles apart.
3. PCM requires a _____ bandwidth than the transmission of standard analog signals.
4. Unipolar pulses are either all _____ or _____ going.
5. Is the MC14402 CODEC a unipolar device?

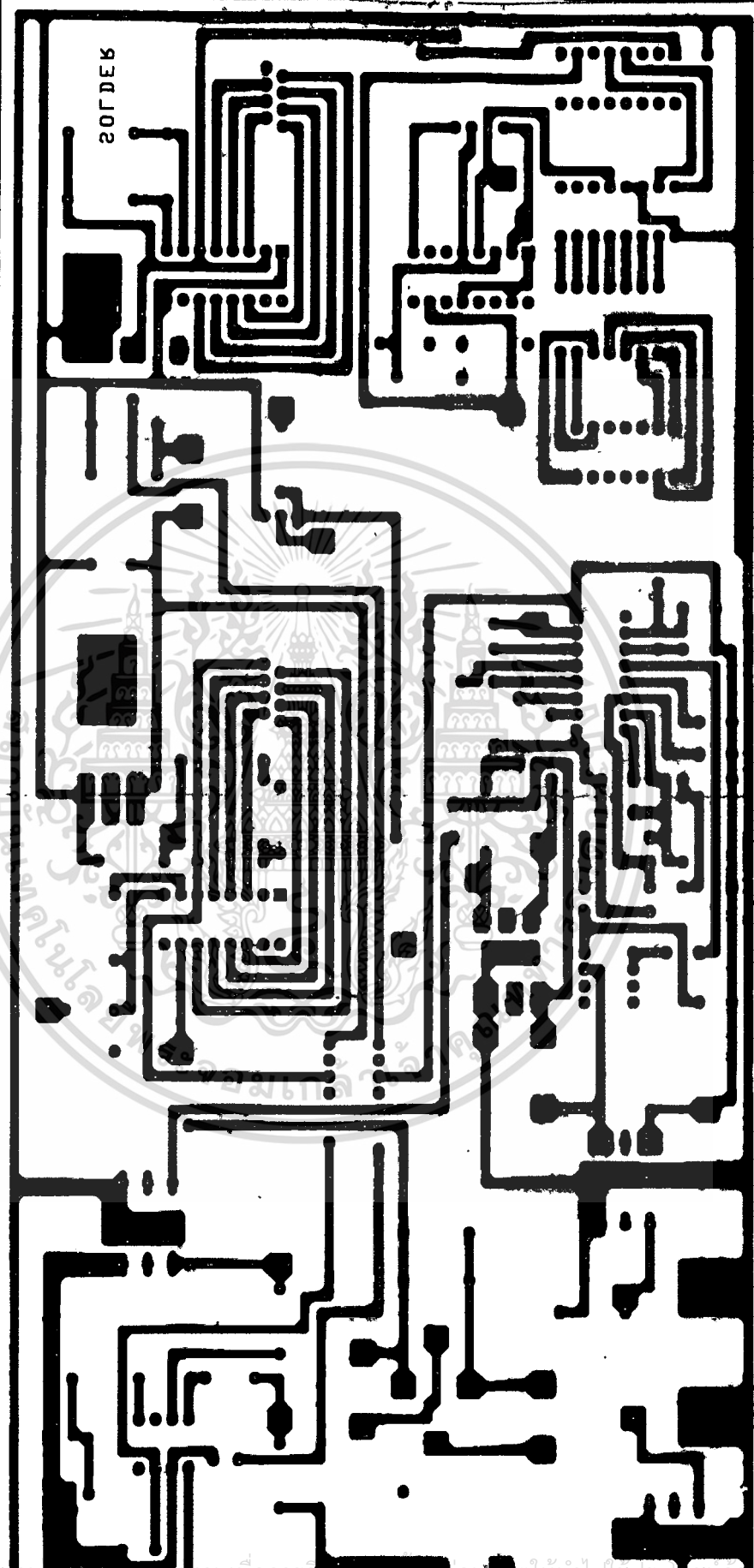6. The clock frequency generally used in the United States is _____ MHz.
7. The framing pulse operates at _____.
8. AMI stands for _____ encoding.
9. PCM transmits a _____ group of pulses.
10. In the United States, a frame contains _____ slots.
11. When the clock frequency is 2.04 MHz, the frame rate is 8 kHz. The period of one time slot is _____ microseconds.
12. Each bit in the 8-bit serial stream occupies _____ microseconds.
13. The MC14417 TSAC has _____ time slots.
14. The TSAC turns on the _____ encoder.
15. The TSAC can turn a transmitter and a receiver on to _____ channels.

เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า

ไม่ว่ากรณีใดๆทั้งสิ้น อีกทั้งห้ามมิให้ดัดแปลงเนื้อหา และต้องอ้างอิงถึงเจ้าของเอกสารทุกครั้งที่มีการนำไปใช้



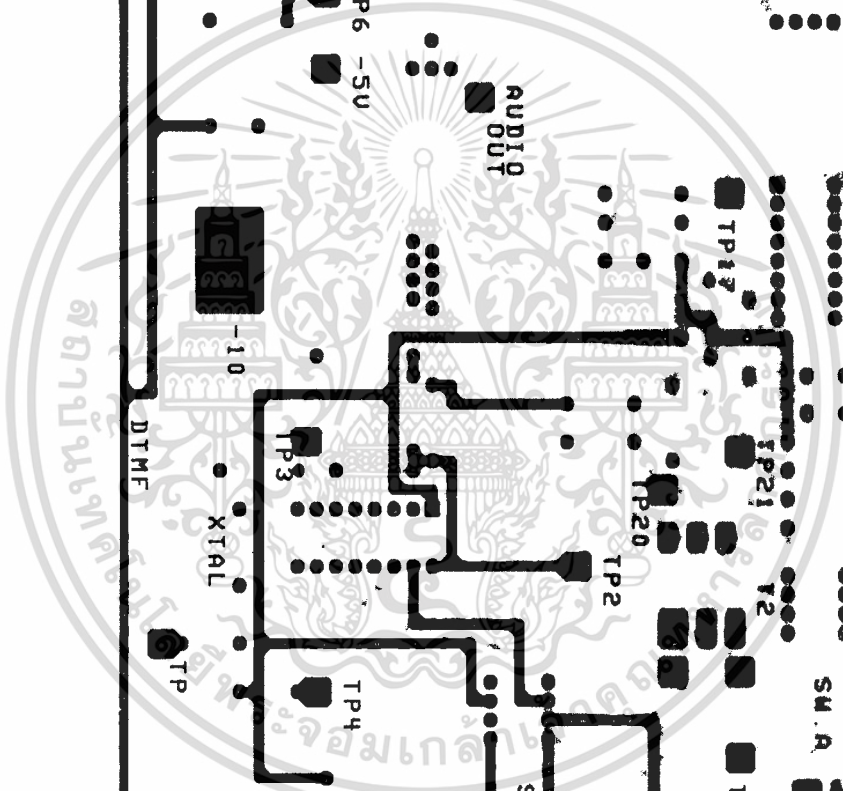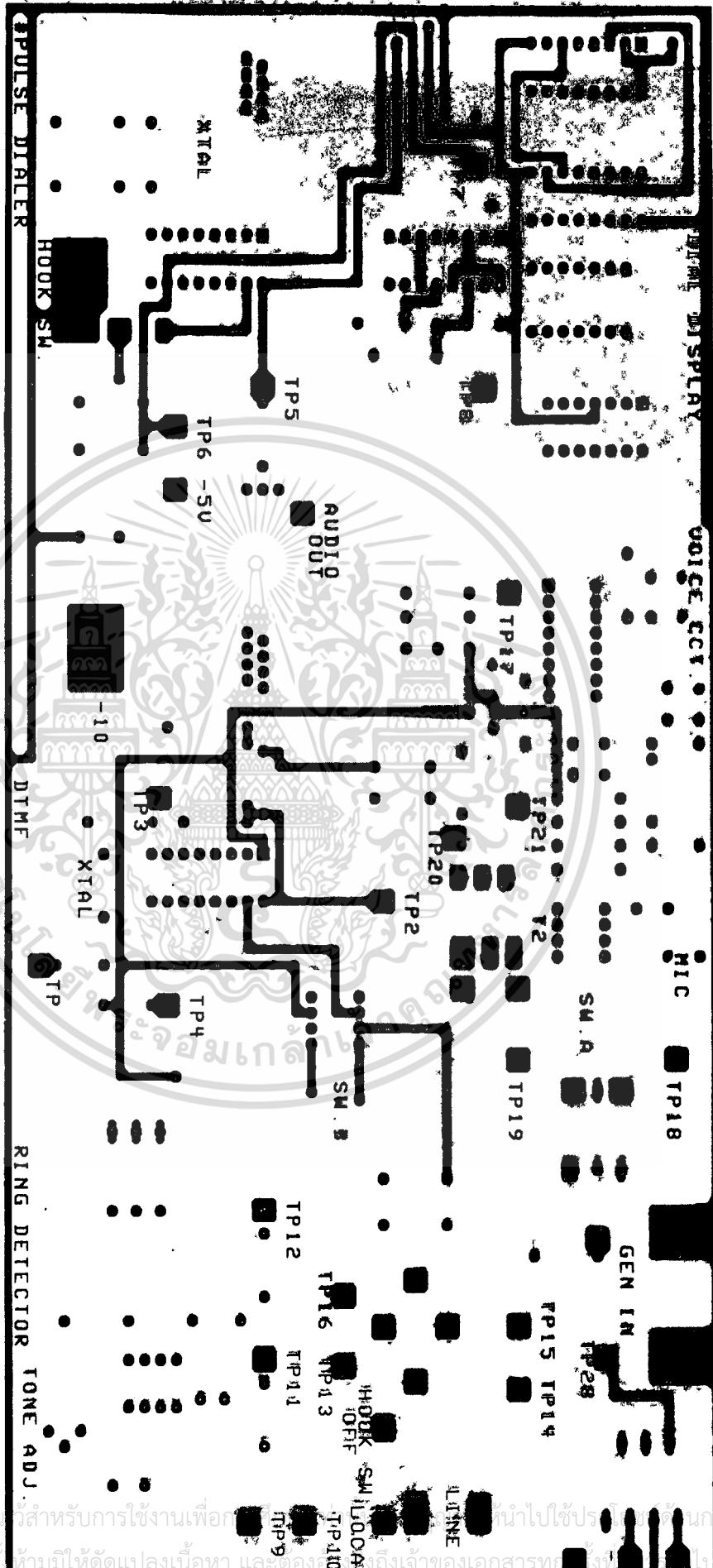

Features

- 150V BIFET technology for efficient use of telephone line power
- Requires 50% fewer parts than a typical CMOS ringler
- Provides up to two times the output power of a typical CMOS IC (40V peak)
- Built-in lightning and static protection
- Built-in anti-'tapping' circuitry
- Built-in regulators
- High input standby impedance

Description

The TCM1501A, 05A, 06A/12A ring detector drivers are monolithic ICs designed, using BIFET technology, to serve as the alerting device in the telephone. These ICs sense incoming ring signals and drive either a piezo transducer or a transformer coupled speaker. The TI ring detector drivers are designed to withstand lightning strikes of up to 1500 v @ 200µsec duration. In addition, internal circuitry will ignore dial pulses from parallel phones so that a false ringing (tapping) will not occur.

The TCM1501A, 05A, 06A, 12A are not limited to telecommunications applications. For example, the ring detector driver can be used, with just a few external components, to produce an inexpensive and highly efficient alarm.

Absolute maximum ratings:


Maximum continuous input voltage (Pin 1 ref. to Pin 8):	70 V
Maximum continuous VCC supply (Pin 6 ref. to Pin 7):	70 V
Maximum package power capability (JG package):	840 mW 25°C
(P package):	1 watt 25°C
Operating ambient temperature	-20° to 70°C
Storage ambient temperature	-40° to +125°C
Surge SCR on-state current (on-time < 200 usec):	0.9 Amp.
Maximum continuous input current (with SCR triggered):	0.5 ARMS

* NOTE: Normally the IC is fed with an AC signal through a 2.2 kΩ-M resistor to guarantee compliance with these maximum ratings. Care should be taken when connecting a DC power supply to the C to prevent the internal SCR from being fired which could result in damage to the IC.


Ring detector driver IC family

PART NUMBER	RECTIFIER	OUTPUT	INTENDED TRANSDUCER
TCM1501A	Diode Bridge	Single-ended Freq. = 2000Hz	Speaker or Piezo
TCM1505A	Voltage Doubler	Single-ended Freq. = 2000Hz	
TCM1506A	Diode Bridge	Single-ended Freq. = 500Hz	
TCM1512A	Diode Bridge	Single-ended Freq. = 1kHz	

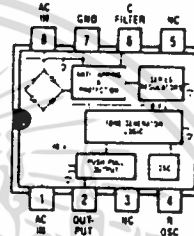TCM 1501A/TCM1506A/TCM1512A pin configuration



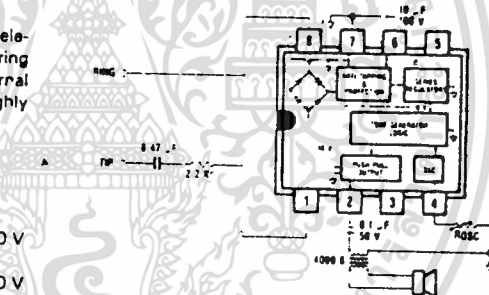TCM1501A/TCM1506A/TCM1512A telephone application




PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNITS
Standby Input Impedance	V _{IN} = 3 Vrms Freq. < 20 kHz	100			kΩMS
Standby Current	V _{IN} = 5 V 0 V with R _L = "open"			20	µA
Threshold Voltage	Adjust V _{IN} up from 0 V with R _L = "open"			28	V
Average Frequency of the Output Signal F _{AVG}	Vary R _{OSC} as required	1800		4000	Hz
		450		1000	
		900		2000	
Operating Voltage DC	Between Pins 1 & 6 R _L = "open"	15		70	V _{DC}
Operating Voltage Telephone Application	Between V _{IN} and ring	40		150	V _{AC}
Output Voltage Swing	V _{IN} = 70 V R _{L,200} = 5.6 kΩ-M			40	V _{pk-pk}

Features

- Monolithic replacement for hybrid coil for the 2/4 wire conversion
- Low power requirement
- Automatic gain variation with DC line
- Externally adjustable transmitting and receiving gains
- Flat electrical response
- Externally adjustable sidetone
- Externally adjustable regulation function
- Externally achievable unregulated version

TCM1705A pin configuration

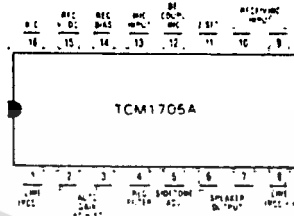

Description

The TCM1705A Telephone hybrid/gain IC is a monolithic circuit which performs the functions of the receiving and transmitting amplifiers and sidetone operations. The T1 telephone hybrid/gain IC replaces the hybrid coil for the 2/4 wire conversion, thus allowing the replacement of the carbon microphone with a passive and more reliable transducer.

The TCM1705A is designed for use with either an electromagnetic microphone or a FET buffered electret element.

Specifications

	1705A
DC voltage operation	4.3 V @ 12 mA
DC current operation	12 mA max
Input impedance	
Transmitting gain	
k = 18 mA	47.8 dB
k = 3C mA	46.8 dB
k = 8C mA	41.7 dB
Receiving gain	
k = 1E mA	-11.8 dB
k = 3C mA	-12.8 dB
k = 8C mA	-17 dB
Receiving distortion 1E to 8C mA	3% @ 50 mV Peak
Transmitting distortion 1E-5C mA	3% @ 55V Peak

Absolute maximum ratings

Max forward	12C mA
Max reverse	-15C mA
Max I3 ms pulse duration	72 V



TP5089 DTMF (TOUCH-TONE[®]) Generator

General Description

The TP5089 is a low threshold voltage, field-implemented, metal gate CMOS integrated circuit. It interfaces directly to a standard telephone keypad and generates all dual tone multi-frequency pairs required in tone-dialing systems. The tone synthesizers are locked to an on-chip reference oscillator using an inexpensive 3.579545 MHz crystal for high tone accuracy. The crystal and an output load resistor are the only external components required for tone generation. A MUTE OUT logic signal, which changes state when any key is depressed, is also provided.

Features

- 2.5V-10V operation when generating tones
- 2V operation of keyscan and MUTE logic
- Static sensing of key closures or logic inputs
- On-chip 3.579545 MHz crystal-controlled oscillator
- High group and low group tones generated and mixed internally
- High group pre-emphasis
- Low harmonic distortion
- Open emitter-follower low-impedance output
- SINGLE TONE INHIBIT pin

Block Diagram

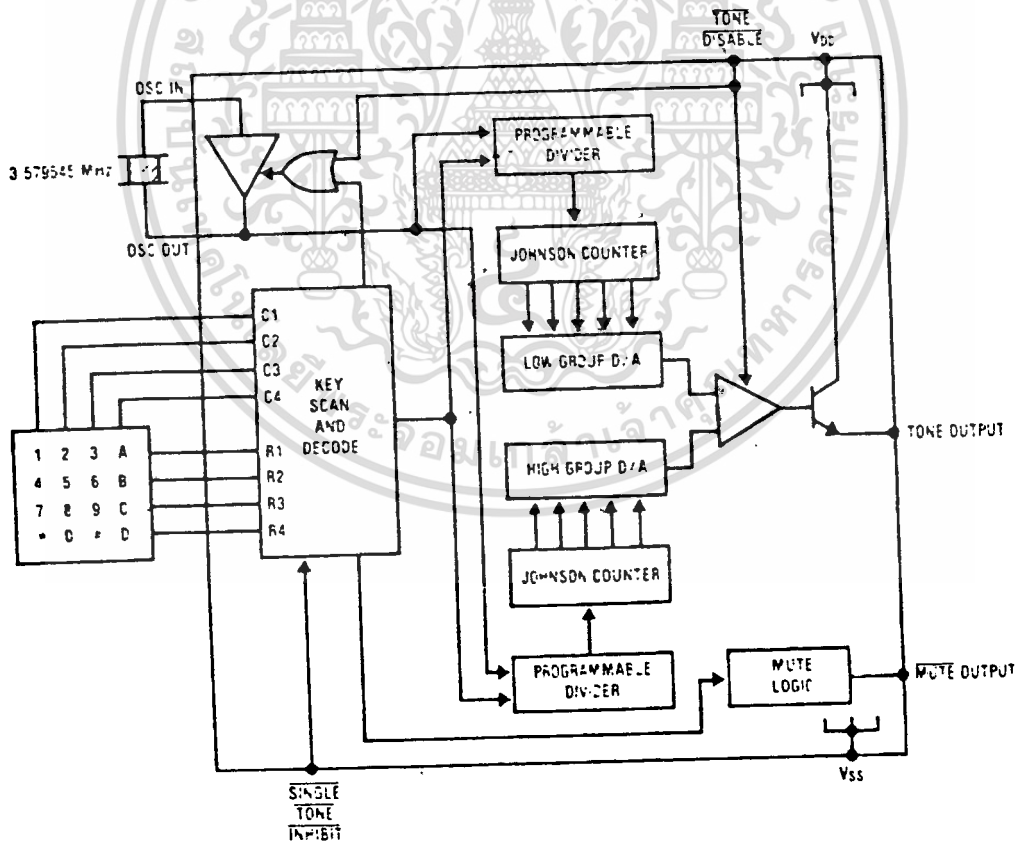


FIGURE 1

TO CONTACT SALES OR TECHNICAL SUPPORT, CALL 1-800-541-2000


Absolute Maximum Ratings

Supply Voltage ($V_{DD} - V_{SS}$)	15V
Maximum Voltage at Any Pin	$V_{DD} + 0.3V$ to $V_{SS} - 0.3V$
Operating Temperature	-30°C to +60°C
Storage Temperature	-55°C to +150°C
Maximum Power Dissipation	500 mW

Electrical Characteristics T_A within operating temperature range, $2.5V < V_{DD} < 10V$ unless otherwise stated.

Parameter	Conditions	Min	Typ	Max	Units
Minimum Supply Voltage for Keyscan and MUTE Logic Functions		2			V
Operating Current Idle	$R_L = 10\text{ k}\Omega$ $V_{DD} = 5V$		20		μA
Input Resistors COLUMN and ROW (Pull-Up) SINGLE TONE INHIBIT (Pull-Down) TONE DISABLE (Pull-Up)			2		$\text{m}\Omega$
			40		$\text{k}\Omega$
			50		$\text{k}\Omega$
MUTE OUT Sink Current (COLUMN and ROW Active)	$V_{DD} = 3V$ $V_o = 0.5V$	0.5			mA
Output Amplitudes Low Group	$R_L = 240\Omega$ $V_{DD} = 3V$		250		mVrms
	$V_{DD} = 10V$		850		mVrms
	$V_{DD} = 3V$		315		mVrms
	$V_{DD} = 10V$		1000		mVrms
Mean Output DC Offset	$V_{DD} = 3V$		1.2		V
	$V_{DD} = 10V$		4.2		V
High Group Pre-Emphasis		2.4	2.7	3.0	dB
Dual Tone/Total Harmonic Distortion Ratio	1 MHz Bandwidth	22			dB
Start-Up Time (to 90% Amplitude)				5	ms

Connection Diagram

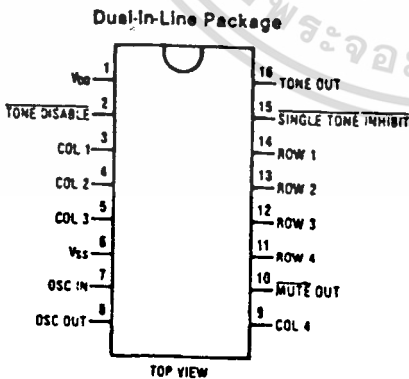

Order Number TP5089N
See NS Package N16A

Pin Descriptions

V_{DD} (Pin 1): This is the positive voltage supply to the device, referenced to V_{SS} . The collector of the TONE OUT transistor is connected to this pin.

V_{SS} (Pin 6): This is the negative voltage supply.

OSCILLATOR (Pins 7 and 8): All tone generation timing is derived from the on-chip oscillator circuit. A low-cost 3.579545 MHz A-cut crystal (NTSC TV color-burst) is needed between pins 7 and 8. Load capacitors and a feedback resistor are included on-chip for good start-up and stability. The oscillator stops when column inputs are sensed with no valid input having been detected. The oscillator is also stopped when the TONE DISABLE input is pulled to logic low.

Row and Column Inputs (Pins 3, 4, 5, 9, 11, 12, 13, 14): When no key is pushed, pull-up resistors are active on row and column inputs. A key closure is recognized when a single row and a single column are connected to V_{SS} , which starts the oscillator and initiates tone generation. Negative-true logic signals simulating key closures can also be used.

Pin Descriptions (Continued)

TONE DISABLE Input (Pin 2): The TONE DISABLE input has an internal pull-up resistor. When this input is open or at logic high, the normal tone output mode will occur. When TONE DISABLE input is at logic low, the device will be in the inactive mode, TONE OUTPUT will be at an open circuit state.

MUTE Output (Pin 10): The MUTE output is an open-drain N-channel device that sinks current to V_{SS} with any key input and is open when no key input is sensed. The MUTE output will switch regardless of the state of the SINGLE TONE INHIBIT input.

SINGLE TONE INHIBIT Input (Pin 15): The SINGLE TONE INHIBIT input is used to inhibit the generation of other than valid tone pairs due to multiple row-column closures. It has a pull-down resistor to V_{SS}, and when left open or tied to V_{SS} any input condition that would normally result in a single tone will now result in no tone, with all other functions operating normally. When tied to V_{DD}, single or dual tones may be generated, see Table II.

TONE OUT (Pin 16): This output is the open emitter of an NPN transistor, the collector of which is connected to V_{DD}. When an external load resistor is connected from TONE OUT to V_{SS}, the output voltage on this pin is the sum of the high and low group sine-waves superimposed on a DC offset. When not generating tones, this output transistor is turned OFF to minimize the device idle current.

Adjustment of the emitter load resistor results in variation of the mean DC current during tone generation, the sine-wave signal current through the output transistor, and the output distortion. Increasing values of load resistance decrease both the signal current and distortion.

Functional Description

With no key inputs to the device the oscillator is inhibited, the output transistor is pulled OFF and device current consumption is reduced to a minimum. Key closures are sensed statically to ensure no modulation of the line when tones are not being generated. Any key closure activates the MUTE output, starts the oscillator and sets the high group and low group programmable counters to the appropriate divide ratio. These counters sequence two ratioed-capacitor D/A converters through a series of 28 equal duration steps per sine-wave cycle. The two tones are summed by a mixer amplifier, with pre-emphasis applied to the high group tone. The output is an NPN emitter-follower requiring the addition of an external load resistor to V_{SS}. This resistor facilitates adjustment of the signal current flowing from V_{DD} through the output transistor.

The amplitude of the output tones is directly proportional to the device supply voltage

TABLE I. Output Frequency Accuracy

Tone Group	Valid Input	Standard DTMF (Hz)	Tone Output Frequency	% Deviation from Standard
Low Group <i>f_L</i>	R1	697	694.8	-0.32
	R2	770	770.1	+0.02
	R3	852	852.4	+0.03
	R4	941	940.0	-0.11
High Group <i>f_H</i>	C1	1209	1206.0	-0.24
	C2	1336	1331.7	-0.32
	C3	1477	1486.5	+0.64
	C4	1633	1639.0	+0.37

TABLE II. Functional Truth Table

SINGLE TONE INHIBIT	TONE DISABLE	ROW	COLUMN	TONE OUT		MUTE
				Low	High	
X	0	O/C	O/C	0V	0V	0
X	X	O/C	O/C	0V	0V	0
X	0	One	One	V _{OS}	V _{OS}	1
X	1	One	One	<i>f_L</i>	<i>f_H</i>	1
1	1	2 or More	One	—	<i>f_H</i>	1
1	1	One	2 or More	<i>f_L</i>	—	1
1	1	2 or More	2 or More	V _{OS}	V _{OS}	1
0	1	2 or More	One	V _{OS}	V _{OS}	1
0	1	One	2 or More	V _{OS}	V _{OS}	1
0	1	2 or More	2 or More	V _{OS}	V _{OS}	1

Note 1: X is don't care state

Note 2: V_{OS} is the output offset voltage



MOTOROLA

MC14511B

BCD-TO-SEVEN SEGMENT LATCH/DECODER/DRIVER

The MC14511B BCD-to-seven segment latch/decoder/driver is constructed with complementary MOS (CMOS) enhancement mode devices and NPN bipolar output drivers in a single monolithic structure. The circuit provides the functions of a 4-bit storage latch, an 8421 BCD-to-seven segment decoder, and an output drive capability. Lamp test (LT), blanking (BI), and latch enable (LE) inputs are used to test the display, to turn-off or pulse modulate the brightness of the display, and to store a BCD code, respectively. It can be used with seven-segment light emitting diodes (LED), incandescent, fluorescent, gas discharge, or liquid crystal readouts either directly or indirectly.

Applications include instrument (e.g., counter, DVM, etc) display driver, computer/calculator display driver, cockpit display driver, and various clock, watch, and timer uses.

- Quiescent Current = 5.0 nA/package typical @ 5 Vdc
• Low Logic Circuit Power Dissipation
• High-Current Sourcing Outputs (Up to 25 mA)
• Latch Storage of Code
• Blanking Input
• Lamp Test Provision
• Readout Blanking on all Illegal Input Combinations
• Lamp Intensity Modulation Capability
• Time Share (Multiplexing) Facility
• Supply Voltage Range = 3.0 Vdc to 18 Vdc
• Capable of Driving Two Low-power TTL Loads, One Low-power Schottky TTL Load or Two HTL Loads Over the Rated Temperature Range

CMOS MSI


(LOW-POWER COMPLEMENTARY MOS)

BCD-TO-SEVEN SEGMENT LATCH/DECODER/DRIVER



L SUFFIX CERAMIC PACKAGE CASE 020
P SUFFIX PLASTIC PACKAGE CASE 040

ORDERING INFORMATION

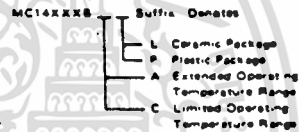

MAXIMUM RATINGS (Voltages referenced to VSS)



Table with 4 columns: Rating, Symbol, Value, Unit. Rows include DC Supply Voltage, Input Voltage, DC Current Drain, Operating Temperature Range, Storage Temperature Range, Maximum Output Drive Current, and Maximum Continuous Output Power.

* P_OHmax = I_OH (V_DD - V_OH)

This device contains circuitry to protect the inputs against damage due to high static voltages or electric fields, however, it is advised that normal precautions be taken to avoid application of any voltage higher than maximum rated voltages to this high impedance circuit.

Due to the sourcing capability of this circuit, damage can occur to the device if VDD is applied, and the outputs are shorted to VSS and are at a logical 1 (See Maximum Ratings)

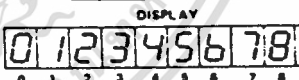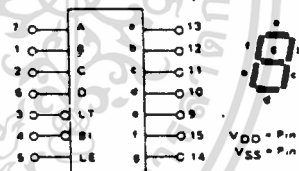Unused inputs must always be tied to an appropriate logic voltage level (e.g., either VSS or VDD).



TRUTH TABLE

Truth table with columns for inputs LE, BI, LT, D, C, B, A and outputs a, b, c, d, e, f, g, DISPLAY. It lists all possible BCD input combinations and the resulting segment outputs.

X = Don't Care
* Depends upon the BCD code previously applied when LE = 0

ELECTRICAL CHARACTERISTICS

Characteristic	Symbol	VDD Vdc	T _{low} *		25°C			T _{high} *		Unit			
			Min	Max	Min	Typ	Max	Min	Max		Vdc		
Output Voltage V _{in} = VDD or 0	"0" Level VOL	5.0	-	0.05	-	0	0.05	-	0.05	Vdc			
		10	-	0.05	-	0	0.05	-	0.05				
		15	-	0.05	-	0	0.05	-	0.05				
	"1" Level VOH	5.0	4.1	-	4.1	4.57	-	4.1	-	Vdc			
		10	9.1	-	9.1	9.58	-	9.1	-				
		15	14.1	-	14.1	14.59	-	14.1	-				
Input Voltage [#] V _O = 3.8 or 0.5 Vdc (V _O = 8.8 or 1.0 Vdc) (V _O = 13.8 or 1.5 Vdc)	"0" Level VIL	5.0	-	1.5	-	2.25	1.5	-	1.5	Vdc			
		10	-	3.0	-	4.50	3.0	-	3.0				
		15	-	4.0	-	6.75	4.0	-	4.0				
	"1" Level VIH	5.0	3.5	-	3.5	2.75	-	3.5	-	Vdc			
		10	7.0	-	7.0	5.50	-	7.0	-				
		15	11.0	-	11.0	8.25	-	11.0	-				
Output Drive Voltage (AL Device) Source	VOH	5.0	4.10	-	4.10	4.57	-	4.1	-	Vdc			
			(I _{OH} = 0 mA)	-	-	4.24	-	-	-				
			(I _{OH} = 5.0 mA)	-	-	3.90	4.12	-	3.5		-		
			(I _{OH} = 10 mA)	-	-	-	3.94	-	-		-		
			(I _{OH} = 15 mA)	-	-	-	3.75	-	3.0		-		
			(I _{OH} = 20 mA)	3.40	-	3.40	3.75	-	-		-		
		(I _{OH} = 25 mA)	-	-	-	3.54	-	-	-				
		10	9.10	-	9.10	9.58	-	9.1	-	Vdc			
			(I _{OH} = 0 mA)	-	-	9.26	-	-	-				
			(I _{OH} = 5.0 mA)	-	-	9.00	9.17	-	8.8		-		
			(I _{OH} = 10 mA)	9.00	-	9.00	9.04	-	-		-		
			(I _{OH} = 15 mA)	-	-	-	8.90	-	8.2		-		
	(I _{OH} = 20 mA)		8.60	-	8.60	8.75	-	-	-				
	(I _{OH} = 25 mA)	-	-	-	-	-	-	-					
	15	14.1	-	14.1	14.59	-	14.1	-	Vdc				
		(I _{OH} = 0 mA)	-	-	14.27	-	-	-					
		(I _{OH} = 5.0 mA)	-	-	14.0	14.18	-	13.8		-			
		(I _{OH} = 10 mA)	14.0	-	14.0	14.07	-	-		-			
		(I _{OH} = 15 mA)	-	-	-	13.95	-	13.2		-			
		(I _{OH} = 20 mA)	13.8	-	13.8	13.80	-	-		-			
		(I _{OH} = 25 mA)	-	-	-	-	-	-		-			
		Output Drive Voltage (CL/CP Device) Source	VOH	5.0	4.10	-	4.10	4.57		-	4.1	-	Vdc
					(I _{OH} = 0 mA)	-	-	4.24		-	-	-	
					(I _{OH} = 5.0 mA)	-	-	3.60		4.12	-	3.3	
(I _{OH} = 10 mA)					-	-	-	3.94		-	-	-	
(I _{OH} = 15 mA)					-	-	-	3.75		-	2.5	-	
(I _{OH} = 20 mA)	2.80				-	2.80	3.75	-	-	-			
(I _{OH} = 25 mA)	-			-	-	3.54	-	-	-				
10	9.10			-	9.10	9.58	-	9.1	-	Vdc			
	(I _{OH} = 0 mA)			-	-	9.26	-	-	-				
	(I _{OH} = 5.0 mA)			-	-	8.75	9.17	-	8.45		-		
	(I _{OH} = 10 mA)			-	-	-	9.04	-	-		-		
	(I _{OH} = 15 mA)			-	-	-	8.90	-	7.8		-		
	(I _{OH} = 20 mA)		8.10	-	8.10	8.75	-	-	-				
(I _{OH} = 25 mA)	-		-	-	-	-	-	-					
15	14.1		-	14.1	14.59	-	14.1	-	Vdc				
	(I _{OH} = 0 mA)		-	-	14.27	-	-	-					
	(I _{OH} = 5.0 mA)		-	-	13.75	14.18	-	13.45		-			
	(I _{OH} = 10 mA)		13.75	-	13.75	14.07	-	-		-			
	(I _{OH} = 15 mA)		-	-	-	13.95	-	12.8		-			
	(I _{OH} = 20 mA)		13.1	-	13.1	13.80	-	-		-			
	(I _{OH} = 25 mA)		-	-	-	-	-	-		-			
	Output Drive Current (AL Device) Sink		IOL	5.0	0.64	-	0.51	0.88		-	0.36	-	mA
				10	1.6	-	1.3	2.25		-	0.9	-	
				15	4.2	-	3.4	8.8		-	2.4	-	
		Output Drive Current (CL/CP Device) Sink	IOL	5.0	0.52	-	0.44	0.82		-	0.36	-	mA
				10	1.3	-	1.1	2.25		-	0.9	-	
15				3.6	-	3.0	8.8	-	2.4	-			

MC14518B MC14520B.

DUAL UP COUNTERS

The MC14518B dual BCD counter and the MC14520B dual binary counter are constructed with MOS P-channel and N-channel enhancement mode devices in a single monolithic structure. Each consists of two identical, independent, internally synchronous 4-stage counters. The counter stages are type D flip-flops, with interchangeable Clock and Enable lines for incrementing on either the positive-going or negative-going transition as required when cascading multiple stages. Each counter can be cleared by applying a high level on the Reset line. In addition, the MC14518B will count out of all undefined states within two clock periods. These complementary MOS up counters find primary use in multi-stage synchronous or ripple counting applications requiring low power dissipation and/or high noise immunity.

- Quiescent Current = 5.0 nA/package typical @ 5 Vdc
- Noise Immunity = 45% of VDD typical
- Diode Protection on All Inputs
- Supply Voltage Range = 3.0 Vdc to 18 Vdc
- Low Input Capacitance = 5.0 pF typical
- Internally Synchronous for High Internal and External Speeds
- Logic Edge-Clocked Design - Incremented on Positive Transition of Clock or Negative Transition on Enable
- 6.0 MHz Counting Rate
- Capable of Driving Two Low-power TTL Loads, One Low-power Schottky TTL Load or Two HTL Loads Over the Rated Temperature Range

MAXIMUM RATINGS (Voltages referenced to VSS)

Rating	Symbol	Value	Unit
DC Supply Voltage	VDD	-0.5 to +18	Vdc
Input Voltage All Inputs	V _{in}	-0.5 to VDD + 0.5	Vdc
DC Current Drain per Pin	I	10	mA
Operating Temperature Range - AL Device	T _A	-55 to +125	°C
		-40 to +85	°C
Storage Temperature Range	T _{stg}	-65 to +150	°C

TRUTH TABLE

CLOCK	ENABLE	RESET	ACTION
↑	1	0	Increment Counter
0	↑	0	Increment Counter
↑	0	0	No Change
x	↑	0	No Change
↑	0	0	No Change
↑	0	0	No Change
x	x	1	Q0 thru Q3 = 0

x = Don't Care

CMOS MSI


(LOW-POWER COMPLEMENTARY MOS)

**DUAL BCD UP COUNTER
(MC14518B)
DUAL BINARY UP COUNTER
(MC14520B)**




L SUFFIX CERAMIC PACKAGE CASE 620 **P SUFFIX PLASTIC PACKAGE CASE 648**

ORDERING INFORMATION

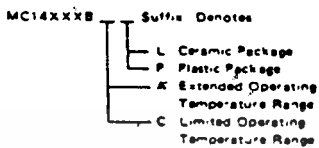

BLOCK DIAGRAM

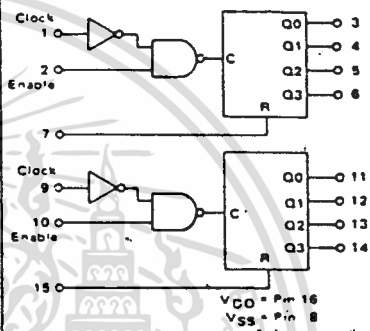

This device contains circuitry to protect the inputs against damage due to high static voltages or electric fields; however, it is advised that normal precautions be taken to avoid application of any voltage higher than maximum rated voltages to this high impedance circuit. For proper operation it is recommended that V_{in} and V_{out} be constrained to the range VSS < (V_{in} or V_{out}) < VDD. Unused inputs must always be tied to an appropriate logic voltage level (e.g., either VSS or VDD).

(V _{in} = 0)										
Quiescent Current (AL Device) (P _{er} Package)	IDD	5.0	—	5.0	—	0.005	5.0	—	150	μA
		10	—	10	—	0.010	10	—	300	
		15	—	20	—	0.015	20	—	600	
Quiescent Current (CL/CP Device) (P _{er} Package)	IDD	5.0	—	20	—	0.005	20	—	150	μA
		10	—	40	—	0.010	40	—	300	
		15	—	80	—	0.015	80	—	600	
Total Supply Current**† (Dynamic plus Quiescent, P _{er} Package) (C _L = 50 pF on all outputs, all buffers switching)	IT	5.0				IT = (0.6 μA/kHz) f + IDD				μA
		10				IT = (1.2 μA/kHz) f + IDD				
		15				IT = (1.7 μA/kHz) f + IDD				

*T_{low} = -55°C for AL Device, -40°C for CL/CP Device
 †T_{high} = +125°C for AL Device, +85°C for CL/CP Device
 ‡Noise immunity specified for worst-case input combination
 Noise Margin for both "1" and "0" level = 1.0 Vdc min @ VDD = 5.0 Vdc
 2.0 Vdc min @ VDD = 10 Vdc
 2.5 Vdc min @ VDD = 15 Vdc
 ††To calculate total supply current at loads other than 50 pF
 IT(C_L) = IT(50 pF) + 2 × 10⁻³ (C_L - 50) VDD f
 where IT is in μA (per package), C_L in pF, VDD in Vdc, and f in kHz is input frequency
 **The formulas given are for the typical characteristics only at 25°C



MOTOROLA

MC14528B

DUAL MONOSTABLE MULTIVIBRATOR

The MC14528B is a dual, retriggerable, resettable monostable multivibrator. It may be triggered from either edge of an input pulse, and will produce an accurate output pulse over a wide range of widths, the duration and accuracy of which are determined by the external timing components, C_X and R_X .

- Separate Reset Available
- Quiescent Current = 5.0 nA/package typical @ 5 Vdc
- Diode Protection on All Inputs
- Triggerable from Leading or Trailing Edge Pulse
- Supply Voltage Range = 3.0 Vdc to 18 Vdc
- Capable of Driving Two Low-power TTL Loads, One Low-power Schottky TTL Load or Two HTL Loads Over the Rated Temperature Range
- See MC14538B Data Sheet for Applications Requiring Precise Control of Output Pulse Width

MAXIMUM RATINGS (Voltages referenced to V_{SS})

Rating	Symbol	Value	Unit
DC Supply Voltage	V_{DD}	-0.5 to +18	Vdc
Input Voltage, All Inputs	V_{in}	-0.5 to $V_{DD} + 0.5$	Vdc
DC Current Drain per Pin	I	10	mAdc
Operating Temperature Range - AL Device	T_A	-55 to +125	$^{\circ}C$
Operating Temperature Range - CL/CP Device		-40 to +85	$^{\circ}C$
Storage Temperature Range	T_{stg}	-65 to +150	$^{\circ}C$

CMOS MSI


(LOW-POWER COMPLEMENTARY MOS)

DUAL RETRIGGERABLE/RESETTING MONOSTABLE MULTIVIBRATOR




L SUFFIX CERAMIC PACKAGE CASE 620
 P SUFFIX PLASTIC PACKAGE CASE 848


ORDERING INFORMATION

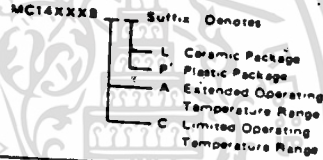

LOGIC DIAGRAM (1/2 of Device Shown)

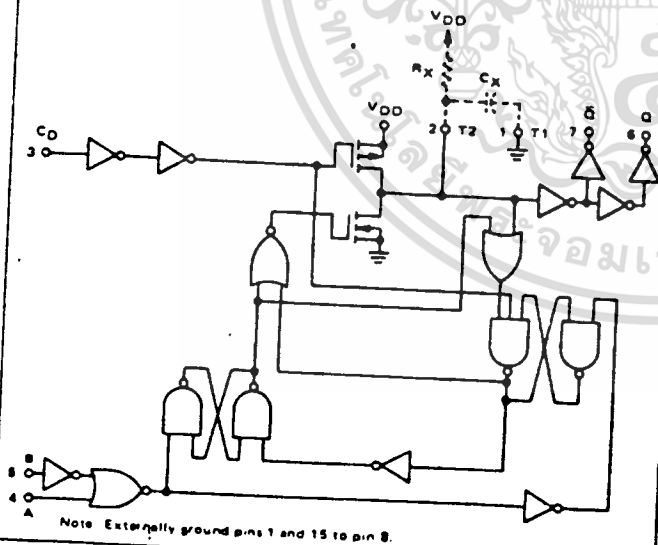

BLOCK DIAGRAM

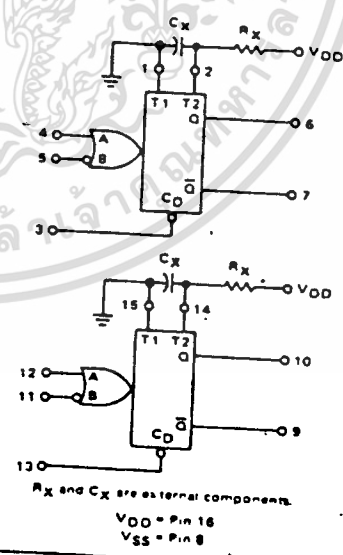

ELECTRICAL CHARACTERISTICS

Characteristic	Symbol	VDD Vdc	T _{low} *		25°C			T _{high} *		Unit
			Min	Max	Min	Typ	Max	Min	Max	
Output Voltage V _{in} = VDD or 0 V _{in} = 0 or VDD	"0" Level VOL	5.0	-	0.05	-	0	0.05	-	0.05	Vdc
		10	-	0.05	-	0	0.05	-	0.05	
		15	-	0.05	-	0	0.05	-	0.05	
	"1" Level VOH	5.0	4.95	-	4.95	5.0	-	4.95	-	Vdc
		10	9.95	-	9.95	10	-	9.95	-	
		15	14.95	-	14.95	15	-	14.95	-	
Input Voltage** (V _O = 4.5 or 0.5 Vdc) (V _O = 9.0 or 1.0 Vdc) (V _O = 13.5 or 1.5 Vdc)	"0" Level VIL	5.0	-	1.5	-	2.25	1.5	-	1.5	Vdc
		10	-	3.0	-	4.50	3.0	-	3.0	
		15	-	4.0	-	6.75	4.0	-	4.0	
	"1" Level VIH	5.0	3.5	-	3.5	2.75	-	3.5	-	Vdc
		10	7.0	-	7.0	5.50	-	7.0	-	
		15	11.0	-	11.0	8.25	-	11.0	-	
Output Drive Current (AL Device) Source (V _{OH} = 2.5 Vdc) (V _{OH} = 4.6 Vdc) (V _{OH} = 9.5 Vdc) (V _{OH} = 13.5 Vdc) Sink (V _{OL} = 0.4 Vdc) (V _{OL} = 0.5 Vdc) (V _{OL} = 1.5 Vdc)	IOH	5.0	-1.2	-	-1.0	-1.7	-	-0.7	-	mA _{dc}
		5.0	-0.25	-	-0.2	-0.36	-	-0.14	-	
		10	-0.62	-	-0.5	-0.9	-	-0.35	-	
	IOL	5.0	0.64	-	0.51	0.88	-	0.36	-	mA _{dc}
		10	1.8	-	1.3	2.25	-	0.9	-	
		15	4.2	-	3.4	8.8	-	2.4	-	
Output Drive Current (CL/CP Device) Source (V _{OH} = 2.5 Vdc) (V _{OH} = 4.6 Vdc) (V _{OH} = 9.5 Vdc) (V _{OH} = 13.5 Vdc) Sink (V _{OL} = 0.4 Vdc) (V _{OL} = 0.5 Vdc) (V _{OL} = 1.5 Vdc)	IOH	5.0	-1.0	-	-0.8	-1.7	-	-0.6	-	mA _{dc}
		5.0	-0.2	-	-0.16	-0.36	-	-0.12	-	
		10	-0.5	-	-0.4	-0.9	-	-0.3	-	
	IOL	5.0	0.52	-	0.44	0.88	-	0.36	-	mA _{dc}
		10	1.3	-	1.1	2.25	-	0.9	-	
		15	3.6	-	3.0	8.8	-	2.4	-	
Input Current (AL Device)	I _{in}	15	-	±0.1	-	±0.00001	±0.1	-	±1.0	μA _{dc}
Input Current (CL/CP Device)	I _{in}	15	-	±0.3	-	±0.00001	±0.3	-	±1.0	μA _{dc}
Input Capacitance (V _{in} = 0)	C _{in}	-	-	-	-	5.0	7.5	-	-	pF
Quiescent Current (AL Device) (Per Package)	IDD	5.0	-	5.0	-	0.005	5.0	-	150	μA _{dc}
		10	-	10	-	0.010	10	-	300	
		15	-	20	-	0.015	20	-	600	
Quiescent Current (CL/CP Device) (Per Package)	IDD	5.0	-	20	-	0.005	20	-	150	μA _{dc}
		10	-	40	-	0.010	40	-	300	
		15	-	80	-	0.015	80	-	600	
**Total Supply Current at an external load Capacitance (C _L) and at external timing capacitance (C _X). use the formula -	I _T	-	I _T (C _L , C _X) = (I _{CL} + 0.36C _X /VDD) + 2×10 ⁻⁸ R _X C _X (VDD-2) ² f × 10 ⁻³ where I _T in μA (per circuit), C _L and C _X in pF, R _X in megohms, VDD in Vdc, f in kHz is input frequency.							

*T_{low} = -55°C for AL Device, -40°C for CL/CP Device

*T_{high} = +125°C for AL Device, +85°C for CL/CP Device

#Noise immunity specified for worst-case input combination.

Noise Margin for both "1" and "0" level = 1.0 Vdc min @ VDD = 5.0 Vdc

2.0 Vdc min @ VDD = 10 Vdc

2.5 Vdc min @ VDD = 15 Vdc

**The formulas given are for the typical characteristics only at 25°C.



**National
Semiconductor**

TP50981/TP50981A, TP50982/TP50982A, TP50985/TP50985A Push Button Pulse Dialer Circuits

General Description

This family of monolithic CMOS circuits provides all logic necessary to convert keyboard inputs into a series of pulses simulating rotary telephone dialing. An on-chip memory capable of storing up to 17 digits allows keyboard entries to be made at rates comparable to those of tone-dialing telephones and provides one-key redial of the last number dialed. The keyboard inputs interface directly to a standard 2-of-7 keypad with positive-common or an inexpensive form A-type keyboard. Two outputs, one for pulsing the telephone line, and one to mute the receiver, are provided along with pin selectable Break/Make ratios and an on-chip voltage regulator. The low voltage and low current requirements of these devices allow direct telephone line powered operation.

Features

- TP50981/TP50981A, TP50985/TP50985A for pulsing loop in shunt with speech network
- TP50982/TP50982A for pulsing loop in series with speech network
- 1.7V, 150 μ A operation TP50981A, TP50982A and TP50985A
- Single-contact or positive-common key inputs
- Break/Make ratio pin selectable
- On-chip voltage regulator
- On-chip oscillator using 480 kHz ceramic resonator
- Scratchpad (new number storage without dialing) on TP50985/TP50985A
- 10/20 pps option on TP50985/TP50985A

Block Diagram


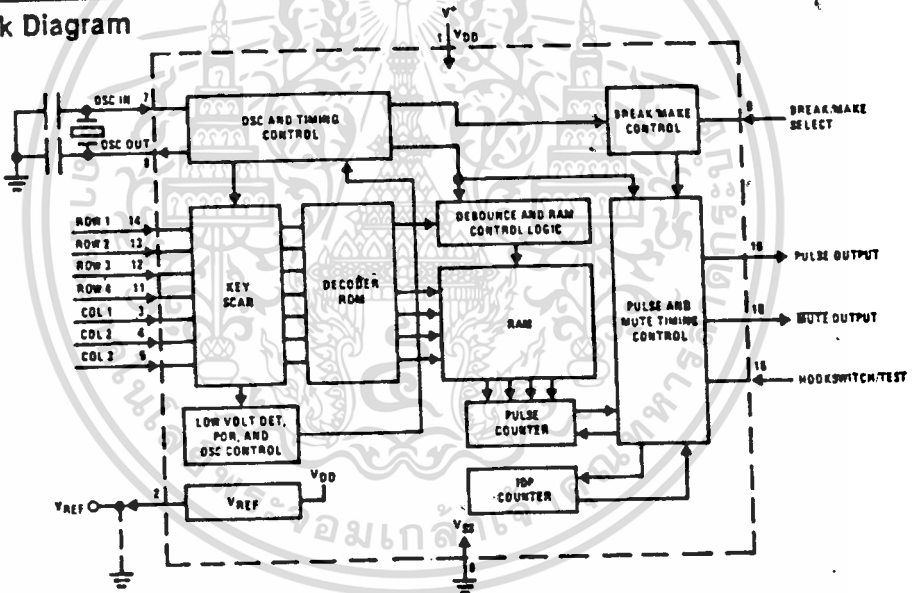


FIGURE 1

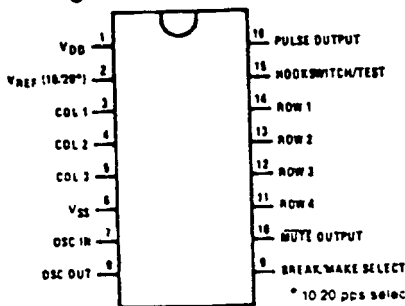Connection Diagram (Dual-In-Line Package, Top View)



Order Number TP50981N, TP50981AN,
TP50982N, TP50982AN, TP50985N
or TP50985AN

* 10/20 pps select: input on TP50985/TP50985A

Absolute Maximum Ratings

DC Supply Voltage ($V_{DD}-V_{SS}$)	6.2V
Voltage on Any Pin	$V_{DD} + 0.3V$ to $V_{SS} - 0.3V$
Operating Temperature	-30°C to +70°C
Storage Temperature	-55°C to +150°C
Maximum Power Dissipation (25°C)	500 mW

DC Electrical Characteristics

T_A within operating temperature range, $V_{DD} \text{ min} \leq V_{DD} \leq 6.0V$, unless otherwise specified.

Parameter	Conditions	Min	Typ	Max	Units
V_{DD} Min DC Supply Voltage TP50981, TP50982, TP50985 TP50981A, TP50982A, TP50985A	Pin 1 Ref. Pin 6	2.5			V
Memory Retention Current TP50981, TP50982, TP50985 TP50981A, TP50982A, TP50985A	$V_{DD} = 2.5V$, Notes 1 and 2 $V_{DD} = 1.7V$, Notes 1 and 2	1.7			V
DC Operating Current	Off-Hook, Valid Key, V_{REF} Tied to V_{SS}		0.7	2.4	mA
V_{REF} Sink Current	$V_{DD} = 5.0V$		0.5	1.0	mA
MUTE Sink Current	$V_{DD} = V_{DD} \text{ Min}$, $V_o = 0.5V$	1.0			mA
PULSE Sink Current	$V_{DD} = V_{DD} \text{ Min}$, $V_o = 0.5V$	0.5	2.0		mA
MUTE and PULSE Leakage	$V_{DD} = 6.0V$, $V_o = 6.0V$	1.0	4.0		mA
Keyboard Contact Resistance			0.001	1.0	mA
Keyboard Capacitance				1.0	kΩ
Logic '0' Level Input				30	pF
Logic '1' Level Input		V_{SS}		$0.2 V_{DD}$	V
Keyboard Pull-Up Resistance		$0.8 V_{DD}$		V_{DD}	V
Keyboard Pull-Down Resistance			4.0		kΩ
HOOKSWITCH Pull-Up Resistance			100		kΩ
			100		kΩ

Note 1: On-hook mode, V_{REF} tied to V_{SS} , all outputs open.

Note 2: Power on reset and low-voltage-detect circuits inhibit the re-dial function if the supply voltage falls below $V_{DD} \text{ Min}$.

AC Electrical Characteristics

T_A within operating temperature range, $V_{DD} \text{ min} \leq V_{DD} \leq 6.0V$, unless otherwise specified.

Parameter	Conditions	Min	Typ	Max	Units
Oscillator Frequency	Anti-Resonant Mode		480		kHz
Keyboard Debounce Time	OSC IN = 480 kHz	9		11	ms
Oscillator Start-Up Time	$V_{DD} = V_{DD} \text{ Min}$		5.0		ms
Pulse Rate			10.0		pps
Break Time	Pin 9 @ V_{DD}		61.0		ms
	Pin 9 @ V_{SS}		67.0		ms
Interdigit Pause			800		ms

TP50981/TP50981A, TP50982/TP50982A, TP50985/TP50985A

เอกสารอ้างอิง

1. DIGITAL COMMUNICATION BY : MORRIS TISCHLER

2. เทคโนโลยี โทรคันท์ น.ต. รัชชัย เตื่อแฉวี



เอกสารนี้เป็นเอกสารที่สงวนไว้สำหรับการใช้งานเพื่อการศึกษาเท่านั้น ไม่อนุญาตให้นำไปใช้ประโยชน์ด้านการค้า
ไปว่ากรก็โดยทั้งสืบ ลึกทั้งห่าวเรีให้ดัดแปลงบื้อหา และต้องอ้างถึงถึงเจ้าของเอกสารทคครั้งทีมีการบวไปใช้